

Computer Architecture
Lecture 05


Set/Reset Latches

Artem Burmyakov, Alexander Tormasov

September 23, 2021




Recap: NOR gate

 

NOR = OR + NOT


Recap: NOR gate

 

NOR = OR + NOT

A	B	OR
1	1	1
1	0	1
0	1	1
0	0	0

Recap: NOR gate


 


NOR = OR + NOT



A	B	OR	NOR
1	1	1	0
1	0	1	0
0	1	1	0
0	0	0	1

If at least one input is “1”, NOR outputs “0”



Circuit Construction: 2 NOR gates

  


Circuit Construction: Input Pin S

  


Circuit Construction: Input Pins S and R

  

 
Circuit Construction: Cross-Coupling of NOR Gates



 
Circuit Construction: Cross-Coupling of NOR Gates



 
Circuit Construction: Cross-Coupling of NOR Gates



 
Circuit Construction: Cross-Coupling of NOR Gates



 
Circuit Construction: Cross-Coupling of NOR Gates



Circuit Construction: Output Pin Q

 


Circuit Construction: Output Pin Q

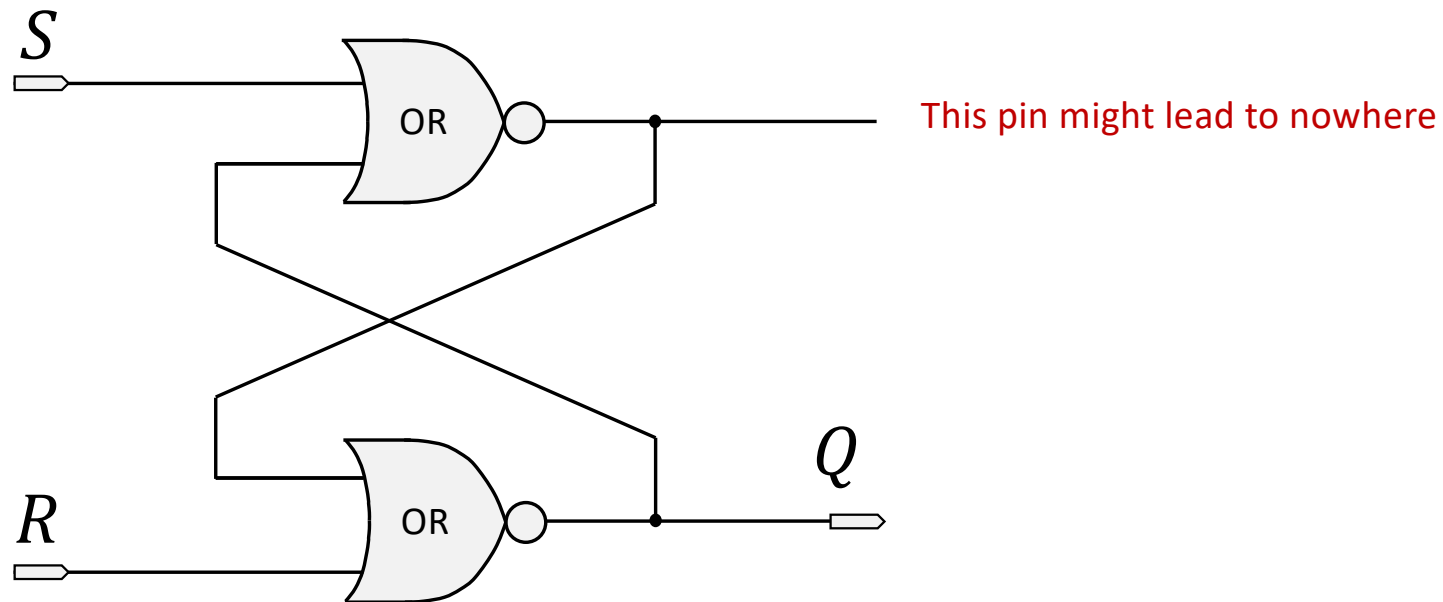


Circuit Analysis

 
OR gate outputs "1" if at least one input is "1"




Circuit Analysis

 


Circuit Analysis

 

Circuit Analysis

 


Circuit Analysis

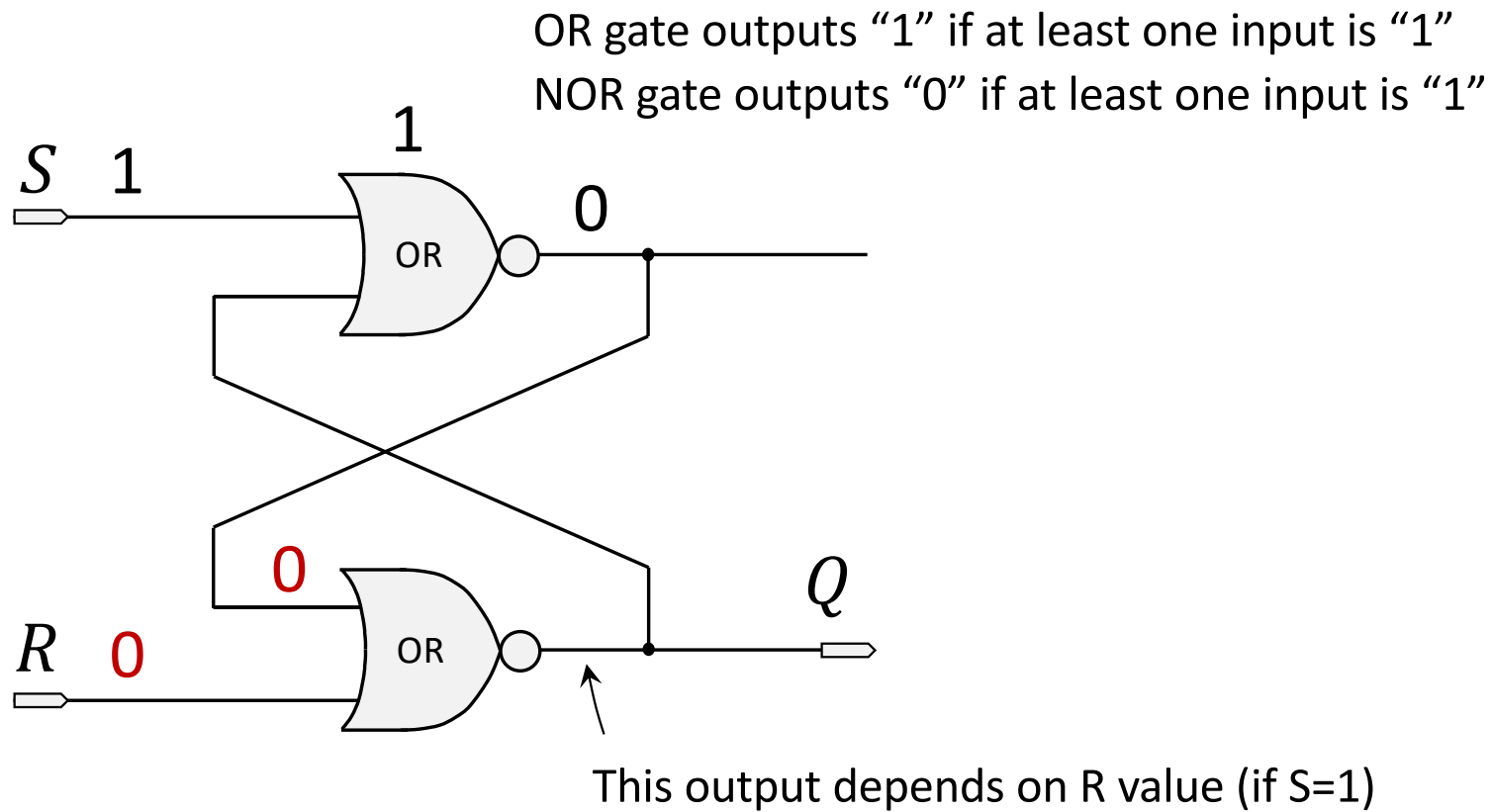


Circuit Analysis

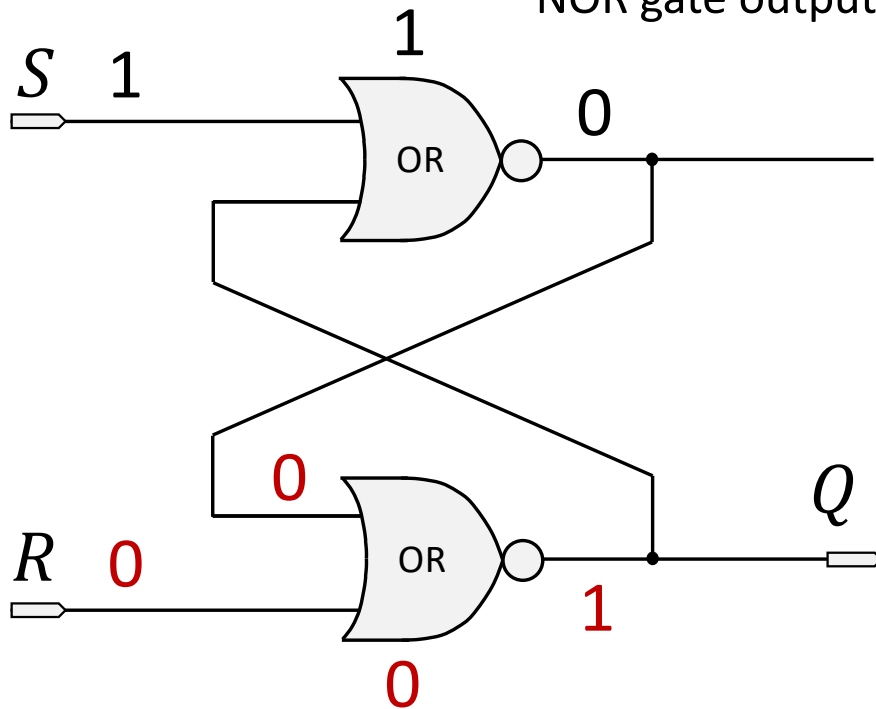OR gate outputs "1" if at least one input is "1"
NOR gate outputs "0" if at least one input is "1"




Circuit Analysis

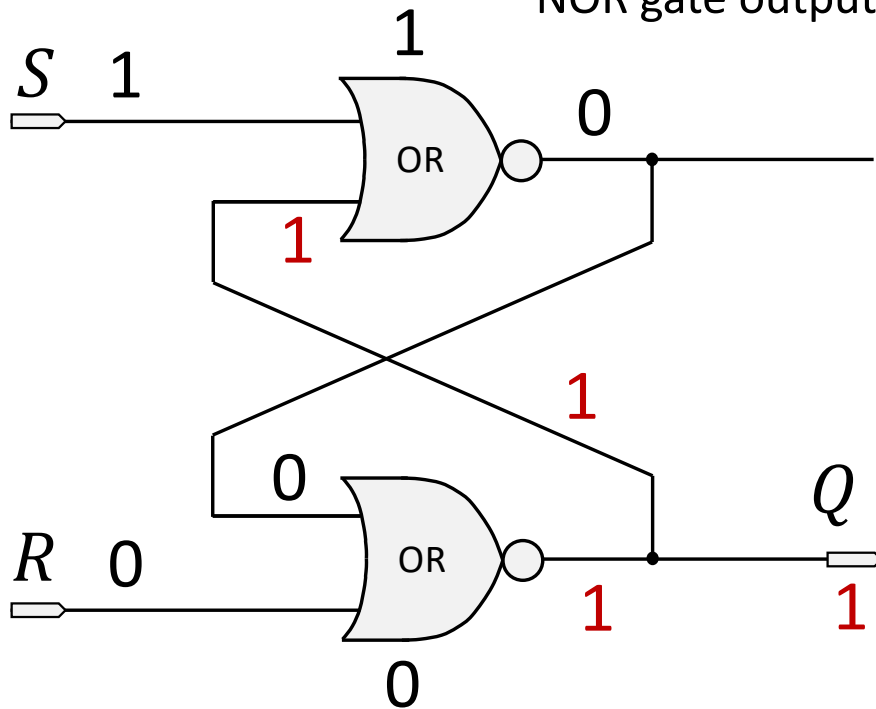OR gate outputs "1" if at least one input is "1"
NOR gate outputs "0" if at least one input is "1"




Circuit Analysis

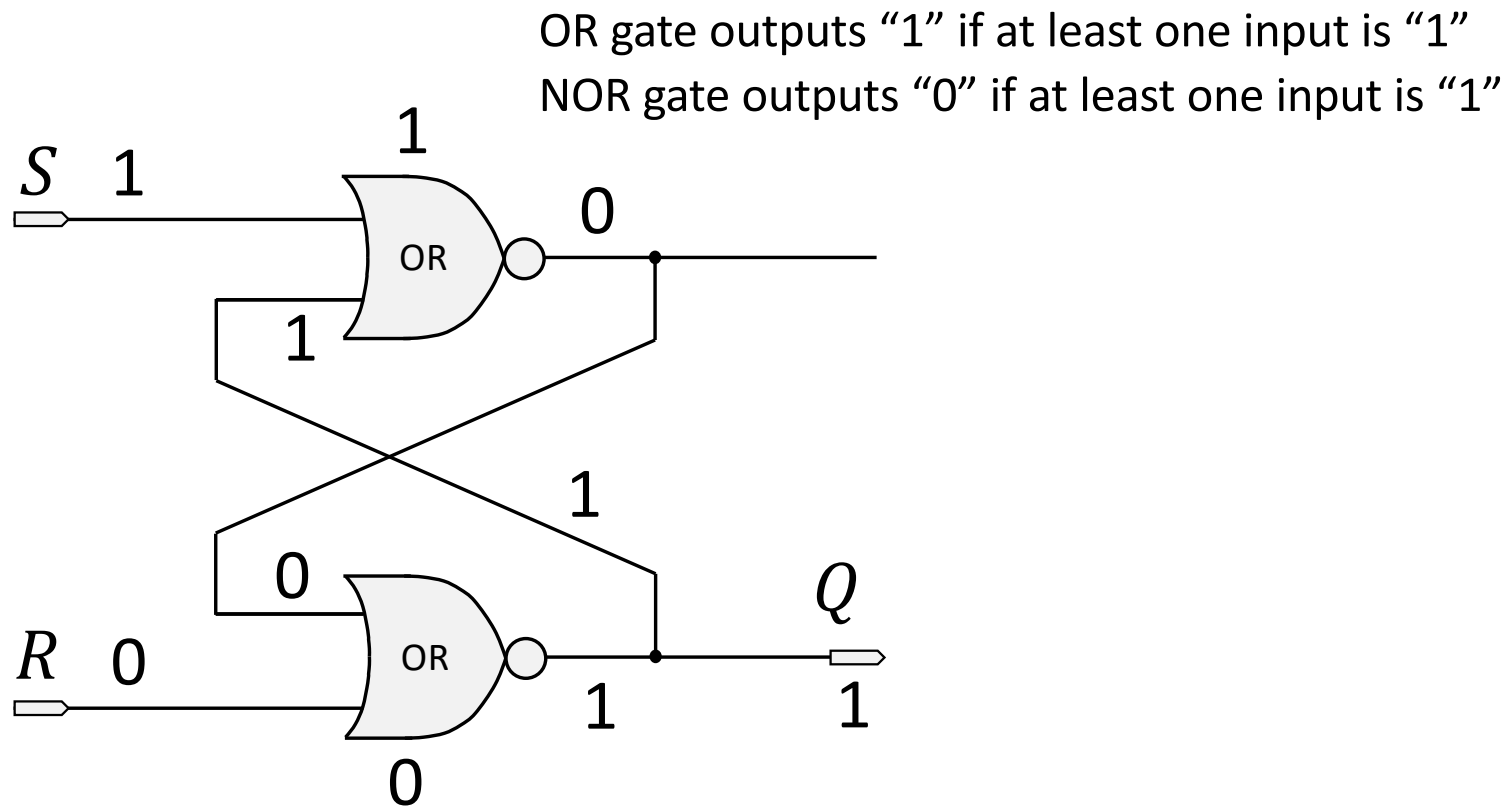

Does Q depend on the order of S and R arrival (e.g. S arrives first, and R arrives next) ?

Circuit Analysis

 


Does Q depend on the order of S and R arrival (e.g. S arrives first, and R arrives next?)

No; you can check it by hand


Circuit Analysis

Assume that S changes from “1” to “0”

 

Circuit Analysis


Assume that S changes from “1” to “0”

 

Circuit Analysis


Assume that S changes from "1" to "0"

 NOR gate outputs "0" if at least one input is "1"



Circuit Analysis


Assume that S changes from "1" to "0"

 

Circuit Analysis


Assume that S changes from “1” to “0”

 NOR gate outputs “0” if at least one input is “1”




Circuit Analysis

Assume that S changes from “1” to “0”

 


Q does not change and remains “1”

Circuit Analysis

 


Circuit Analysis

 Next, assume that R changes from "0" to "1"




Circuit Analysis

 Next, assume that R changes from "0" to "1"



Circuit Analysis

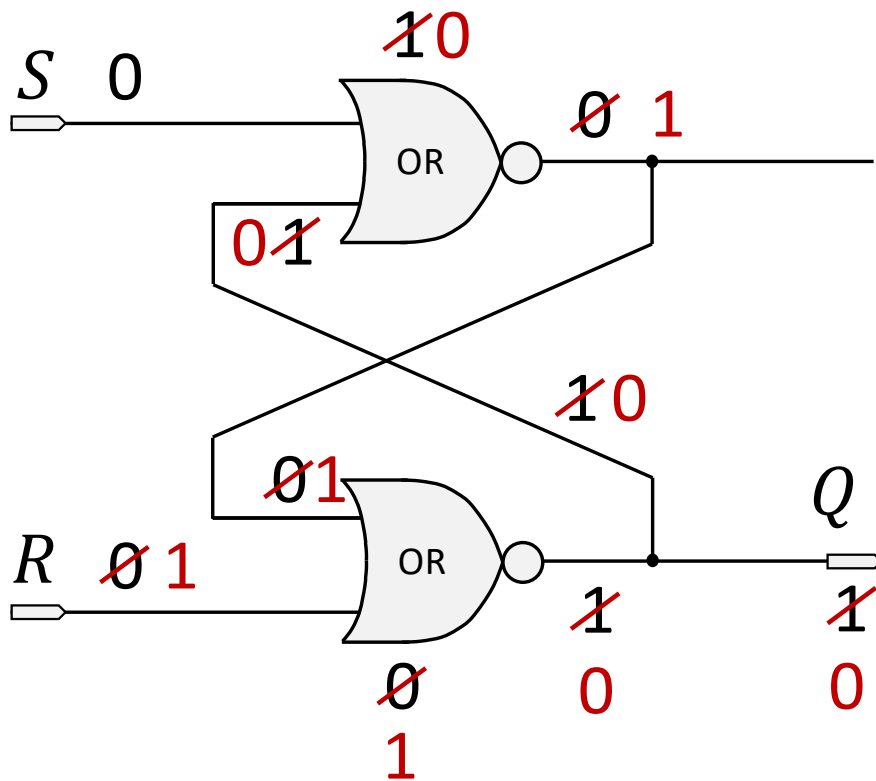
Next, assume that R changes from “0” to “1”



Q changes to “0”


Circuit Analysis

 Finally, let R to change from “1” back to “0”




Circuit Analysis

 Finally, let R to change from “1” back to “0”



Circuit Analysis

 
Finally, let R to change from “1” back to “0”



NOR gate outputs “0” if at least one input is “1”

Circuit Analysis

 
Finally, let R to change from “1” back to “0”



NOR gate outputs “0” if at least one input is “1”

Circuit Analysis

 
Finally, let R to change from “1” back to “0”



Q does not change

Summary


$S = 1, R = 0: \quad Q = 1$

 


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

 

 

Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$


$S = 0, R = 0:$ Q is stored by circuit

Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit


 


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

  


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit


 


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

 
 


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

 
 


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

 
 


Summary

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

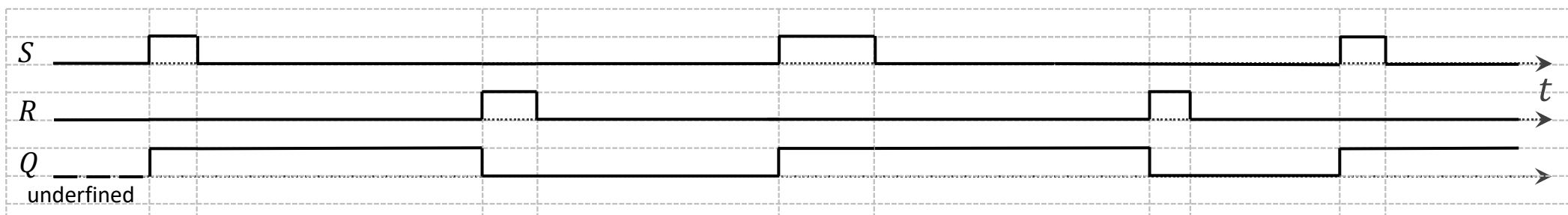 


Summary


$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

 


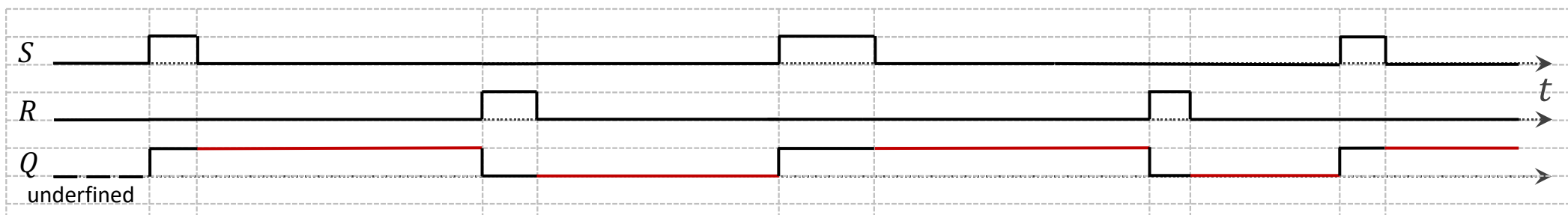The value of Q is stored by a circuit for some time
(due to complex physics processes)



S/R Latch Circuit

Stores 1 bit of information

 


$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$


$S = 0, R = 0:$ Q is stored by circuit

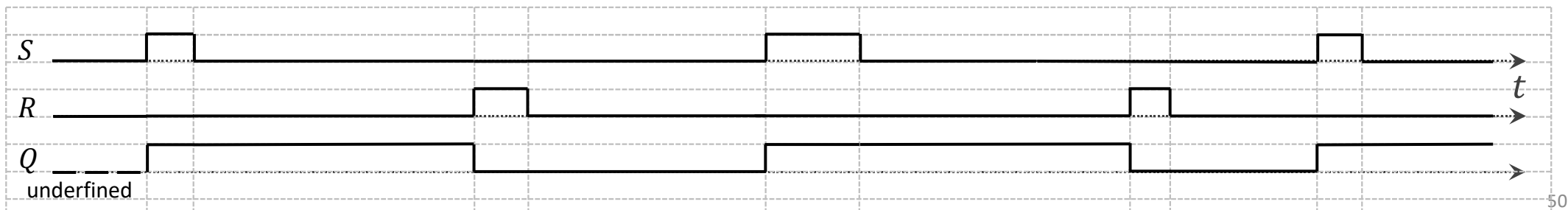The value of Q is stored by a circuit for some time
(due to complex physics processes)



S/R Latch Circuit

Stores 1 bit of information

 

$$S = 1, R = 0: \quad Q = 1$$

$$S = 0, R = 1: \quad Q = 0$$

$$S = 0, R = 0: \quad Q \text{ is stored by circuit}$$

Interpretation:


S – “set” pin

R – “reset” pin

Q – stored value

S/R Latch Circuit

Stores 1 bit of information

 

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

$S = 1, R = 1:$ An illegal combination

Interpretation:


S – “set” pin

R – “reset” pin

Q – stored value

S/R Latch Circuit

Stores 1 bit of information

 

$S = 1, R = 0:$ $Q = 1$

$S = 0, R = 1:$ $Q = 0$

$S = 0, R = 0:$ Q is stored by circuit

$S = 1, R = 1:$ An illegal combination


Interpretation:

S – “set” pin

R – “reset” pin


Q – stored value

S/R Latch: Truth Table

 

S	R	Q
1	0	1
0	1	0
0	0	Q^{prev}
1	1	Illegal inputs

S/R Latch: Truth Table

 


S	R	Q
1	0	1
0	1	0
0	0	Q^{prev}
1	1	Illegal inputs

Cross-coupled connection – the key feature of latches:
the output of one gate serves as an input to another gate


S/R Latch: Multiple Implementations Available

 1) Implementation by using NOR logic gates:




S/R Latch: Multiple Implementations Available

 1) Implementation by using NOR logic gates:




2) by using NAND logic gates:

 


S/R Latch: Multiple Implementations Available

 1) Implementation by using NOR logic gates:









2) by using NAND logic gates:

 


These representations are logical oversimplified representations, hiding many implementation details

Recap: Each logic gate is an electronic circuit, implemented by using transistors

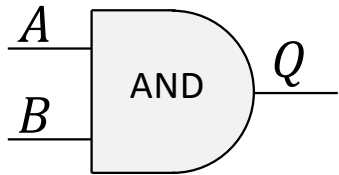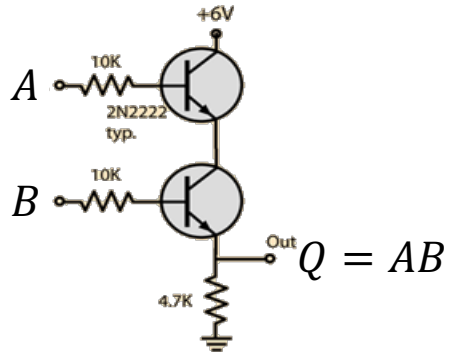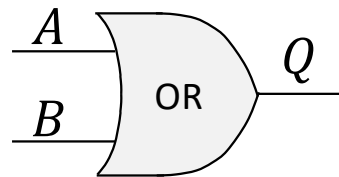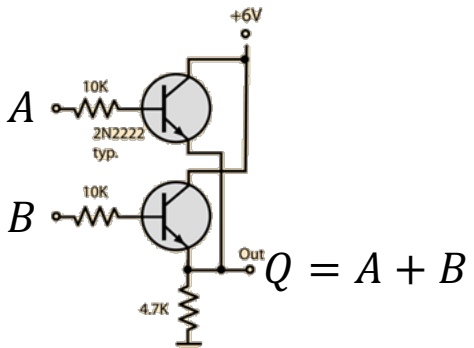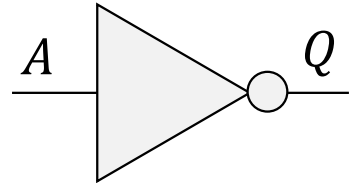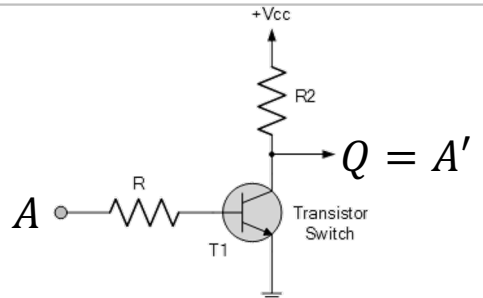Logic Gate	Symbolic Representation	Truth Table	Implementation with Transistors															
AND		<table><tr><th>A</th><th>B</th><th>Q=AB</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Q=AB	0	0	0	1	0	0	0	1	0	1	1	1	
A	B	Q=AB																
0	0	0																
1	0	0																
0	1	0																
1	1	1																
OR		<table><tr><th>A</th><th>B</th><th>Q=A+B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Q=A+B	0	0	0	1	0	1	0	1	1	1	1	1	
A	B	Q=A+B																
0	0	0																
1	0	1																
0	1	1																
1	1	1																
NOT		<table><tr><th>A</th><th>Q=A'</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	Q=A'	0	1	1	0										
A	Q=A'																	
0	1																	
1	0																	


Transistor implementations are taken from <http://hyperphysics.phy-astr.gsu.edu/hbase/Electronic/trangate.html#c1> and https://www.electronics-tutorials.ws/logic/logic_4.html

Latch Logical representation:

 


Before usage, latch is initialized by one of these input combinations:
either $R = 1$ & $S = 0$, or $S = 1$ & $R = 0$;

 
Electrical circuit implementation (one of many):



Latch Logical representation:

 


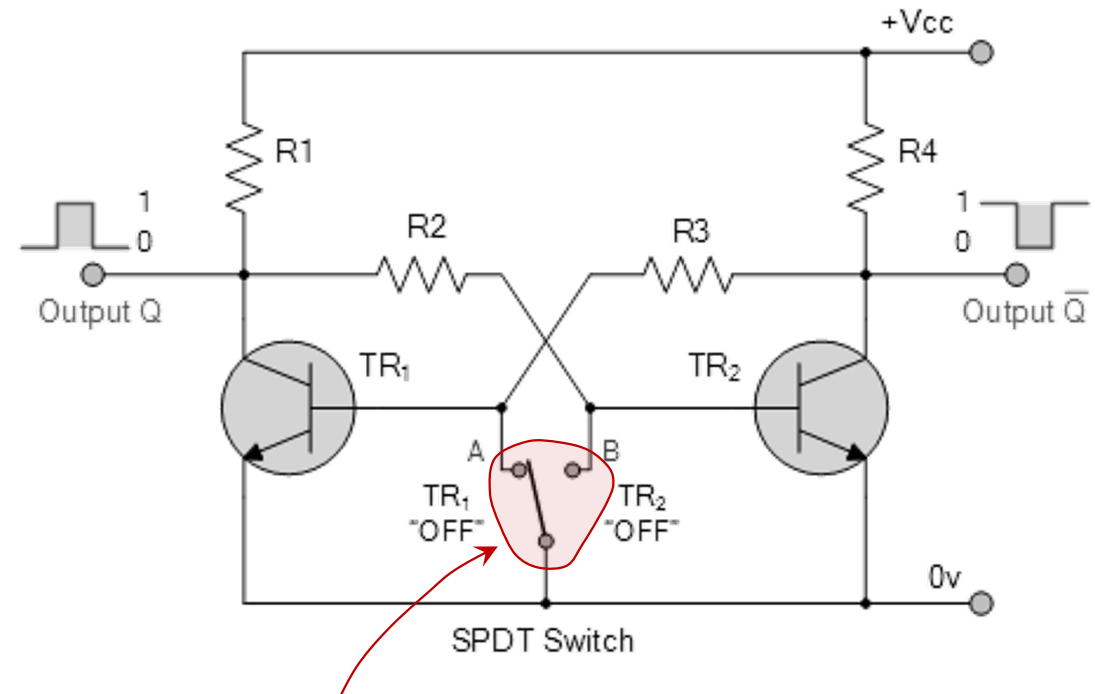Electrical circuit implementation (one of many):



Switch to control
the input values of S and R
(assumed to have 3 positions)


Latch Logical representation:

 

Electrical circuit implementation (one of many):


If S and R are "0"s, Q might remain "1";
 Latch is not an "endless engine", it has a
 power supply

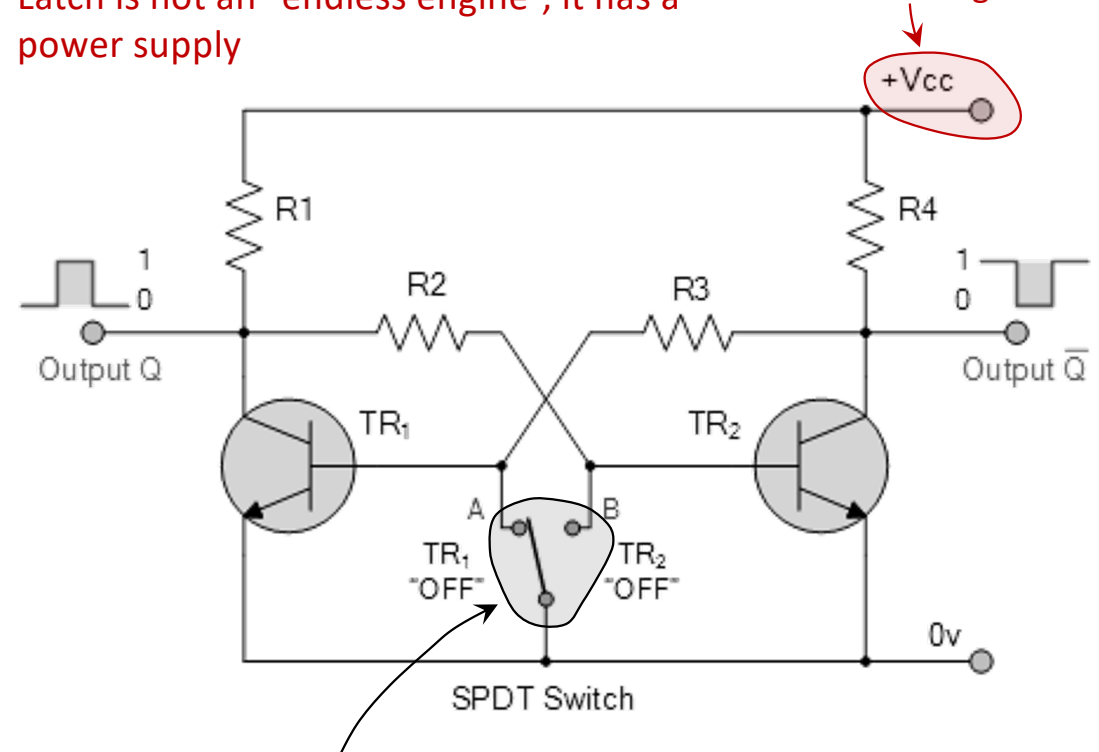There is an external
 power supply, to support
 latch functioning




Switch to control
 the input values of S and R
 (assumed to have 3 positions)

Latch Logical representation:

 


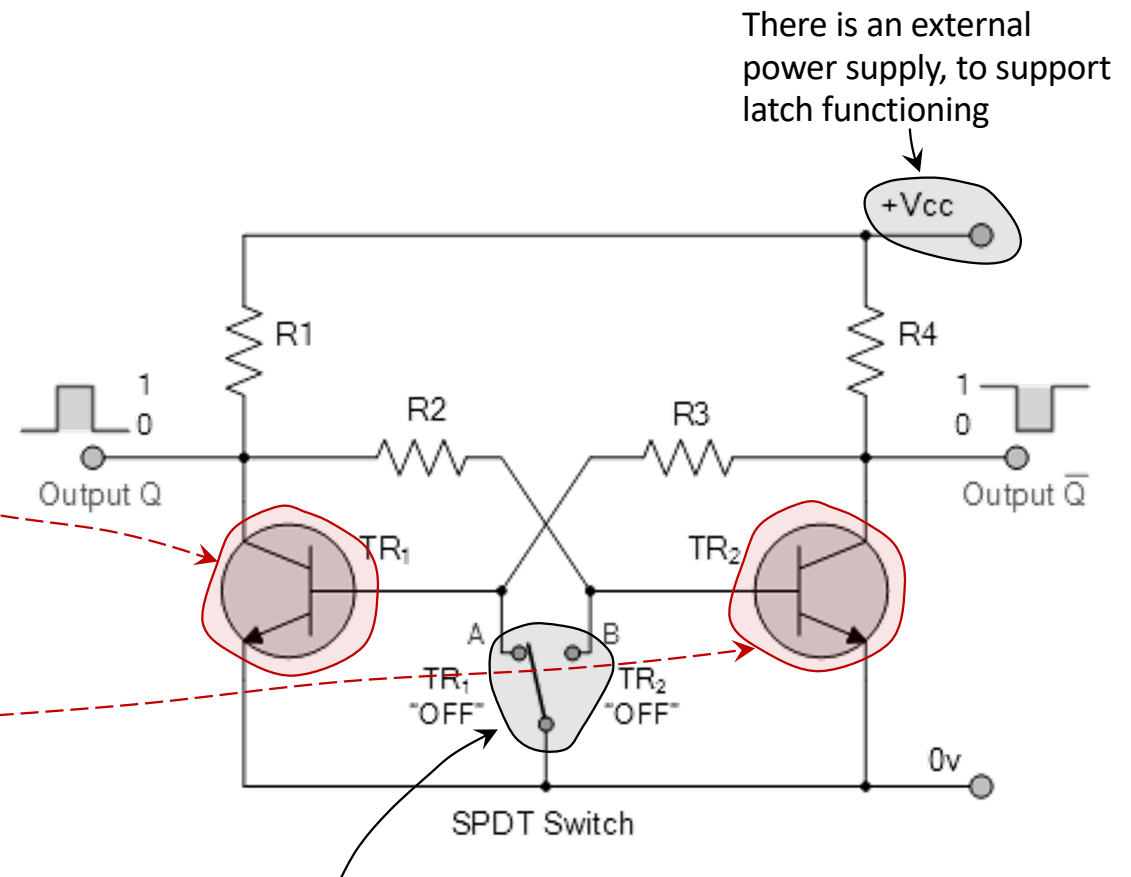Electrical circuit implementation (one of many):




Switch to control
the input values of S and R
(assumed to have 3 positions)

Latch Logical representation:

 

 Electrical circuit implementation (one of many):




Cross-coupled connections between gates and corresponding transistors

State Transition Diagram for a Latch



At this state, Q and \bar{Q} are typically set to 0, for most of the available hardware implementations

 Uninitialized state
(Q, \bar{Q} - arbitrary)





State Transition Diagram for a Latch

 
 
At this state, Q and \bar{Q} are typically set to 0, for most of the available hardware implementations





State Transition Diagram for a Latch

 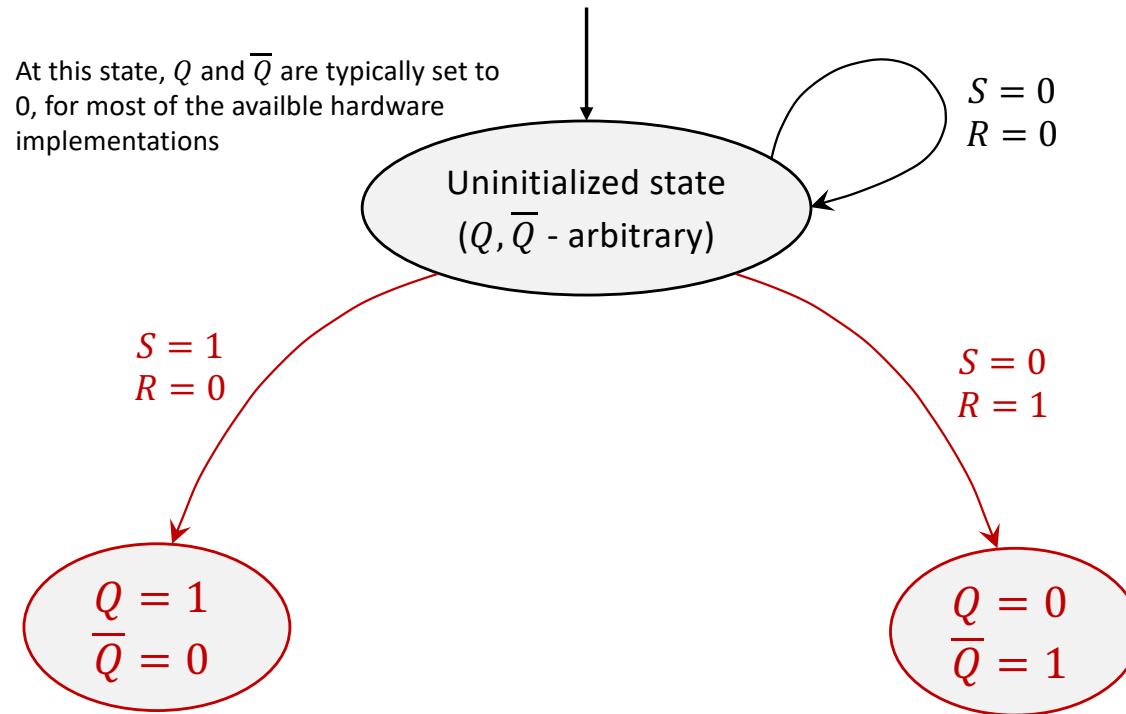



State Transition Diagram for a Latch

 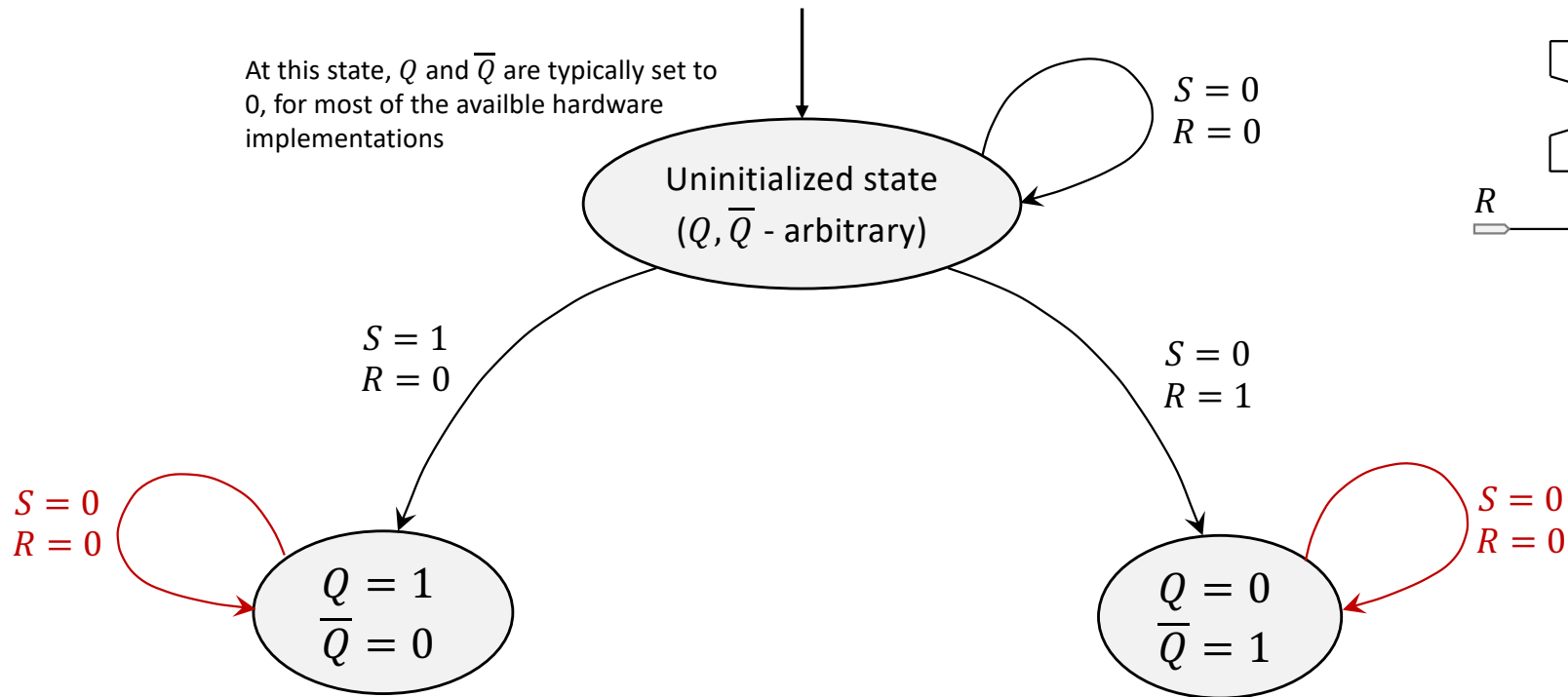



State Transition Diagram for a Latch

  



State Transition Diagram for a Latch

 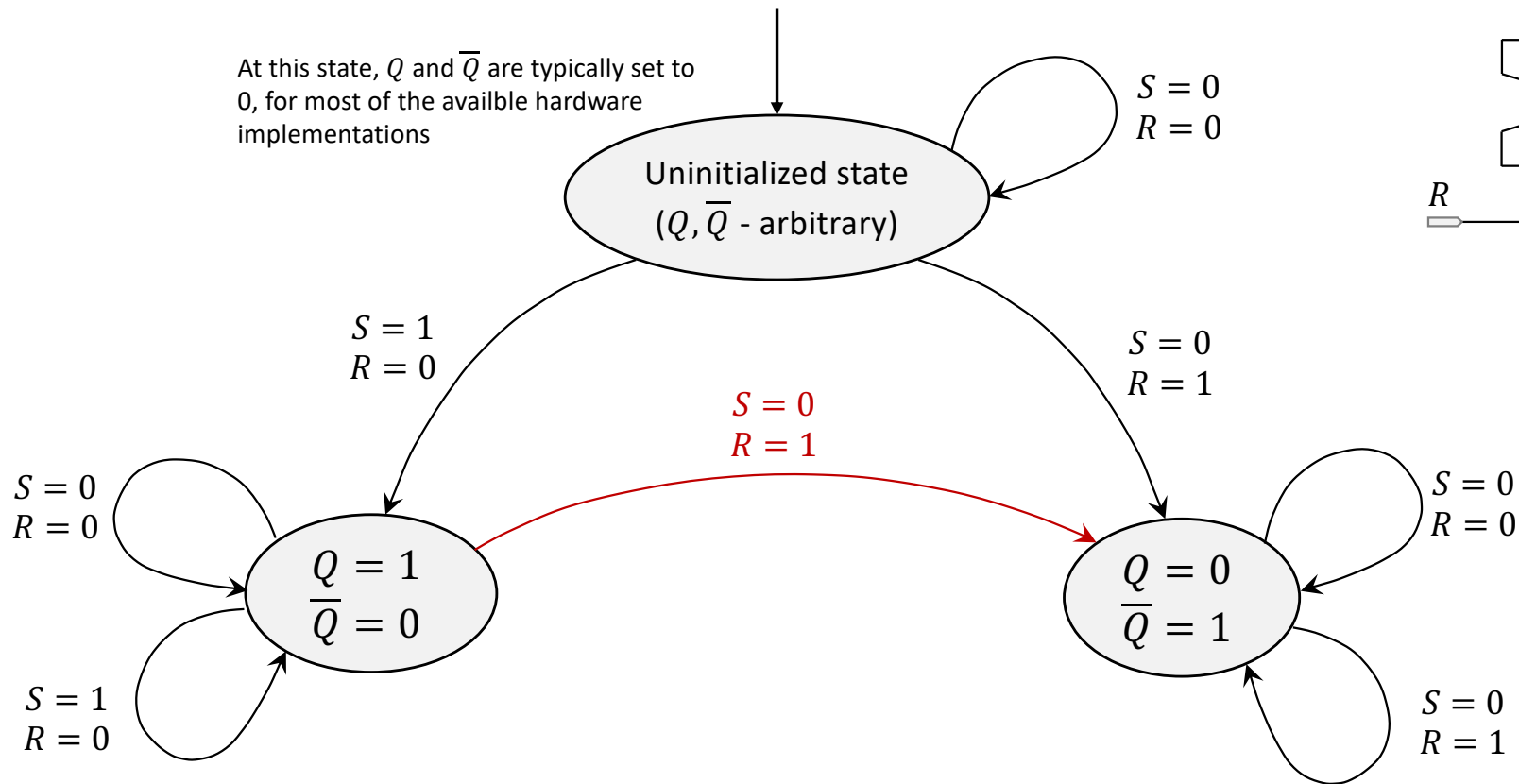



State Transition Diagram for a Latch

 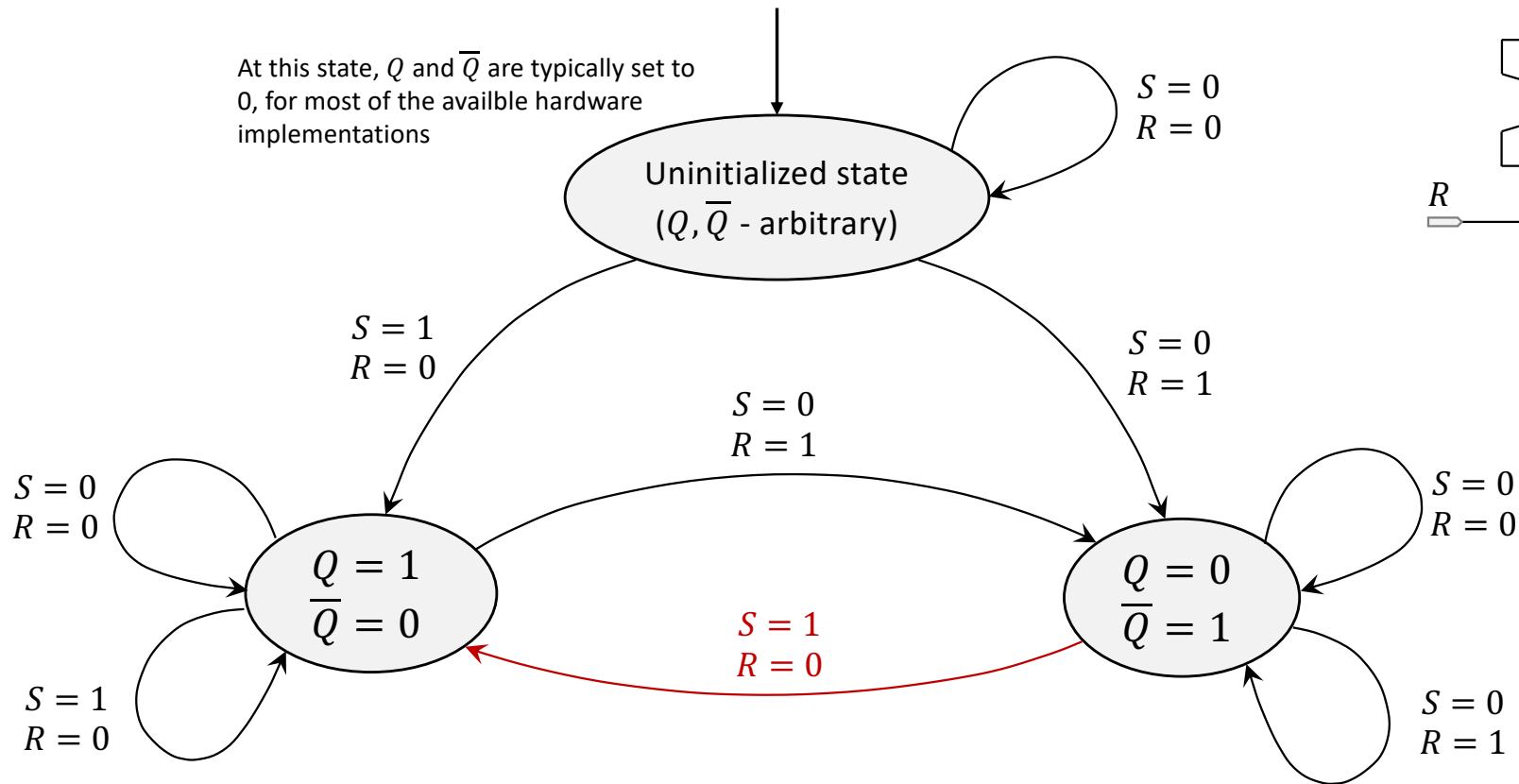



State Transition Diagram for a Latch

 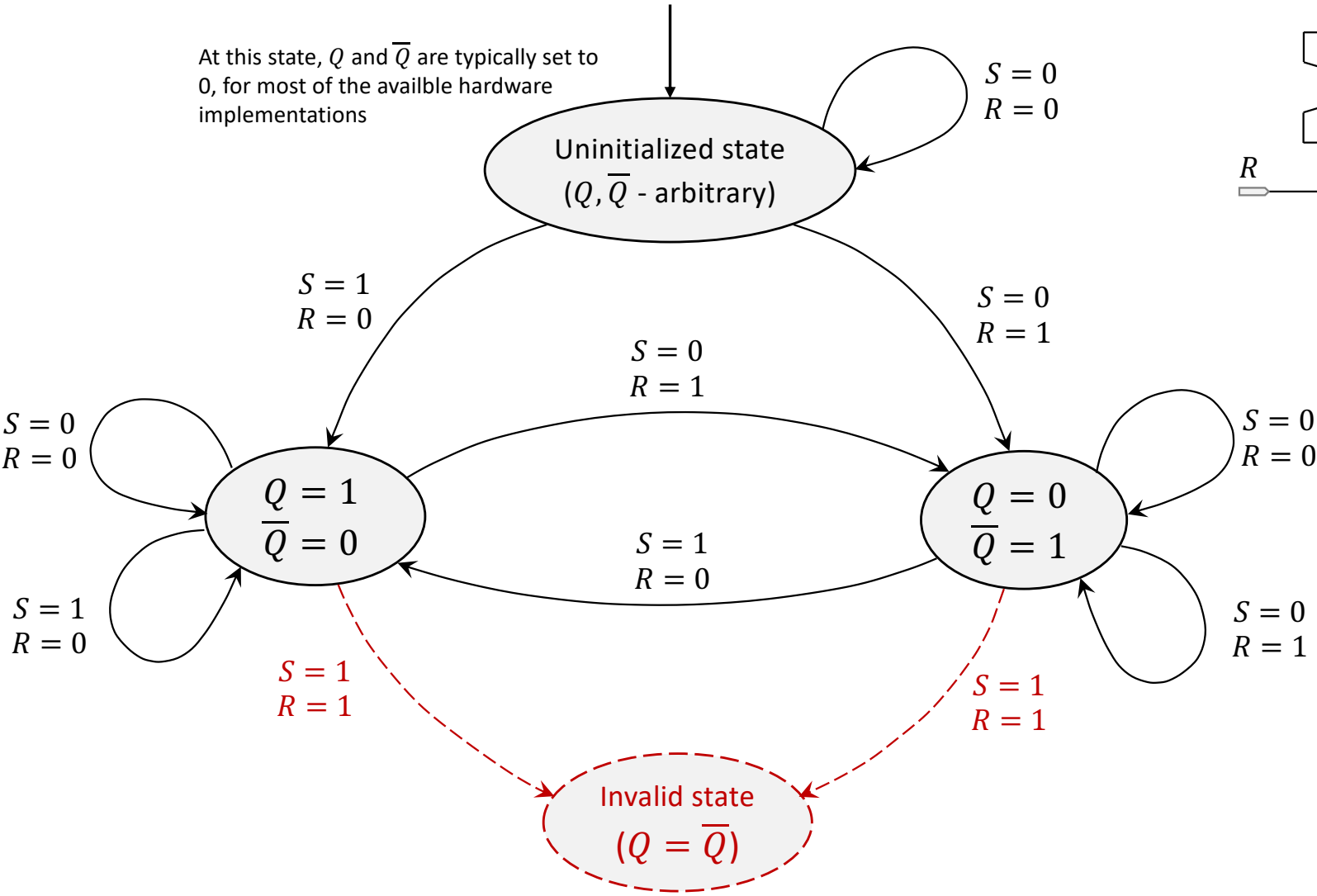


State Transition Diagram for a Latch

  



State Transition Diagram for a Latch

  

State-Transition Diagram for a Latch

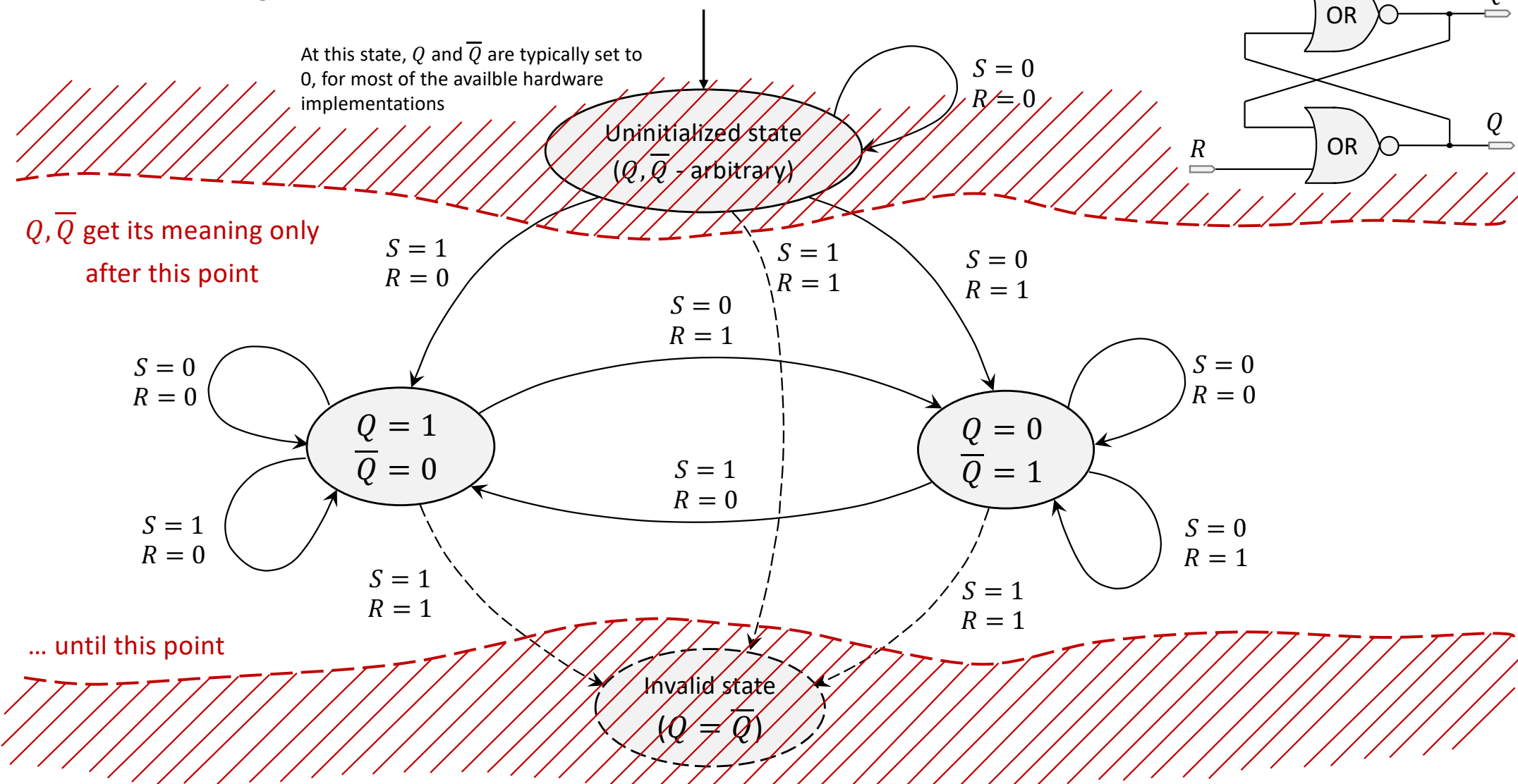

State-Transition Diagram for a Latch

  

A reversible state?

State-Transition Diagram for a Latch

