

Computer Architecture
Tutorial 12

Verilog HDL: A Brief Syntax Overview

Artem Burmyakov, Alexander Tormasov

November 11, 2021




Recap: Characteristics of Combinational Logic Circuits

- 1) An output signal depends just on input signals
- 2) Comprised of logic gates, such as AND, OR, etc., and wires connecting them
- 3) Output signal is updated after the change of input signals, subject to propagation delay
- 4) Use no memory units, such as registers
- 5) Typically, no clock signal is present (exceptions might apply)

Key advantage: Fast (thus, used in such components, as processor ALU)

Key disadvantage: No support of inputs synchronization (will be discussed later)

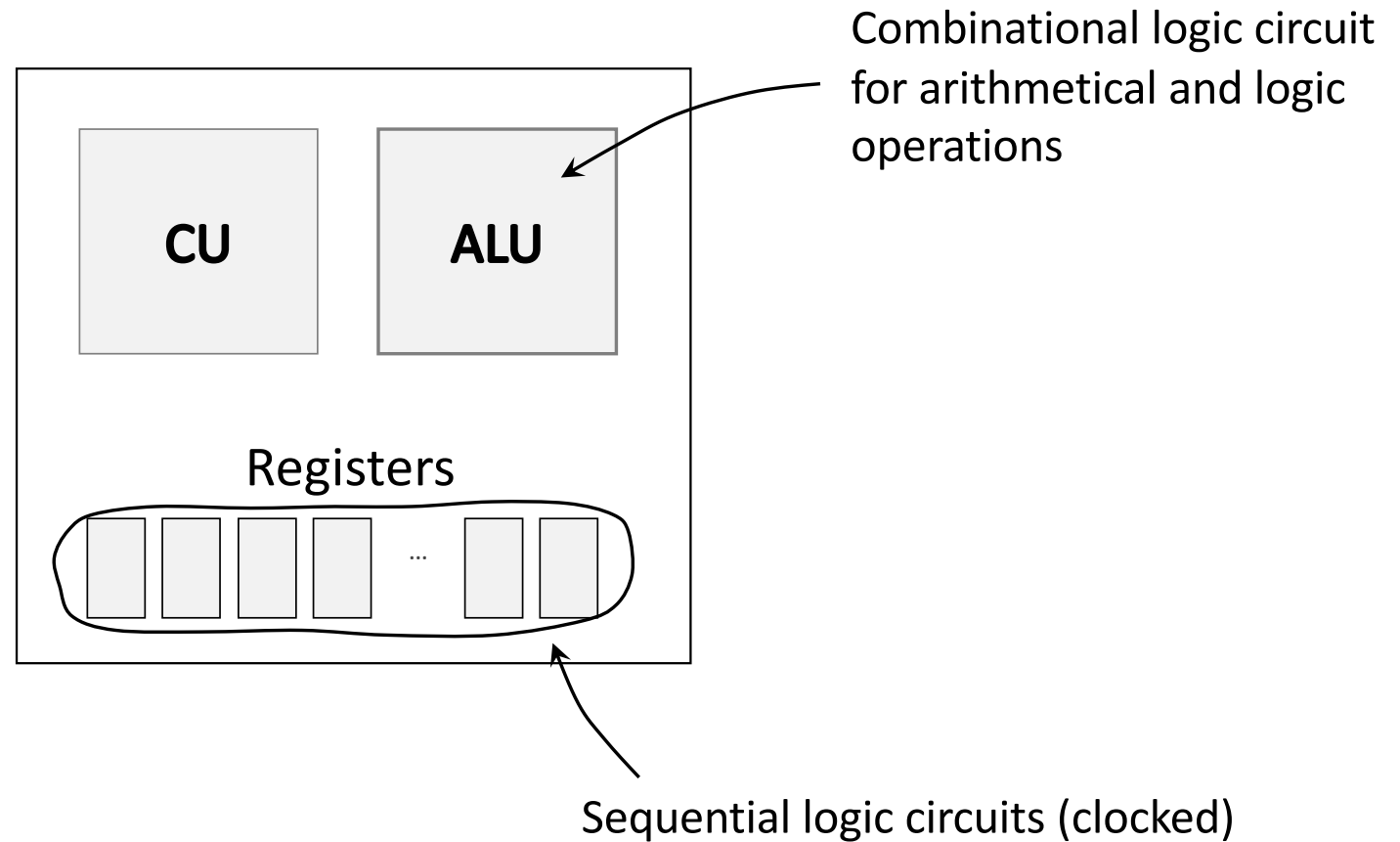
Types of Logic Circuits for CPU Components




Recap: Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	Higher (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	Simpler , smaller (<i>Note</i> : an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity)	More complex , larger
Sample Use Cases	Arithmetic-Logic Unit (ALU); Small fast peripheral circuits supporting CPU operation	Register files; Most of the circuits containing memory elements

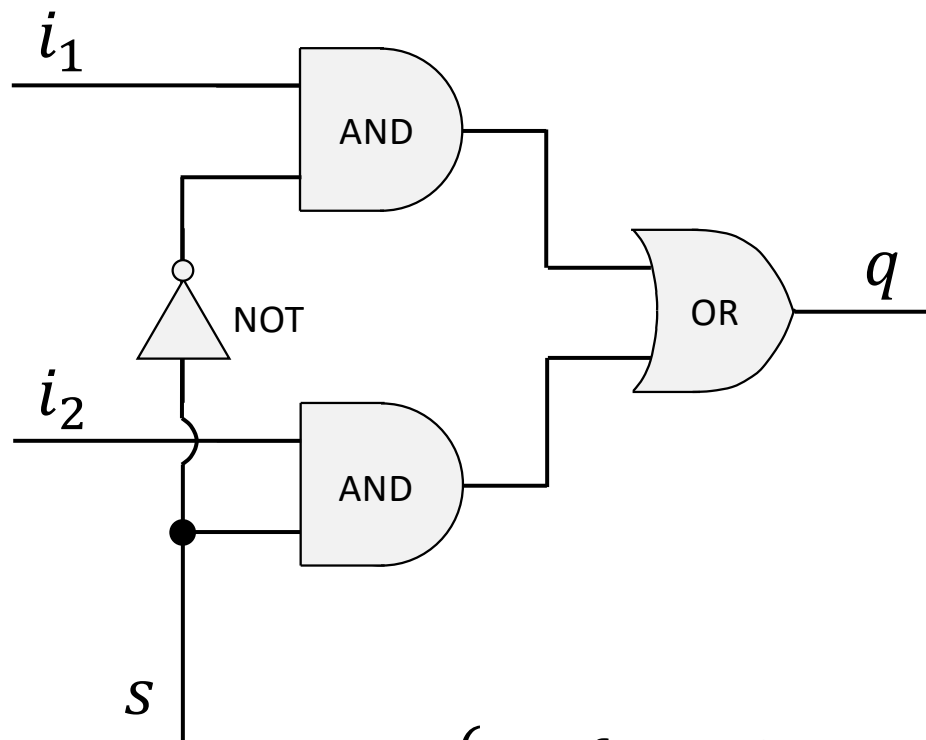2-to-1 Multiplexor: Digital Circuit by Using Logic Gates




 2-to-1 Multiplexor: Digital Circuit by Using Logic Gates



Multiplexer – a hardware module


Multiplexor Implementation in Verilog

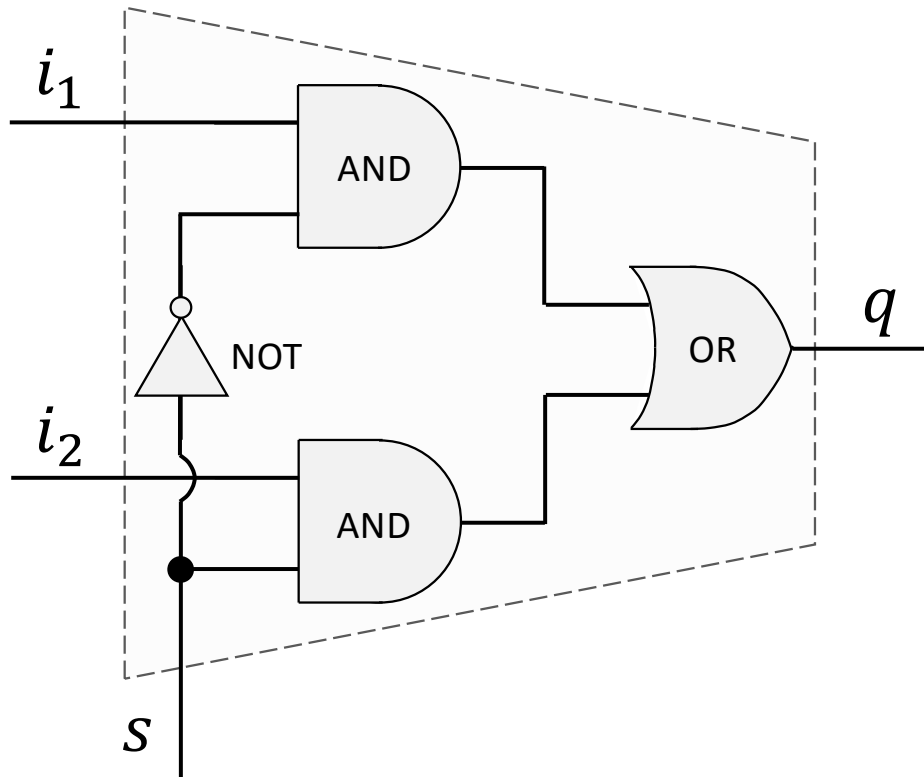

Multiplexer – a hardware module

1	module mux
9	endmodule

Multiplexor Implementation in Verilog

 


Multiplexer – a hardware module:

i_1, i_2, s – input pins;

q – output pin

1	module mux
9	endmodule


Multiplexor Implementation in Verilog

 

Multiplexer – a hardware module:
 i_1, i_2, s – input pins;
 q – output pin

1	module mux (i_1, i_2, s, q);
9	endmodule

Multiplexor Implementation in Verilog

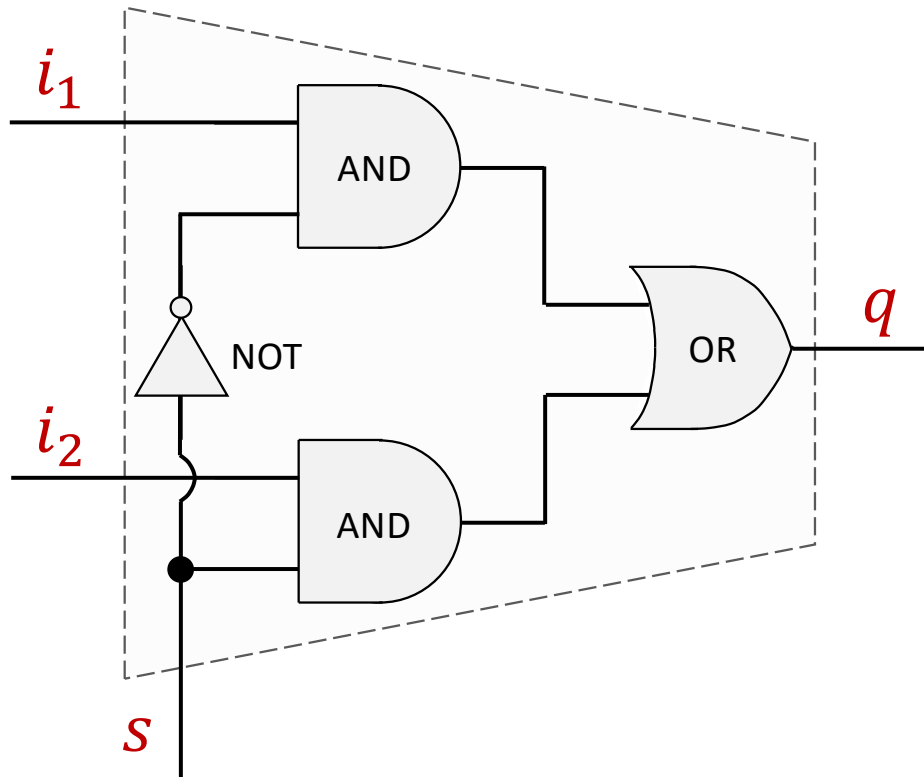


Multiplexer – a hardware module:
 i_1, i_2, s – input pins;
 q – output pin

The list of all input and output pins
of a module

1	module mux (i_1, i_2, s, q);
9	endmodule


Multiplexor Implementation in Verilog

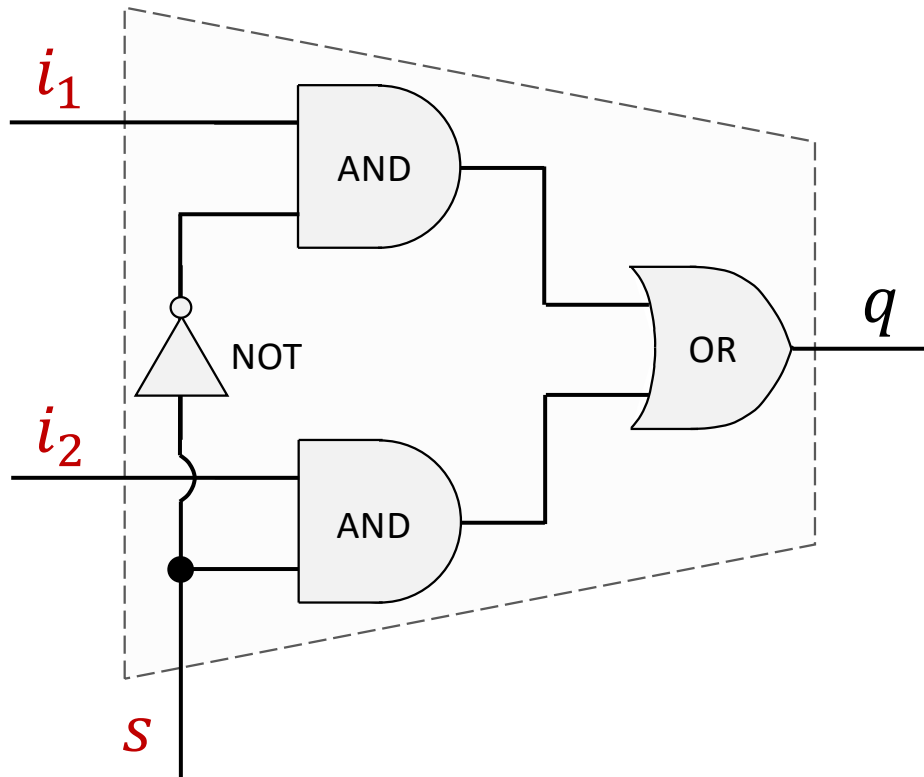

Multiplexer – a hardware module:
 i_1, i_2, s – input pins;
 q – output pin

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
9	endmodule


Multiplexor Implementation in Verilog

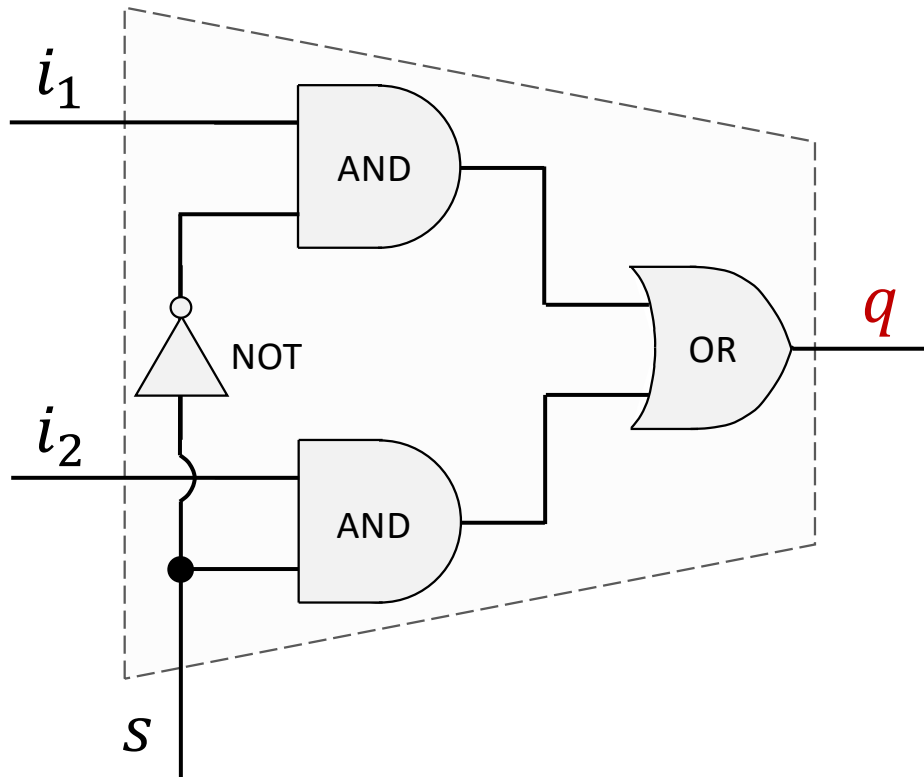

Multiplexer – a hardware module:
 i_1, i_2, s – input pins;
 q – output pin


1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
9	endmodule

Multiplexor Implementation in Verilog

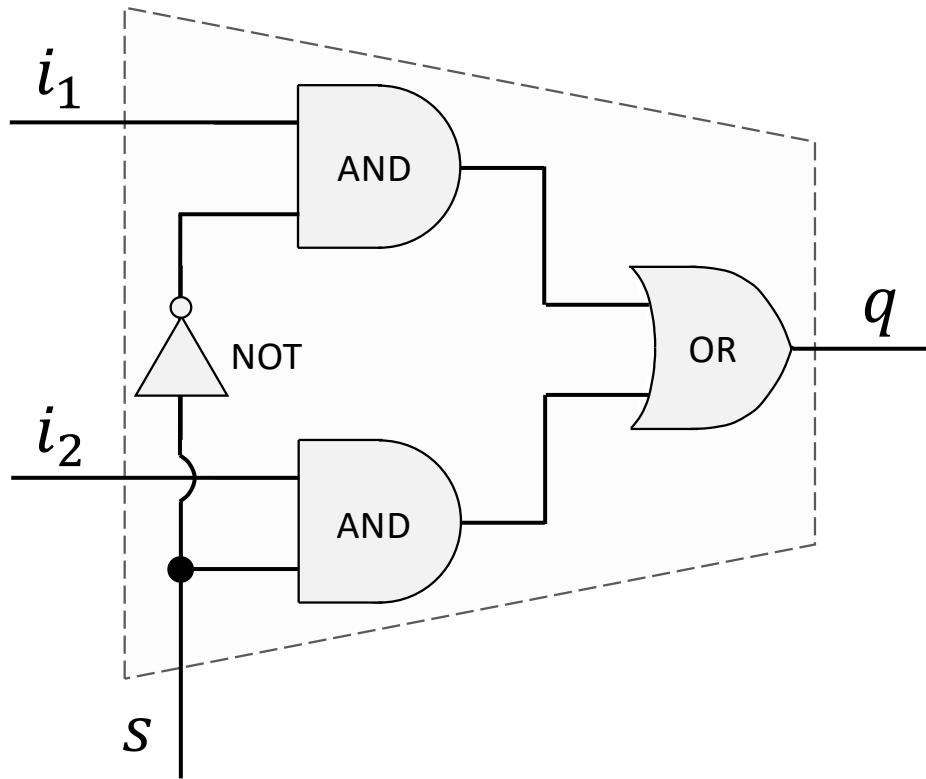

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
9	endmodule


Multiplexor Implementation in Verilog

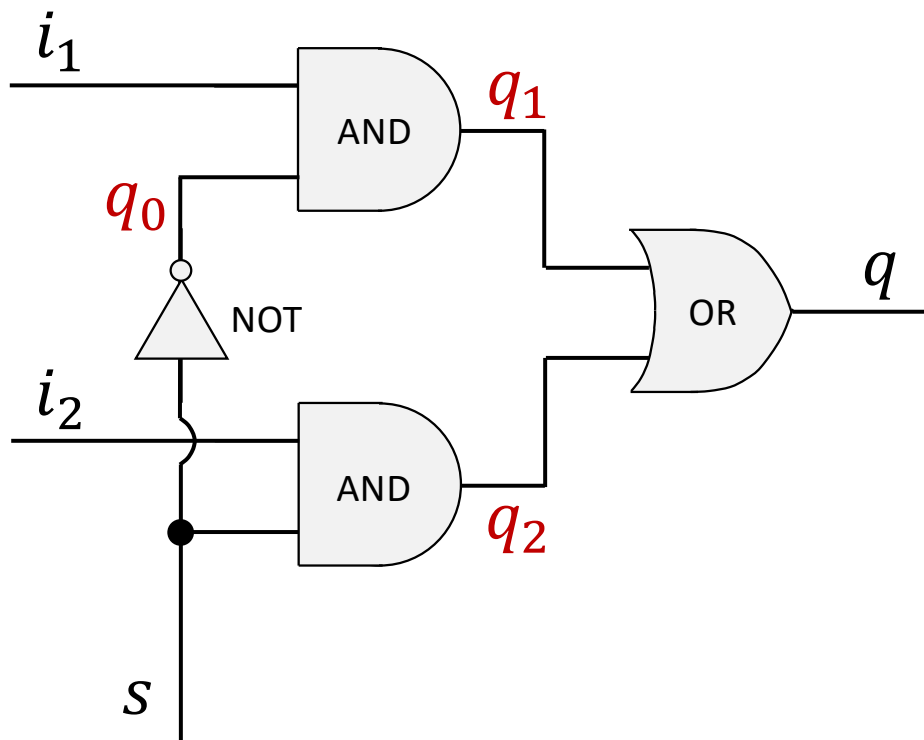

q_0, q_1, q_2 - internal wires of our hardware module

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
9	endmodule


Multiplexor Implementation in Verilog

 

q_0, q_1, q_2 - internal wires of our hardware module

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
9	endmodule

Multiplexor Implementation in Verilog

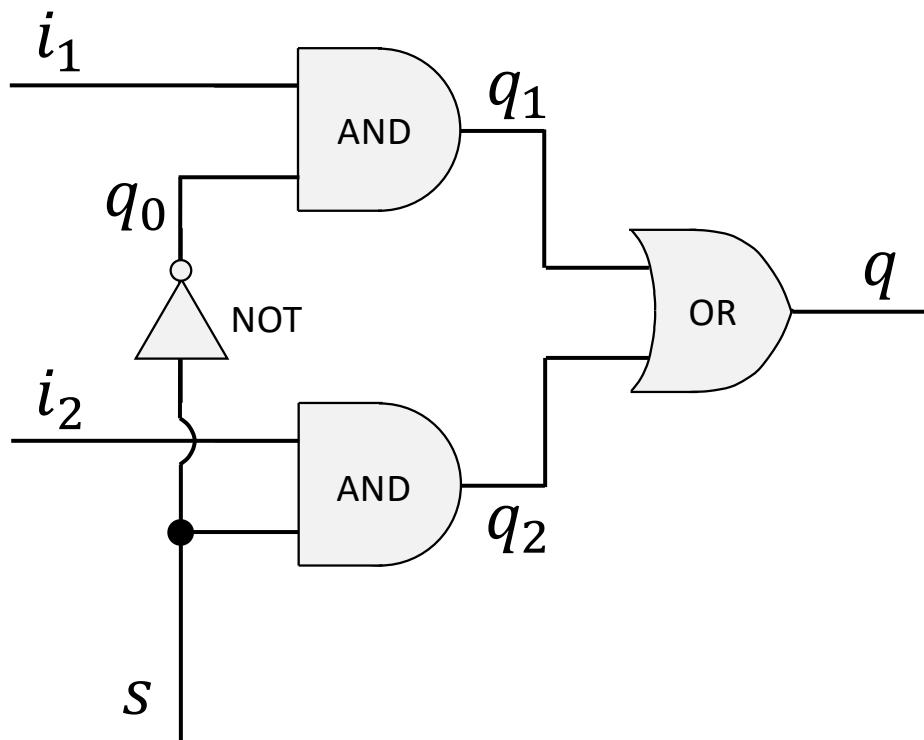


q_0, q_1, q_2 - internal wires of our hardware module

Input and output pins are always of type “wire”


1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
9	endmodule

Multiplexor Implementation in Verilog

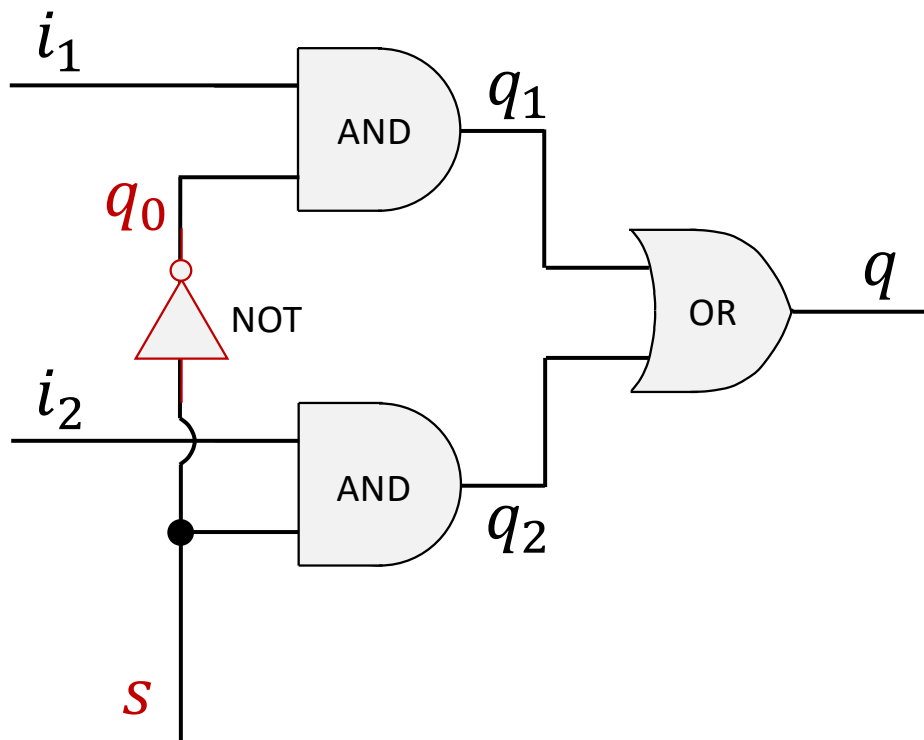

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
9	endmodule


Multiplexor Implementation in Verilog

 

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
9	endmodule

Verilog provides built-in primitive hardware modules (not, add, or, etc.)


Multiplexor Implementation in Verilog

 

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
9	endmodule

Verilog provides built-in primitive hardware modules (not, add, or, etc.)

Multiplexor Implementation in Verilog

 


1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
9	endmodule

Verilog provides built-in primitive hardware modules (not, add, or, etc.)

Output pins (wires) are listed first (similarity to MIPS assembler)


Multiplexor Implementation in Verilog

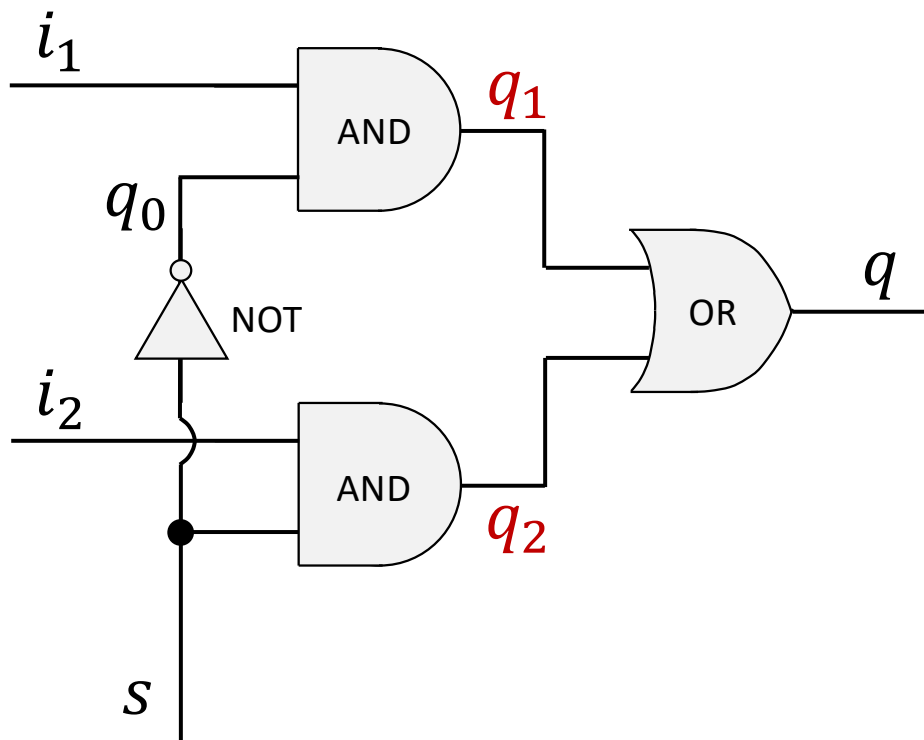

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
9	endmodule

Verilog provides built-in primitive hardware modules (not, add, or, etc.)


Multiplexor Implementation in Verilog

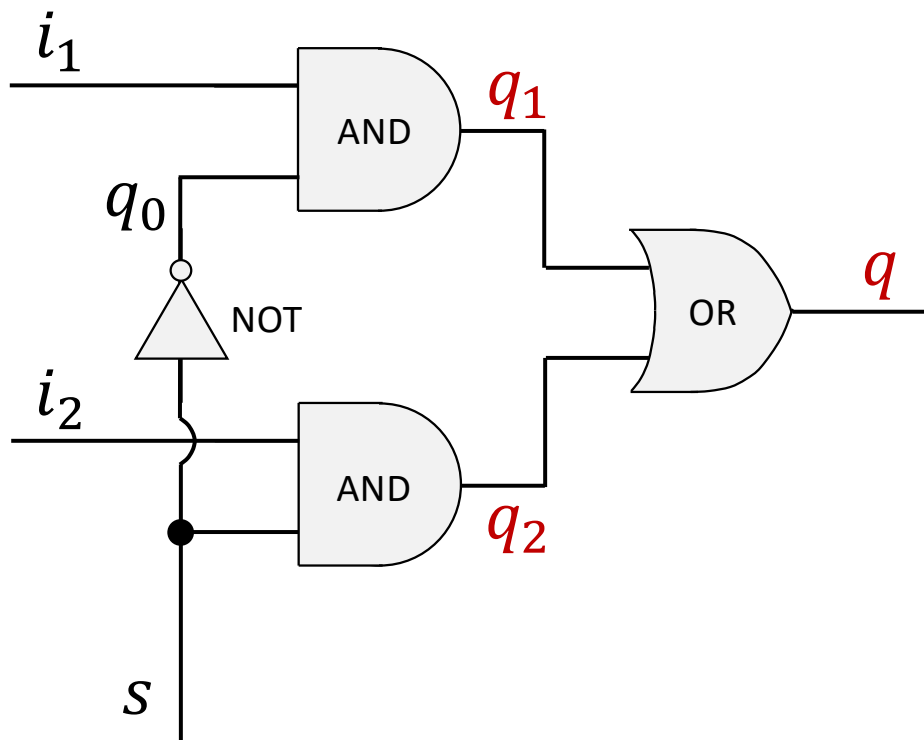

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
8	or (q, q1, q2);
9	endmodule

Verilog provides built-in primitive hardware modules (not, add, or, etc.)

Multiplexor Implementation in Verilog

 

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
8	or (q, q1, q2);
9	endmodule

Syntax Variation for Module Declaration in Verilog

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
8	or (q, q1, q2);
9	endmodule

Syntax Variation for Module Pins Declaration in Verilog

1	module mux (
2	input i1,
3	input i2,
4	input s,
5	output q
6);
7	wire q0, q1, q2;
8	not (q0, s);
9	and (q1, i1, q0);
10	and (q2, i2, s);
11	or (q, q1, q2);
12	endmodule

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
8	or (q, q1, q2);
9	endmodule

These two declarations are equivalent


Some Verilog Operators

Operator Symbol	Function/Purpose	Operands
~	Bitwise negation	Unary
&	Bitwise AND	Binary
	Bitwise OR	Binary
^	Bitwise XOR	Binary
^~	Bitwise XNOR	Binary
?:	Conditional	Ternary

Some Verilog Operators

Operator Symbol	Function/Purpose	Operands
<code>~</code>	Bitwise negation	Unary
<code>&</code>	Bitwise AND	Binary
<code> </code>	Bitwise OR	Binary
<code>^</code>	Bitwise XOR	Binary
<code>^~</code>	Bitwise XNOR	Binary
<code>?:</code>	Conditional	Ternary

Example of possible implementations:

 


Block diagram impl.

Some Verilog Operators

Operator Symbol	Function/Purpose	Operands
~	Bitwise negation	Unary
&	Bitwise AND	Binary
	Bitwise OR	Binary
^	Bitwise XOR	Binary
^~	Bitwise XNOR	Binary
?:	Conditional	Ternary

Example of possible implementations:

 

Block diagram impl.


```
and(q1, i1, q0);
```

Verilog implementation by
using “and” primitive

Some Verilog Operators

Operator Symbol	Function/Purpose	Operands
~	Bitwise negation	Unary
&	Bitwise AND	Binary
	Bitwise OR	Binary
^	Bitwise XOR	Binary
^~	Bitwise XNOR	Binary
?:	Conditional	Ternary

Example:

 

Block diagram impl.

```
and(q1, i1, q0);
```

Verilog implementation by
using “and” primitive

```
assign q1 = ( i1 & q0);
```

Verilog implementation by
a continuous assignment of an expression

Continuous Assignment in Verilog

```
assign q1 = ( i1 & q0);
```

Whenever some input is changed, output q1 is updated as well

Multiplexer Implementation: Alternatives

Implementation by using “and”, “or”, and “not” primitives:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
8	or (q, q1, q2);
9	endmodule

Implementation by using continuos assignments and “&”, “|”, and “~” operators:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	assign q0 = (~s);
6	assign q1 = (i1 & q0);
7	assign q2 = (i2 & s);
8	assign q = (q1 q2);
9	endmodule

Multiplexer Implementation: Alternatives

Implementation by using “and”, “or”, and “not” primitives:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	not (q0, s);
6	and (q1, i1, q0);
7	and (q2, i2, s);
8	or (q, q1, q2);
9	endmodule

Implementation by using continuous assignments and “&”, “|”, and “~” operators:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	assign q0 = (~s);
6	assign q1 = (i1 & q0);
7	assign q2 = (i2 & s);
8	assign q = (q1 q2);
9	endmodule

Multiplexer Implementation: Syntax Variations

A more *compact* program code:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	assign q = (i1 & ~s) (i2 & s);
5	endmodule

Implementation by using continuous assignments and “&”, “|”, and “~” operators:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	wire q0, q1, q2;
5	assign q0 = (~s);
6	assign q1 = (i1 & q0);
7	assign q2 = (i2 & s);
8	assign q = (q1 q2);
9	endmodule

Statement “assign” vs. Procedural Block “always” in Verilog

Implementation based on continuous assignment:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	assign q = (i1 & ~s) (i2 & s);
5	endmodule

← We force q to be updated whenever i1, or i2, or s changes

Statement “assign” vs. Procedural Block “always” in Verilog

Implementation based on continuous assignment:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output q;
4	assign q = (i1 & ~s) (i2 & s);
5	endmodule

Implementation based on “always @ ” procedural block:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (i1 or i2 or s)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Procedural Block “always” in Verilog

Implementation based on “always @ ”
procedural block:

Update q whenever i1, i2, or s changes →

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (i1 or i2 or s)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Procedural Block “always” in Verilog

Only “regs” can be modified
within an “always” code block→

Implementation based on “always @ ”
procedural block:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (i1 or i2 or s)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Sensitivity List in Procedural Block “always”

Sensitivity list of “always” block →
(contains i1, i2, and s pins):

Execute the body of the code block
whenever one of the inputs in sensitivity
list changes

Implementation based on “always @ ”
procedural block:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (i1 or i2 or s)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Sensitivity List in Procedural Block “always”

Sensitivity list of “always” block: →
i2 is omitted

Implementation based on “always @ ”
procedural block:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (i1 or s)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Sensitivity List in Procedural Block “always”

“wildcard” operator (*) at sensitivity list →
Forces to automatically determine the dependencies of q, and to update q whenever some of those input dependencies changes

Implementation based on “always @ ” procedural block:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Blocking and Non-Blocking Assignments in Verilog

Implementation based on “always @ ”
procedural block:

Assignment statement →

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	end
8	endmodule

Blocking and Non-Blocking Assignments in Verilog

“Blocking” assignment statements:

- First, line 6 is executed;
- After completing line 6, line 7 is executed

Implementation based on “always @ ”
procedural block:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	q1 <= (i1 & ~s) & (i2 & s);
8	end
9	endmodule

Blocking and Non-Blocking Assignments in Verilog

“Non-Blocking” assignment statements:

- Lines 6 and 7 execute concurrently

Implementation based on “always @ ”
procedural block:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	q1 <= (i1 & ~s) & (i2 & s);
8	end
9	endmodule

Blocking and Non-Blocking Assignments in Verilog

Implementation based on “always @ ”
procedural block:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	q1 <= (i1 & ~s) & (i2 & s);
8	end
9	endmodule

Whenever possible, non-blocking assignments are preferred

Blocking and Non-Blocking Assignments in Verilog

Code with blocking assignments:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	q1 = ~q;
8	end
9	endmodule

Code with non-blocking assignments:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	q1 <= ~q;
8	end
9	endmodule

What is the difference ?

Blocking and Non-Blocking Assignments in Verilog

Code with blocking assignments:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q = (i1 & ~s) (i2 & s);
7	q1 = ~q;
8	end
9	endmodule

Code with non-blocking assignments:

1	module mux (i1, i2, s, q, q1);
2	input i1, i2, s;
3	output reg q, q1;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	q1 <= ~q;
8	end
9	endmodule

Because of non-blocking assignments used, either line 6 or line 7 can be completed first;
Thus, the resulted value for q1 is non-deterministic

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	end
8	endmodule

If-Else Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	end
8	endmodule

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) begin
7	q <= i1;
8	end
9	else if (s == 1) begin
10	q <= i2;
11	end
12	end
13	endmodule

If-Else Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	q <= (i1 & ~s) (i2 & s);
7	end
8	endmodule

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) begin
7	q <= i1;
8	end
9	else if (s == 1) begin
10	q <= i2;
11	end
12	end
13	endmodule

If-Else Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) begin
7	q <= i1;
8	end
9	else if (s == 1) begin
10	q <= i2;
11	end
12	end
13	endmodule

If-Else Statement

More compact code:

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) q <= i1;
9	else q <= i2;
12	end
13	endmodule

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) begin
7	q <= i1;
8	end
9	else if (s == 1) begin
10	q <= i2;
11	end
12	end
13	endmodule

If-Else Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) q <= i1;
9	else q <= i2;
12	end
13	endmodule

If-Else Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) q <= i1;
9	else q <= i2;
12	end
13	endmodule

Case Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	case (s)
7	0: q <= i1;
8	1: q <= i2;
9	endcase
10	end
11	endmodule

If-Else Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	if (s == 0) q <= i1;
9	else q <= i2;
12	end
13	endmodule

Case Statement

1	module mux (i1, i2, s, q);
2	input i1, i2, s;
3	output reg q;
4	always @ (*)
5	begin
6	case (s)
7	0: q <= i1;
8	1: q <= i2;
9	endcase
10	end
11	endmodule