

Computer Architecture

Lecture + Tutorial 05

Extension of Latches to Flip-Flops
Asynchronous and Synchronous Logic Circuits
Sequential Logic Circuits



Artem Burmyakov, Alexander Tormasov

September 23, 2021




The Recap of a Transparent S/R Latch

  
(Transparent = the change of inputs triggers **immediately** the update of the output)



The Recap of a Transparent S/R Latch


 


 An idealistic case (no propagation overhead considered):





The Recap of a Transparent S/R Latch

  Values for inputs S and R are produced at these times
(somewhere in neighbouring subcircuits)




The Recap of a Transparent S/R Latch

 


 

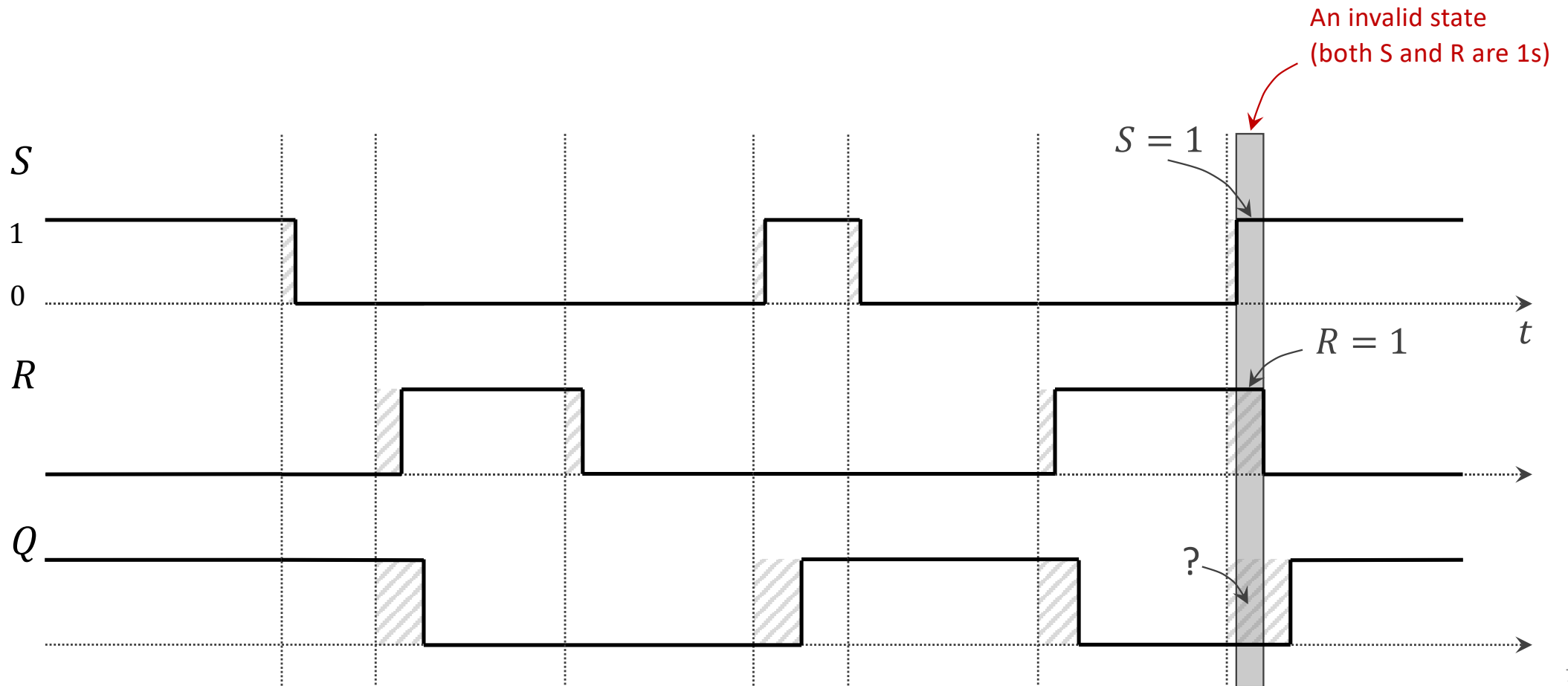Various problems might be caused by unpredicted propagation delays, such as an invalid state for a transparent S/R latch





 Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




Transformation of an Asynchronous Latch into a Synchronous Flip-Flop

  Step 1:
The inclusion
of a clock
generator



Clock Generator (Oscillator)

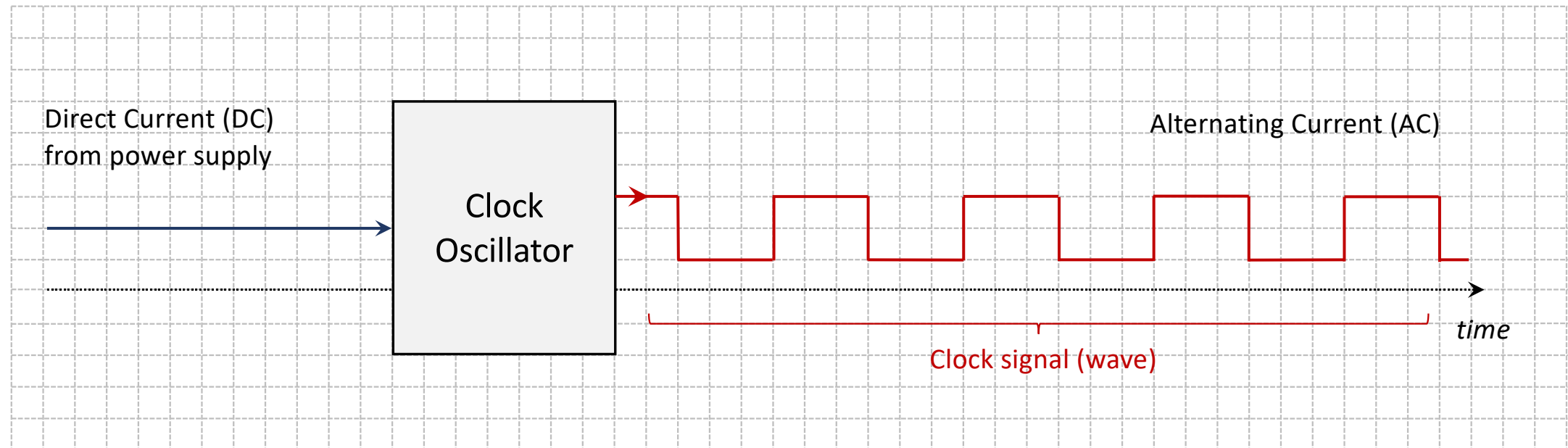An electronic device, producing a periodic clock signal




Clock oscillator – a physical device, that converts direct current (DC) from a power supply into an alternating periodic signal

Oscillation – a repetitive variation, typically in time, of some measure between two or several values

Clock Generator (Oscillator)

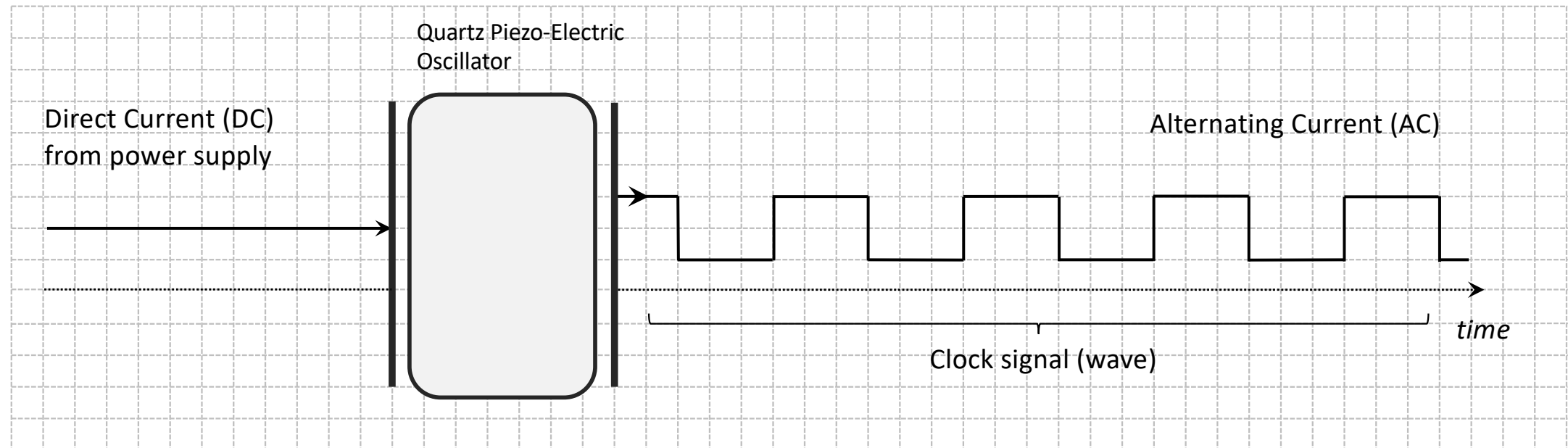
An electronic device, producing a periodic clock signal




Clock oscillator – a physical device, that converts direct current (DC) from a power supply into an alternating periodic signal

Oscillation – a repetitive variation, typically in time, of some measure between two or several values

Clock Signal Terminology

 

 
Edge-Triggered and Level-Triggered Timing Methodologies



Edge-Triggered and Level-Triggered Timing Methodologies

Edge-Triggered Circuit:

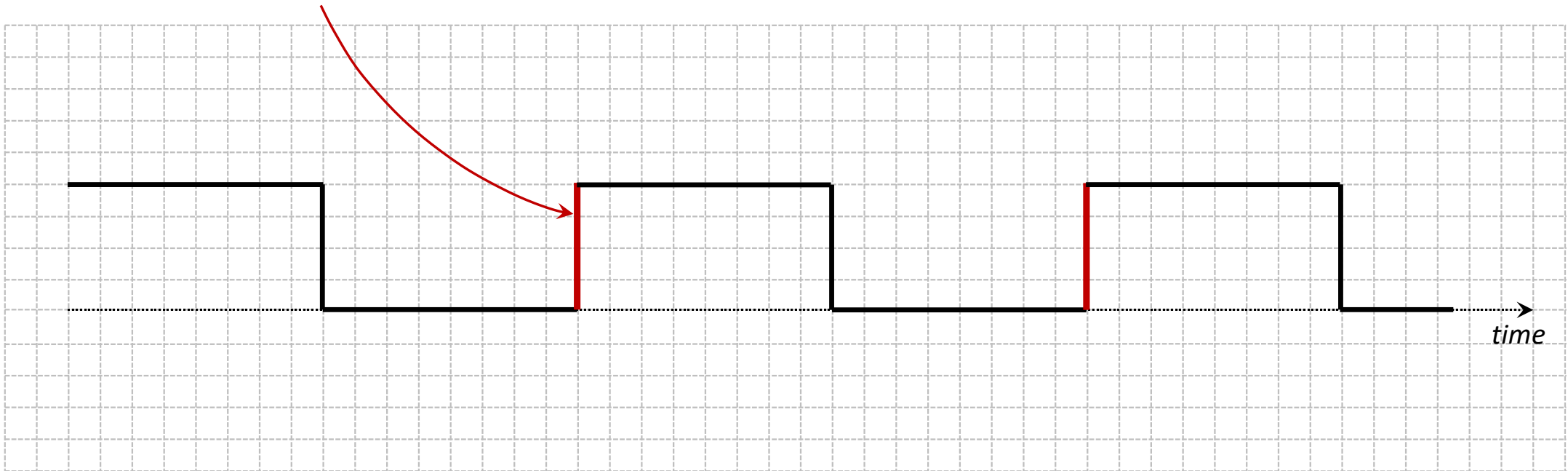
a circuit is activated either on a raising or a falling edge




Edge-Triggered and Level-Triggered Timing Methodologies

Edge-Triggered Circuit:

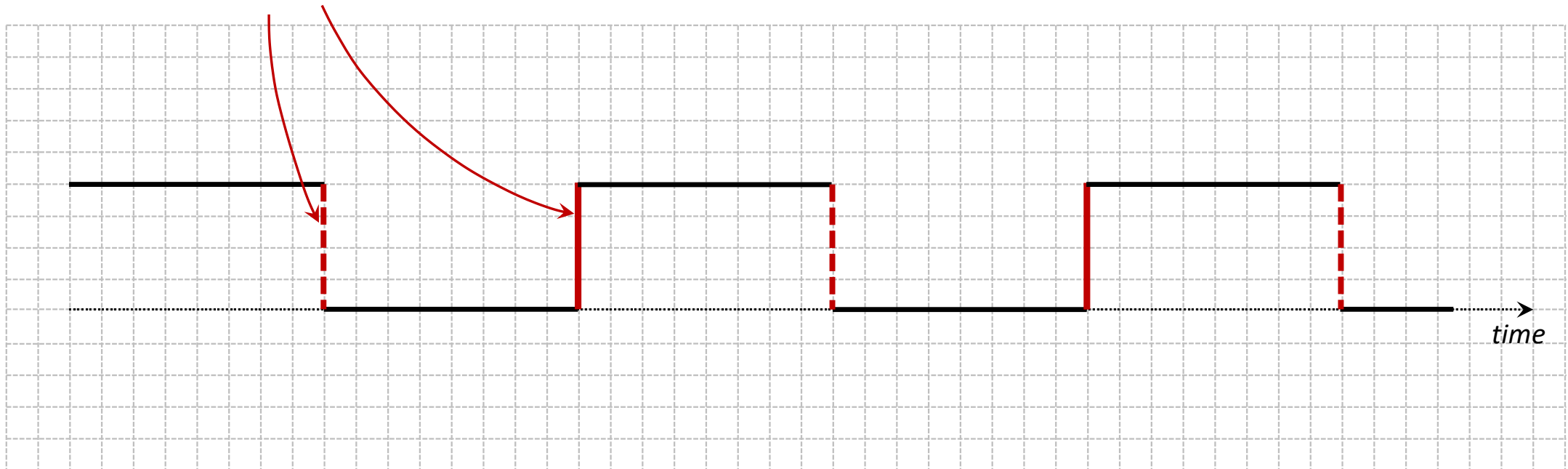a circuit is activated either on a raising or a falling edge



 Edge-Triggered and Level-Triggered Timing Methodologies




Level-Triggered Circuit:

a circuit is activated either when clock signal is asserted, or deasserted

Edge-Triggered and Level-Triggered Timing Methodologies

Edge-Triggered:

 a circuit is activated either on a raising or a falling edge




Level-Triggered:

a circuit is activated either when clock signal is asserted, or deasserted

Characteristics of a Rectangular Clock Signal

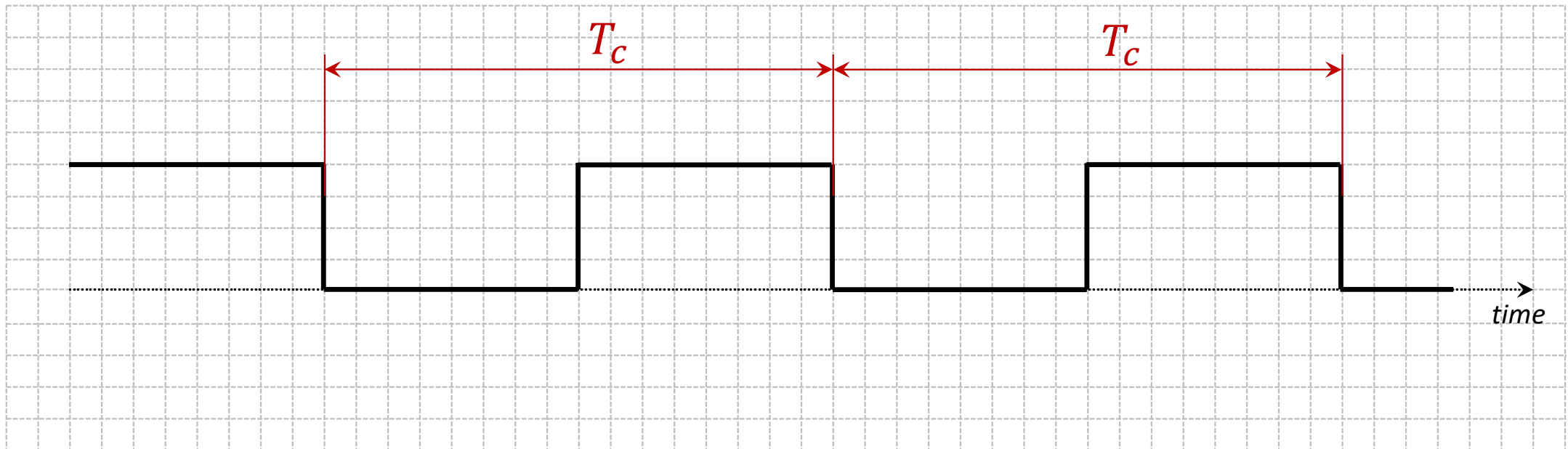
T_c - clock cycle time, or period, or cycle length



Characteristics of a Rectangular Clock Signal

T_c - clock cycle time, or period, or cycle length

$F_c = 1/T_c$ - clock frequency

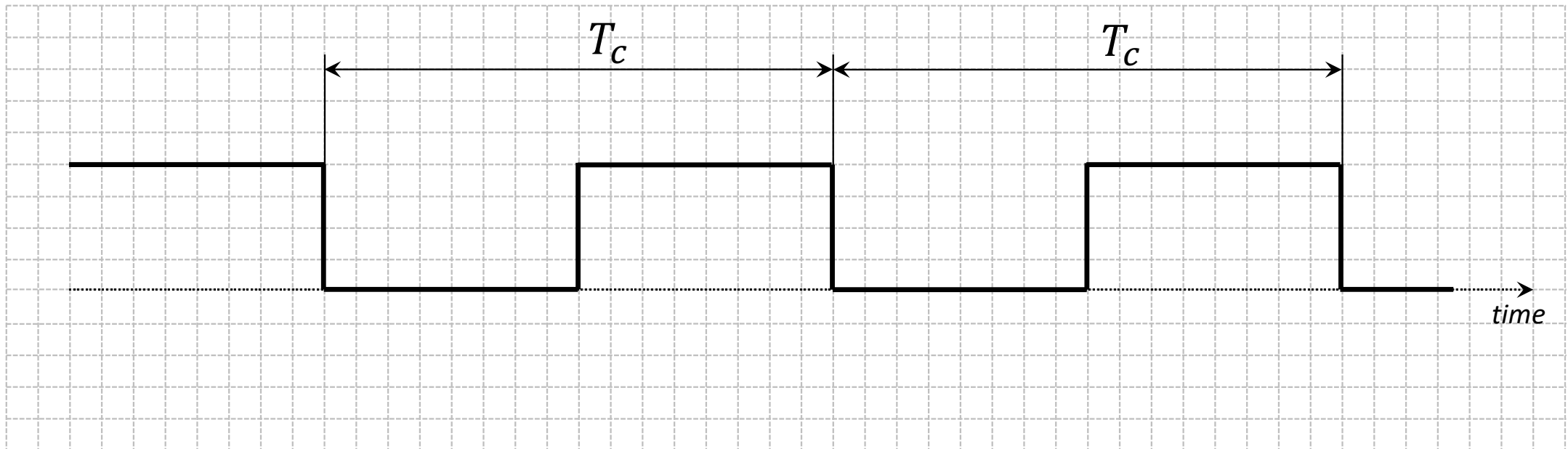


Clock frequency sets the tempo for the processor to execute instructions

Characteristics of a Rectangular Clock Signal

T_c - clock cycle time, or period, or cycle length

$F_c = 1/T_c$ - clock frequency

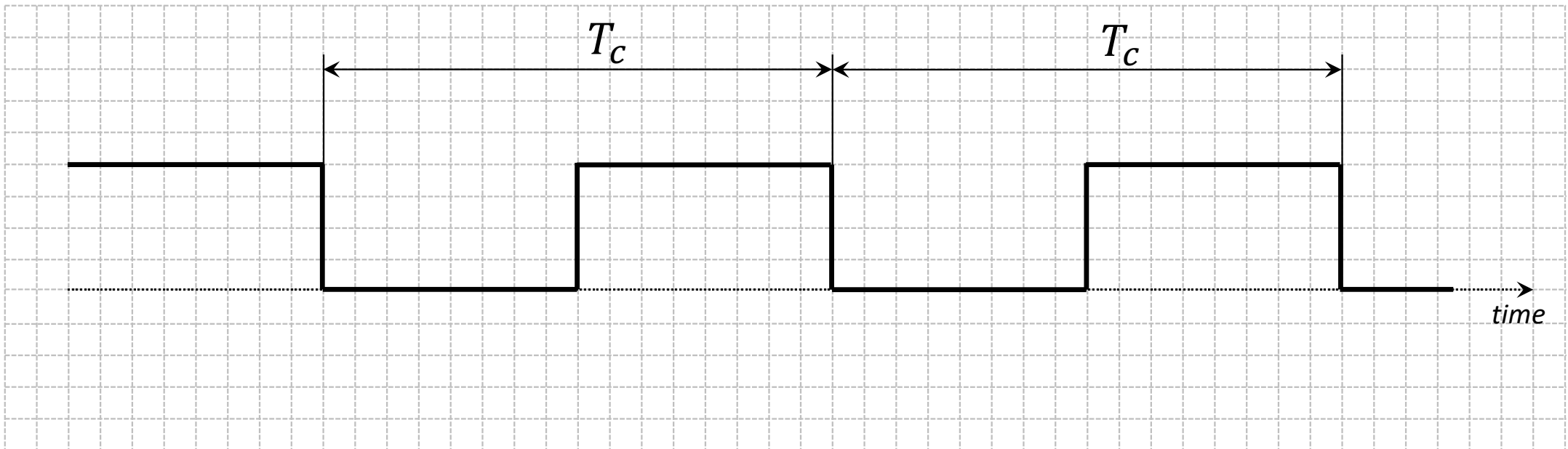

Clock frequency sets the tempo for the processor to execute instructions



Common characteristics for modern general-purpose CPUs:

T_c - a few nanoseconds, $\sim 10^{-9}$ sec



F_c - a few gigahertz, 2-3 GHz

Clock Signal Variations

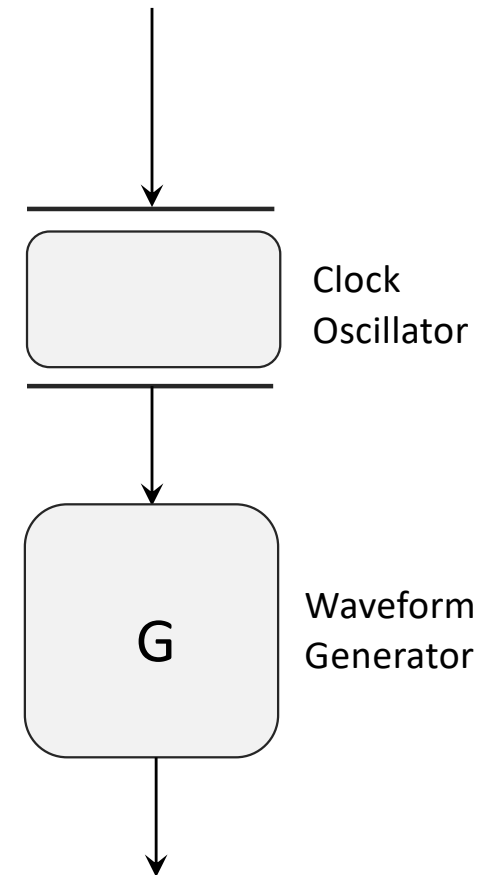 
(A waveform generator is used to control the form of a clock wave signal)



  
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



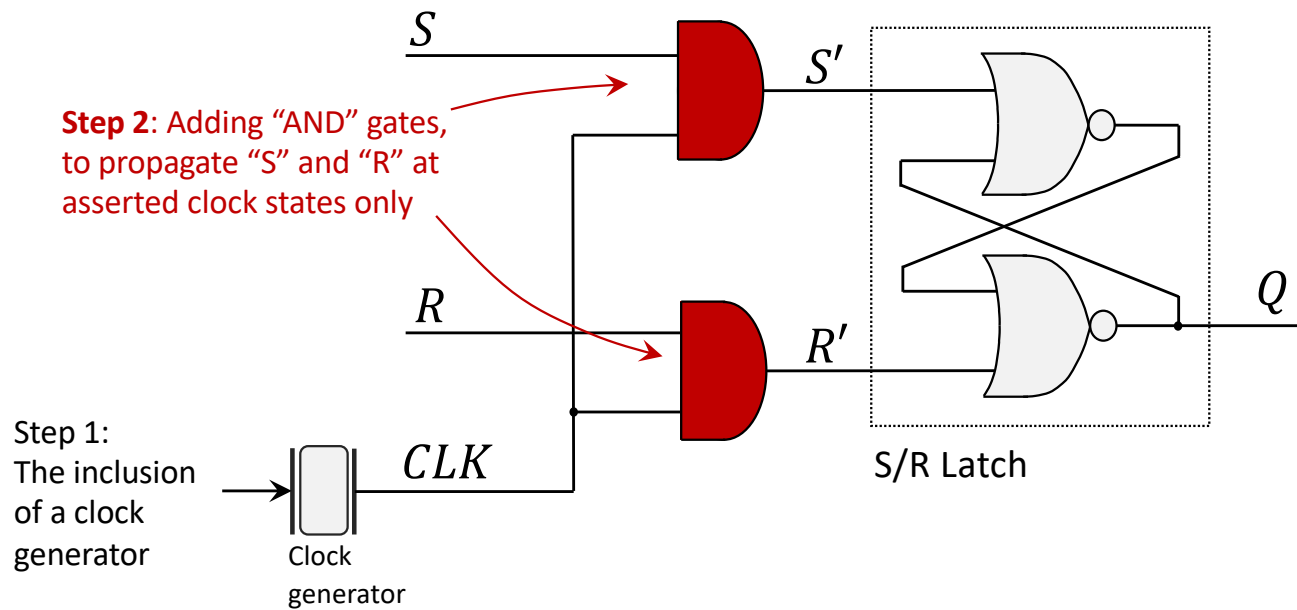
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




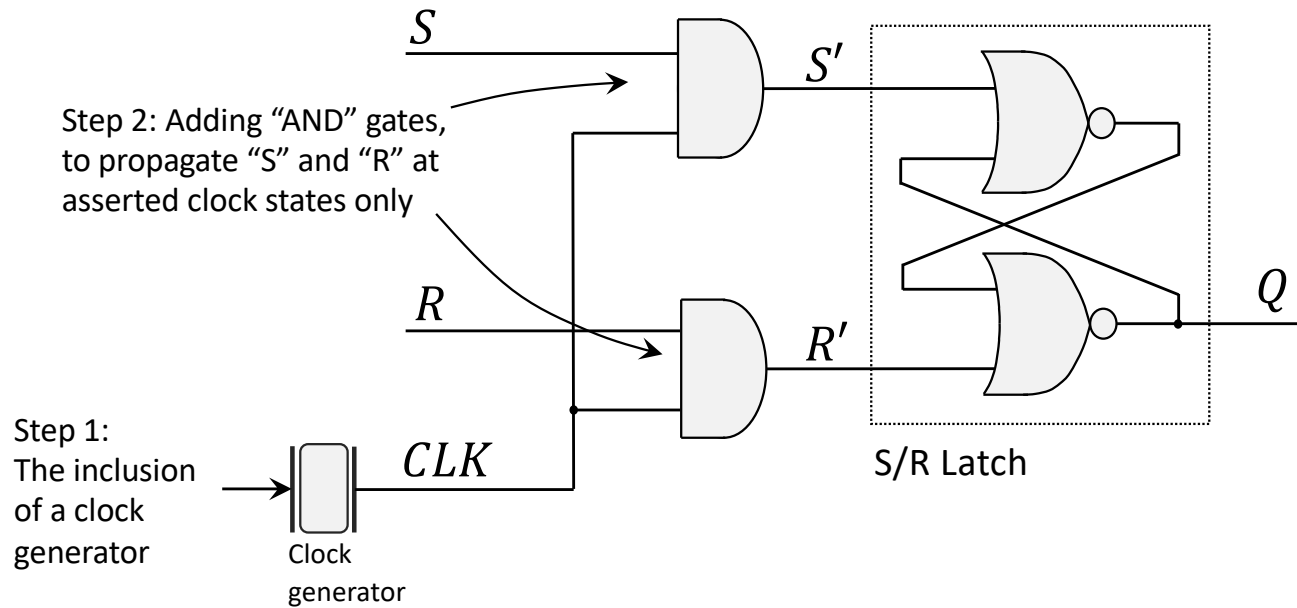
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



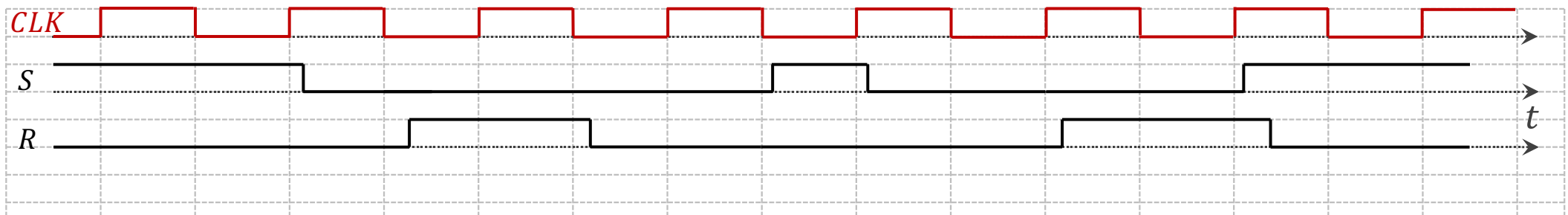
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



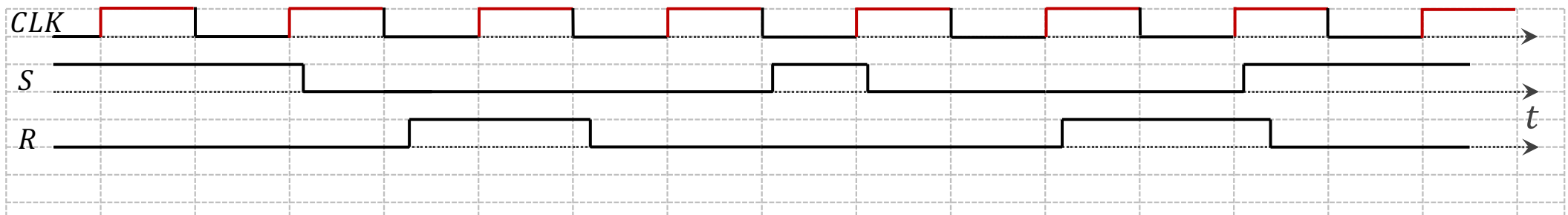
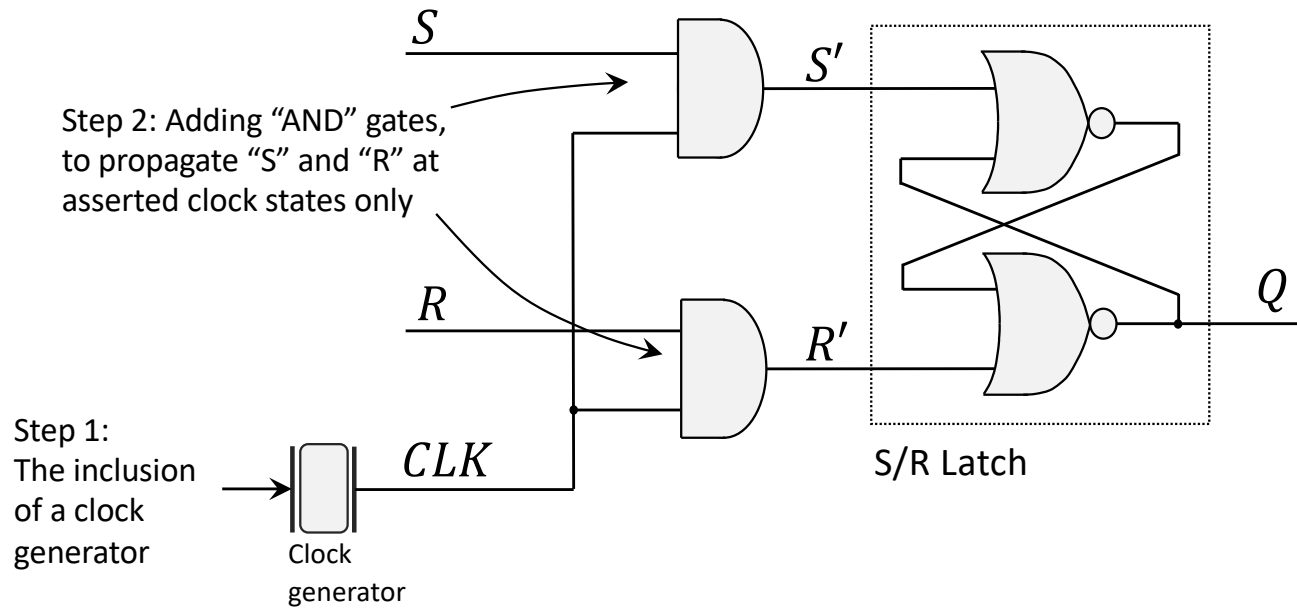
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



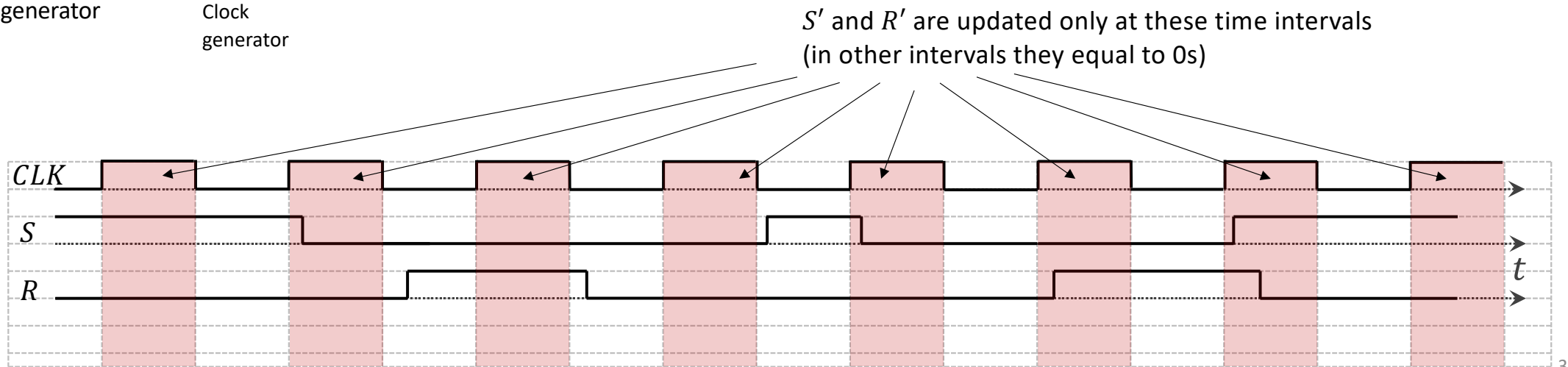
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



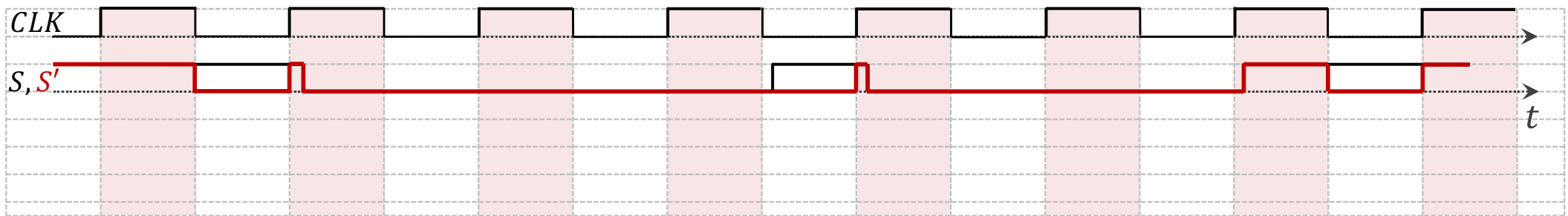 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



  Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




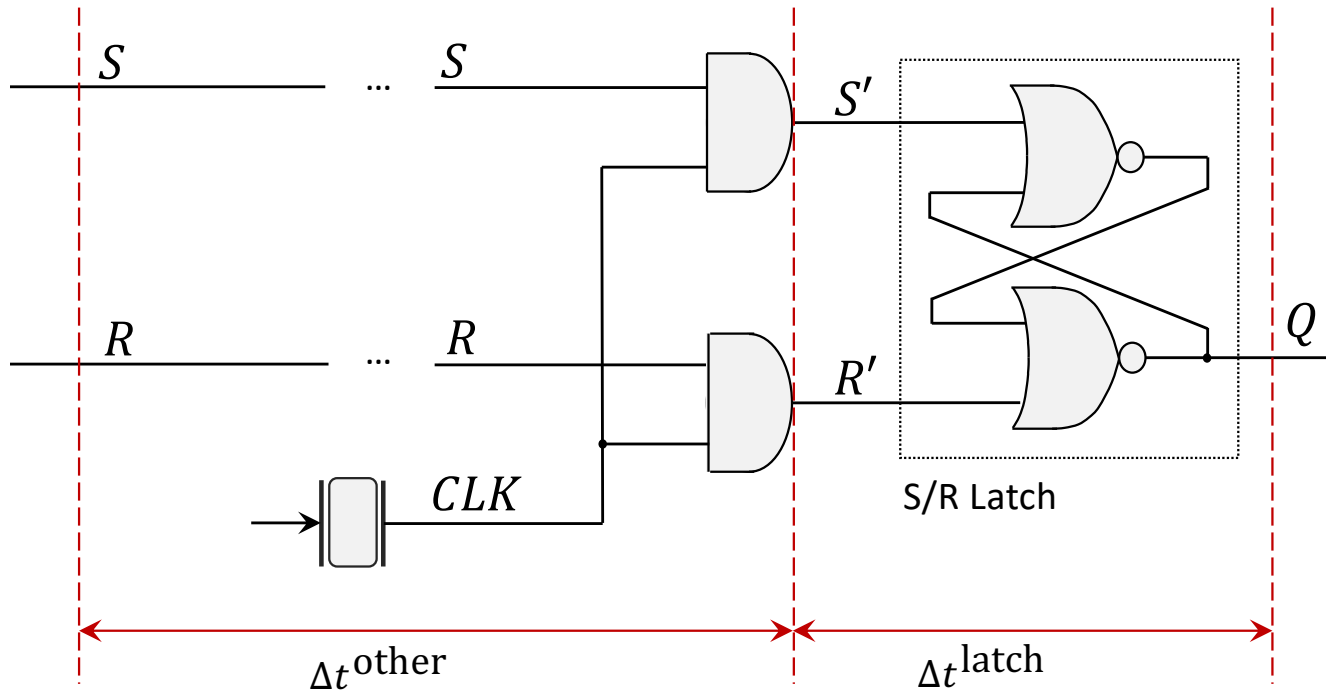Transformation of an Asynchronous Latch into a Synchronous Flip-Flop





Assumption:

 
Latch propagation delay Δt^{latch} is insignificant, as compared to Δt^{other}



  
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



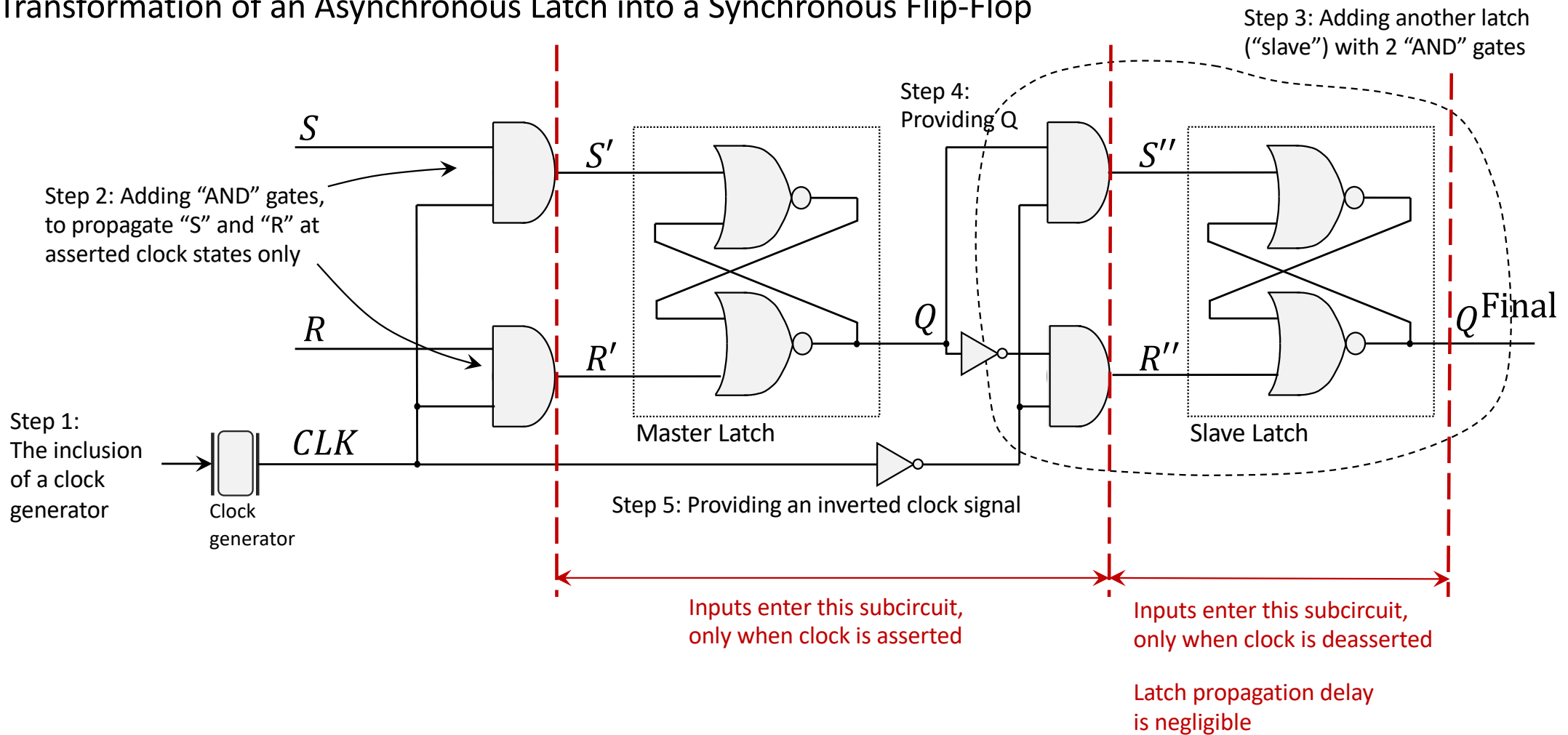
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




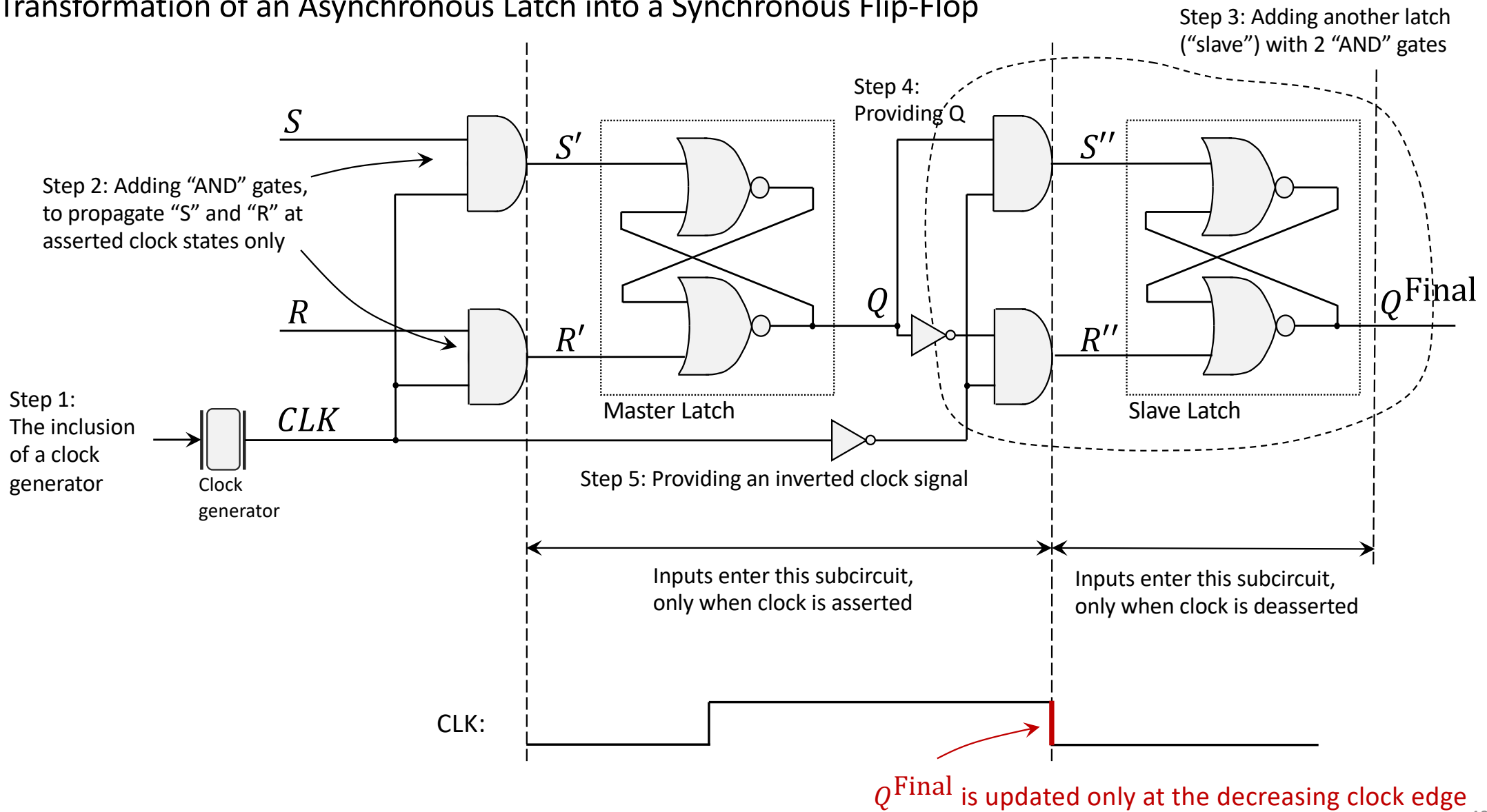
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



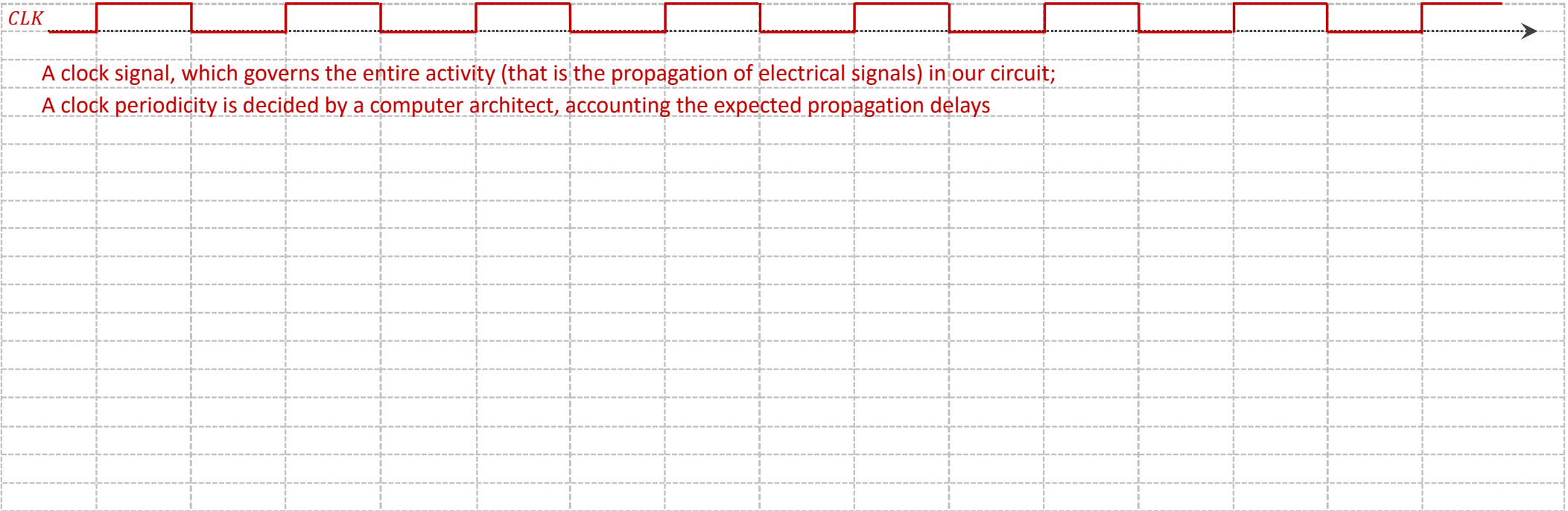
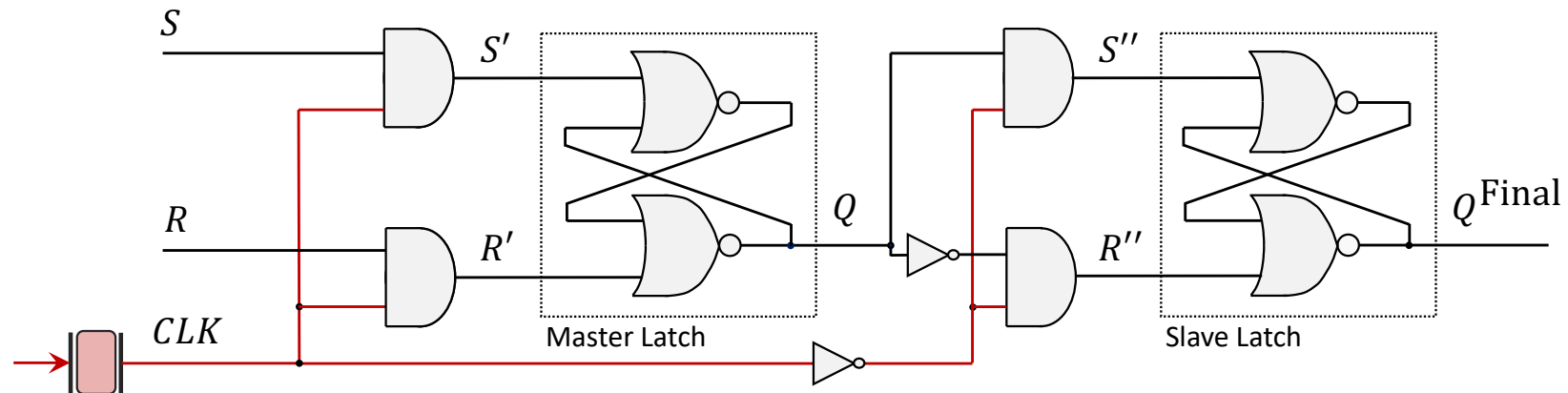
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



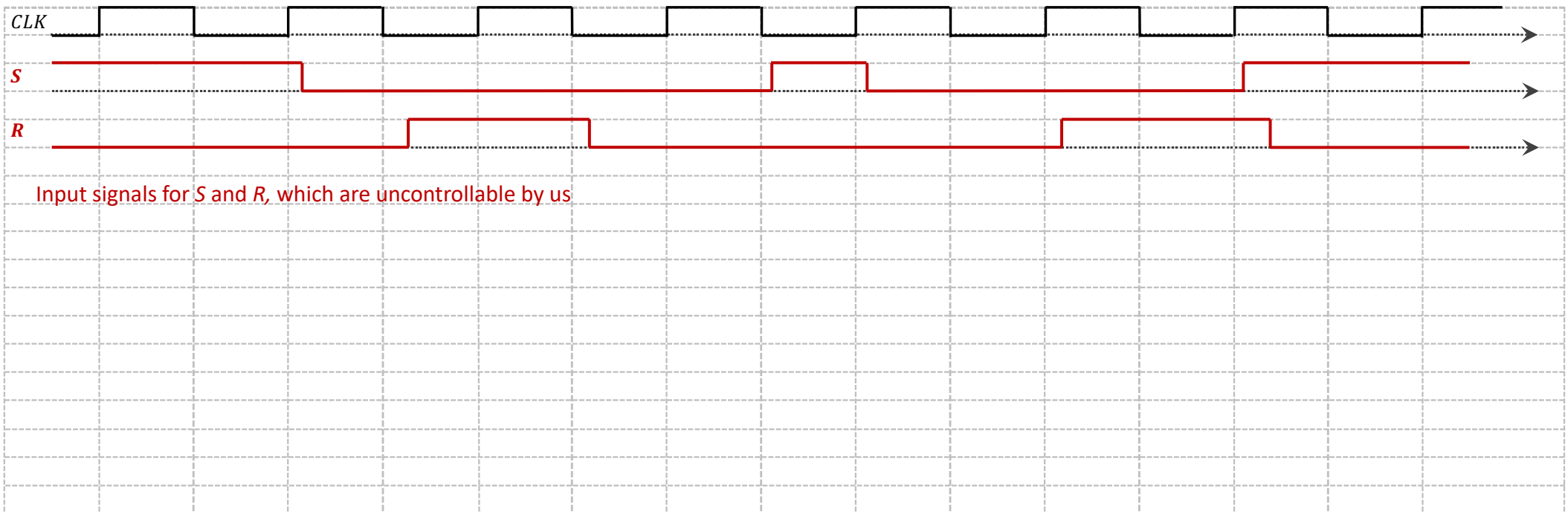
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



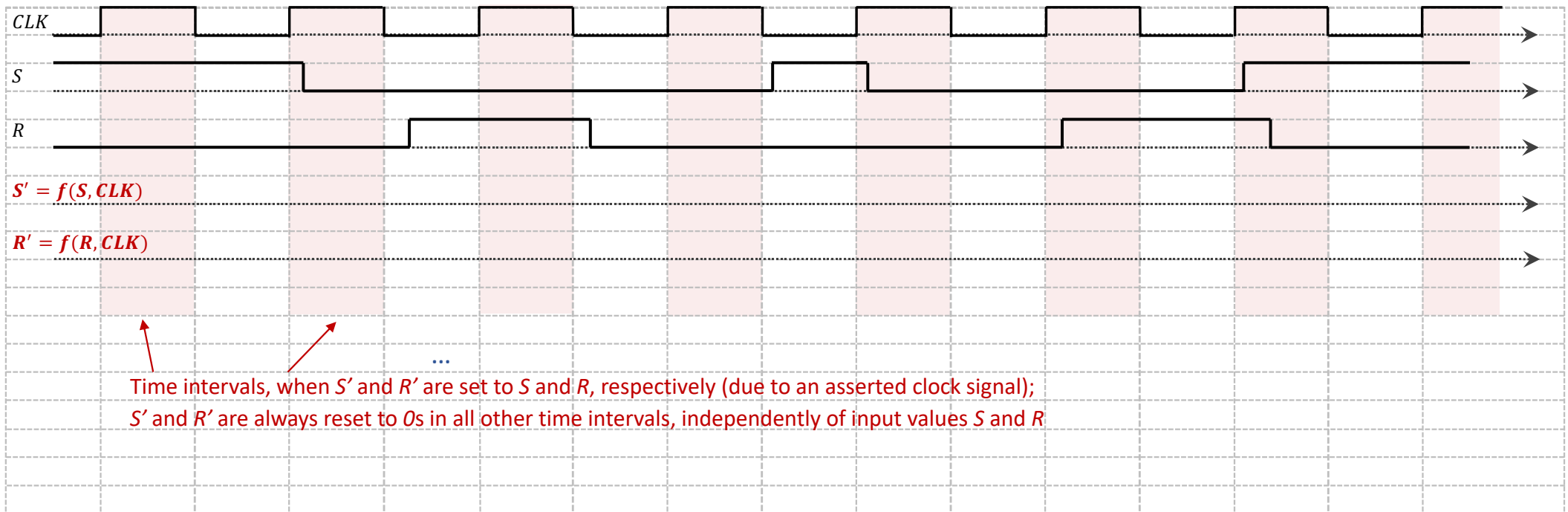
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



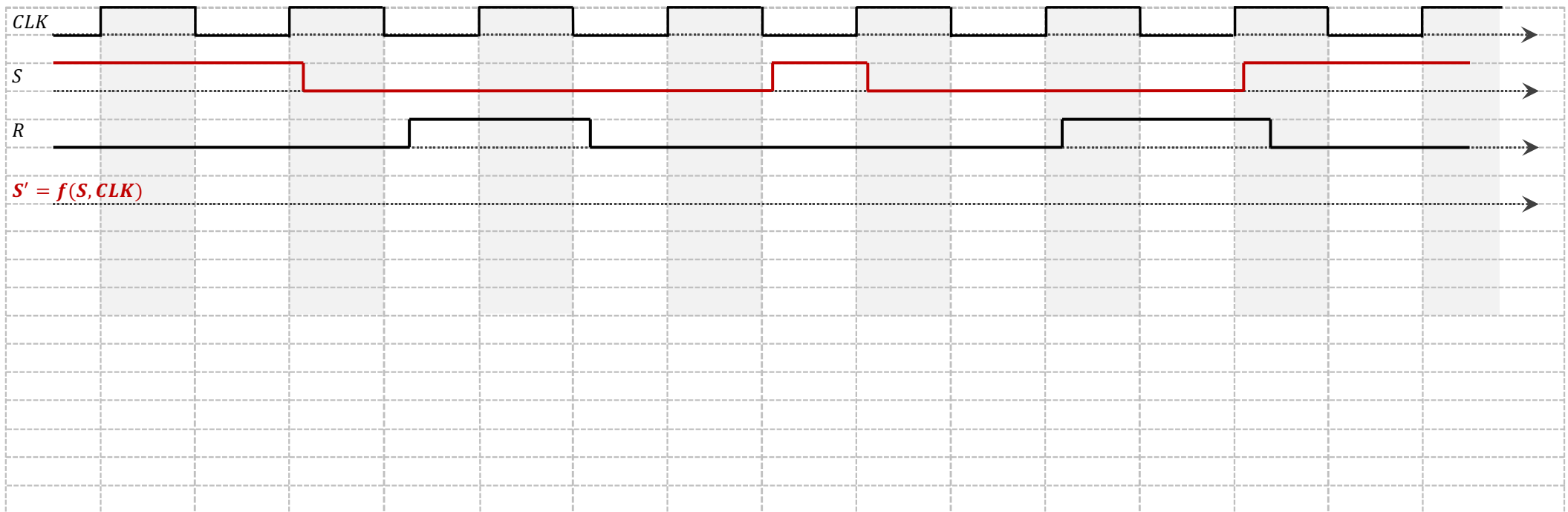
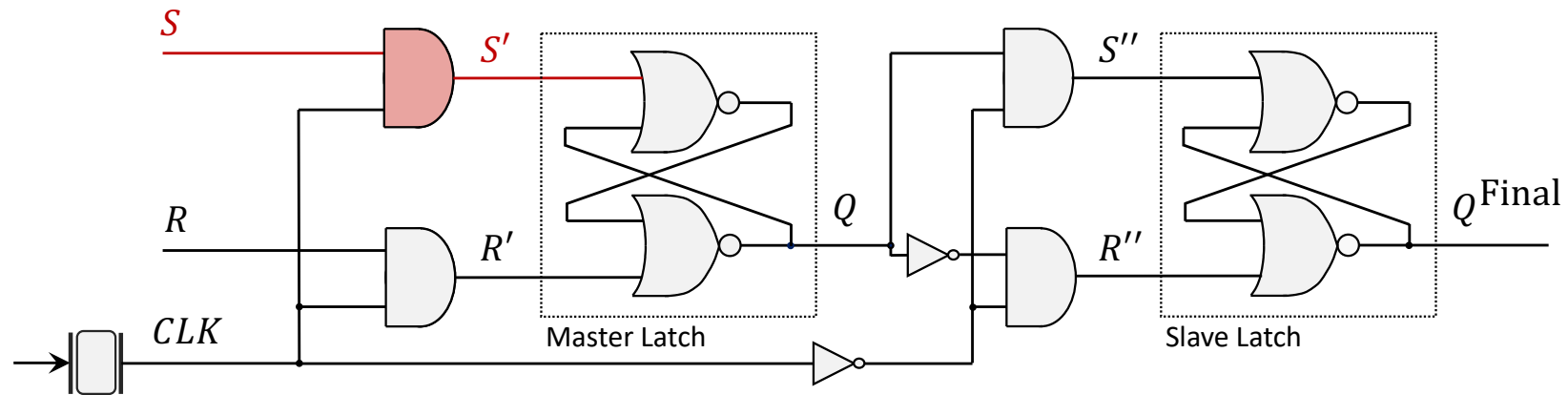
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



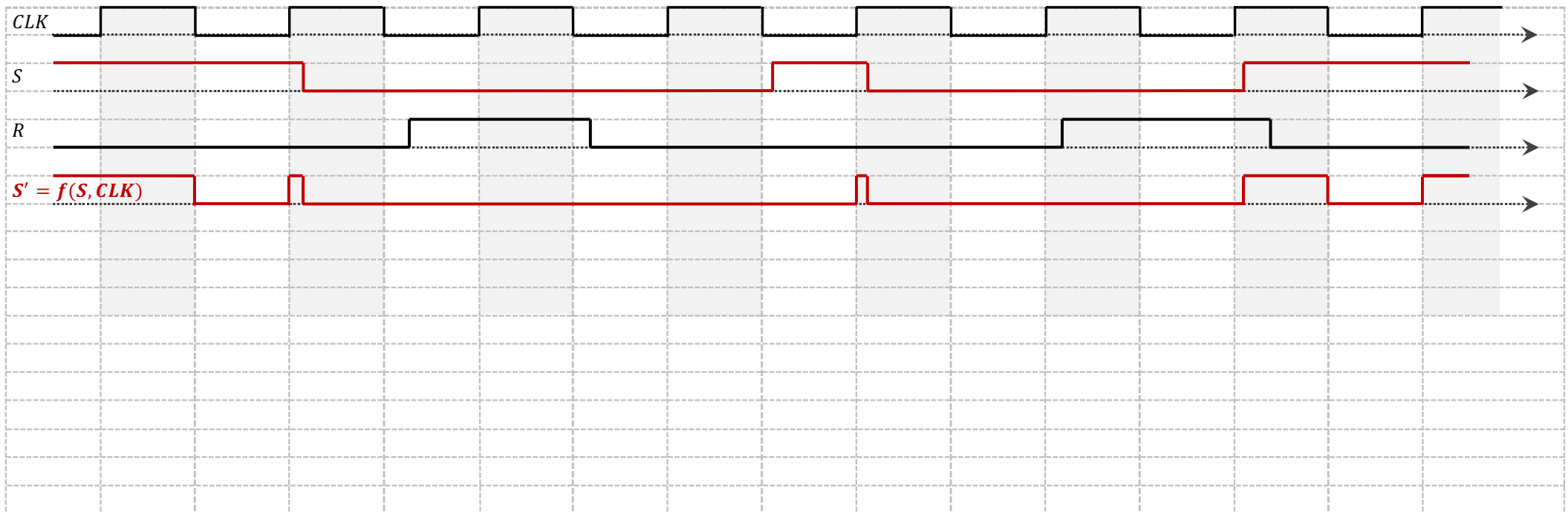
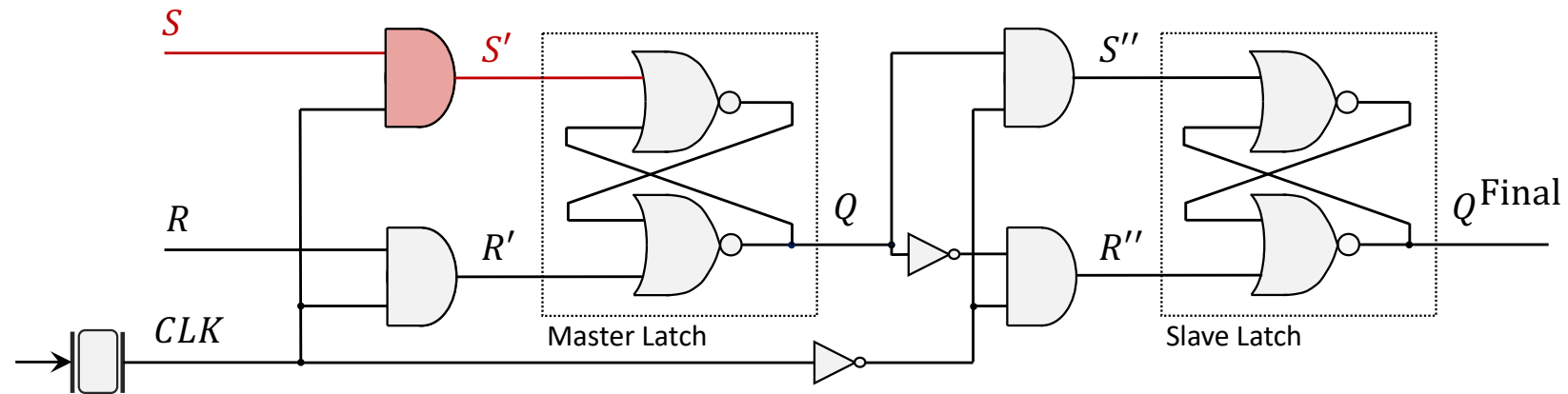
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



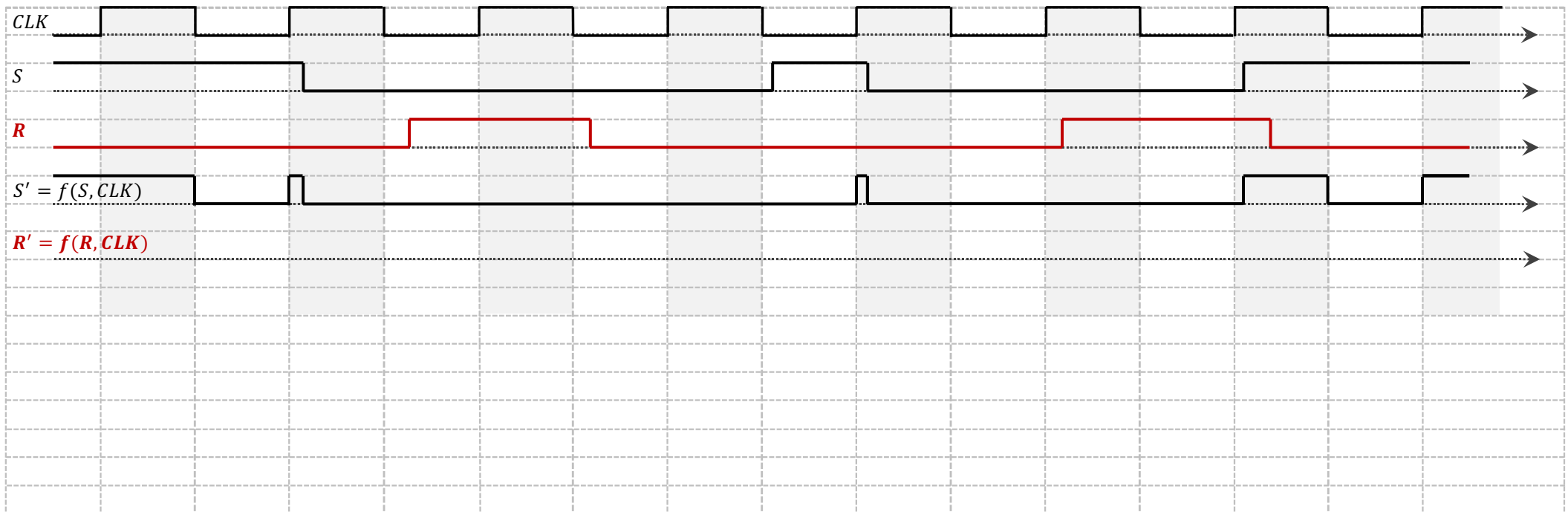
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



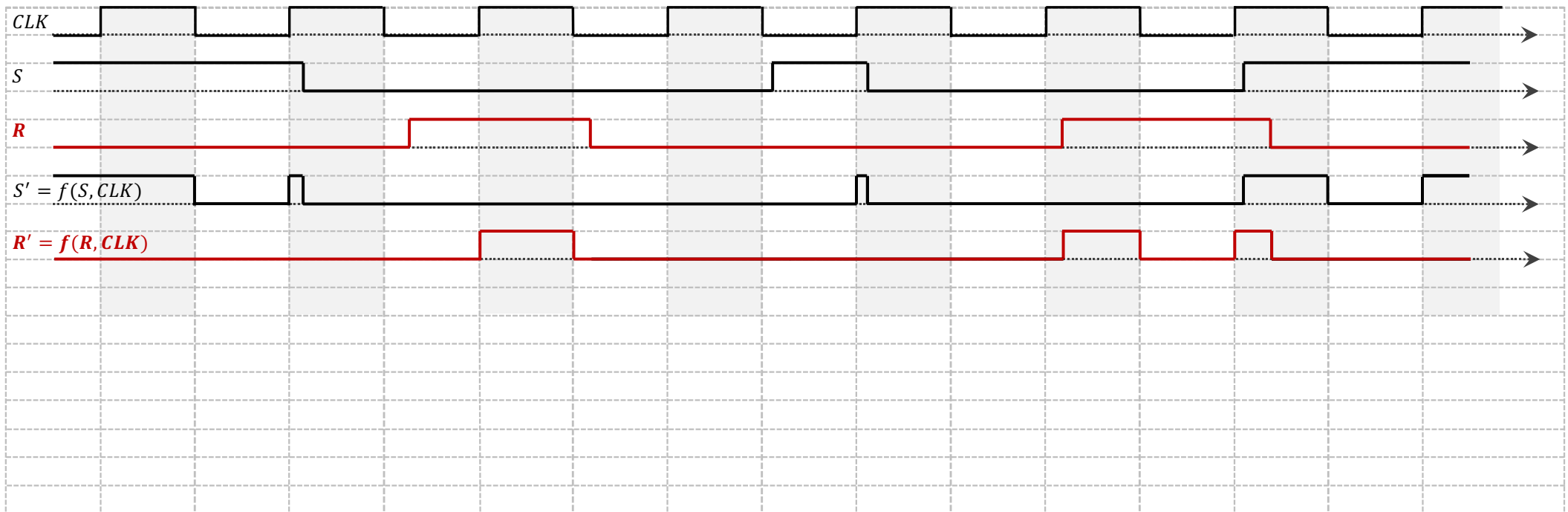 Transformation of an Asynchronous Latch into a Synchronous Flip-Flop





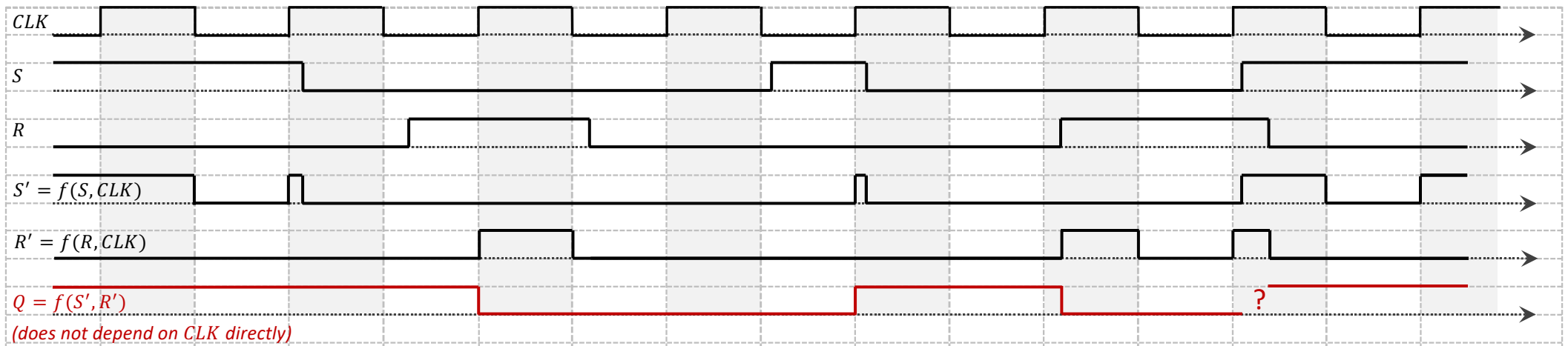 Transformation of an Asynchronous Latch into a Synchronous Flip-Flop





Recap: Whenever R' and S' go to 0s, Q retains its value unchanged (the property of a latch)

 
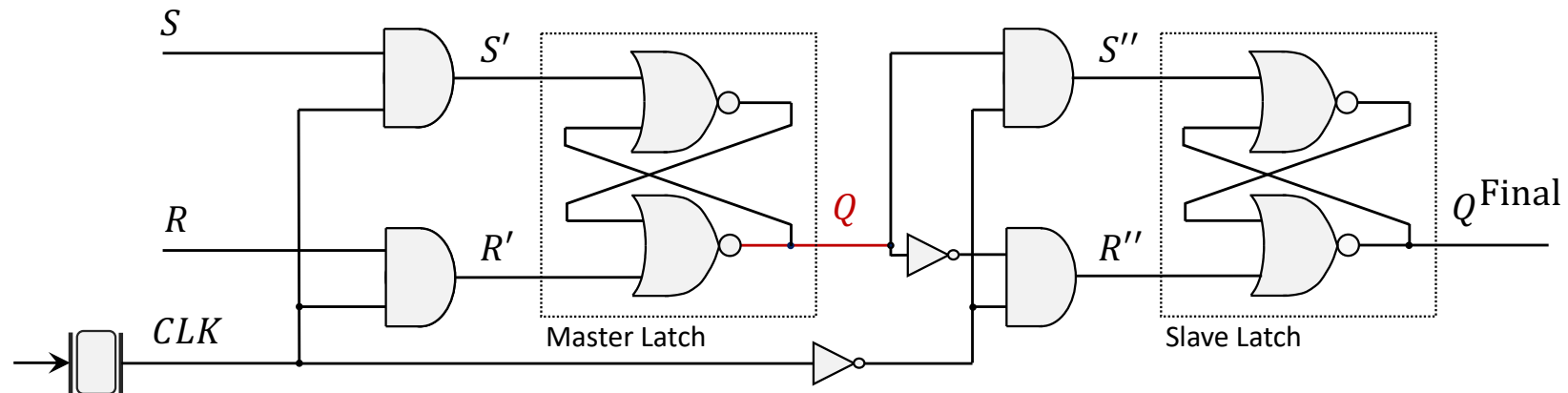
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



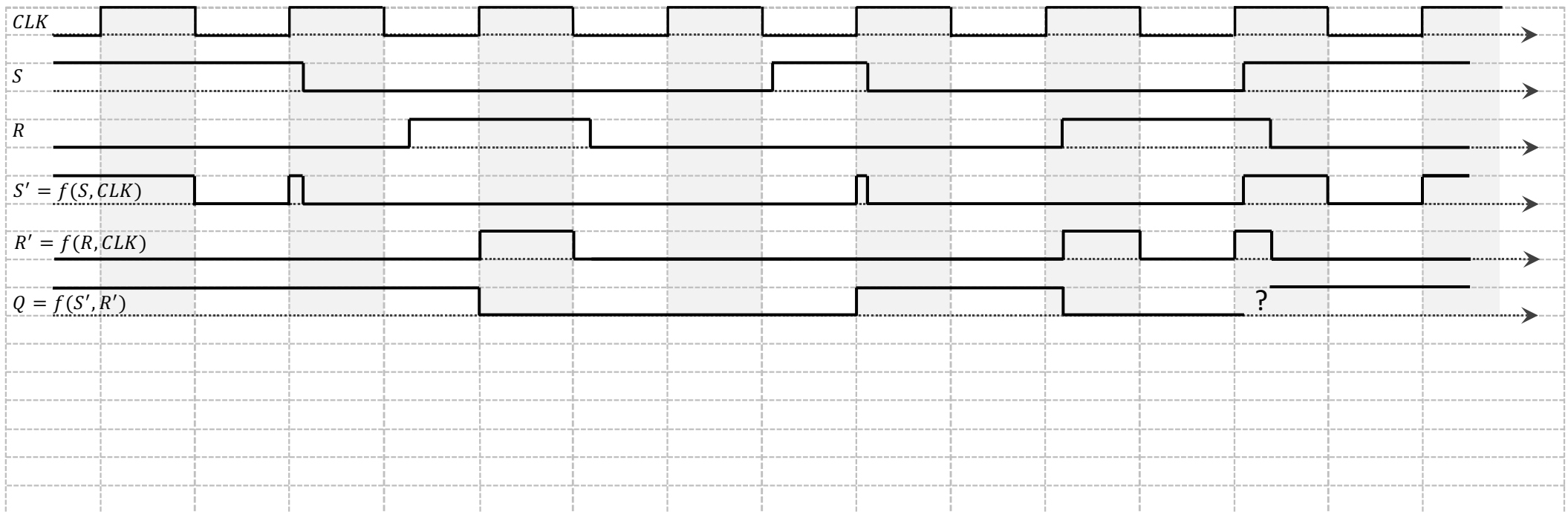
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



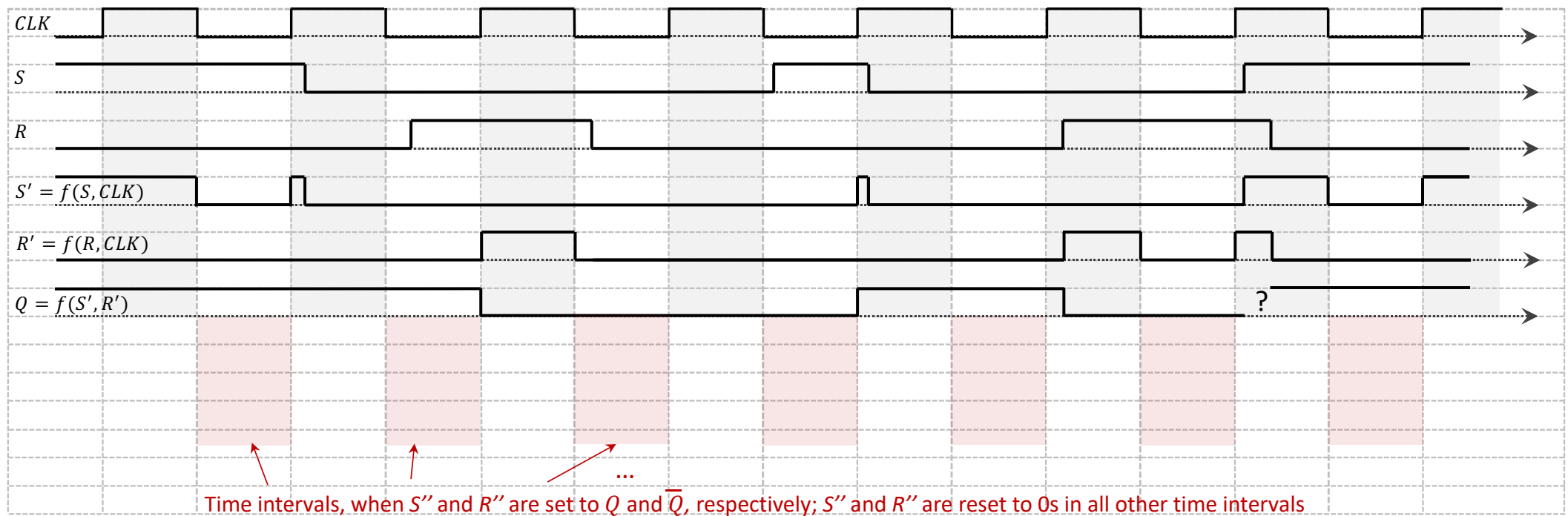
 
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



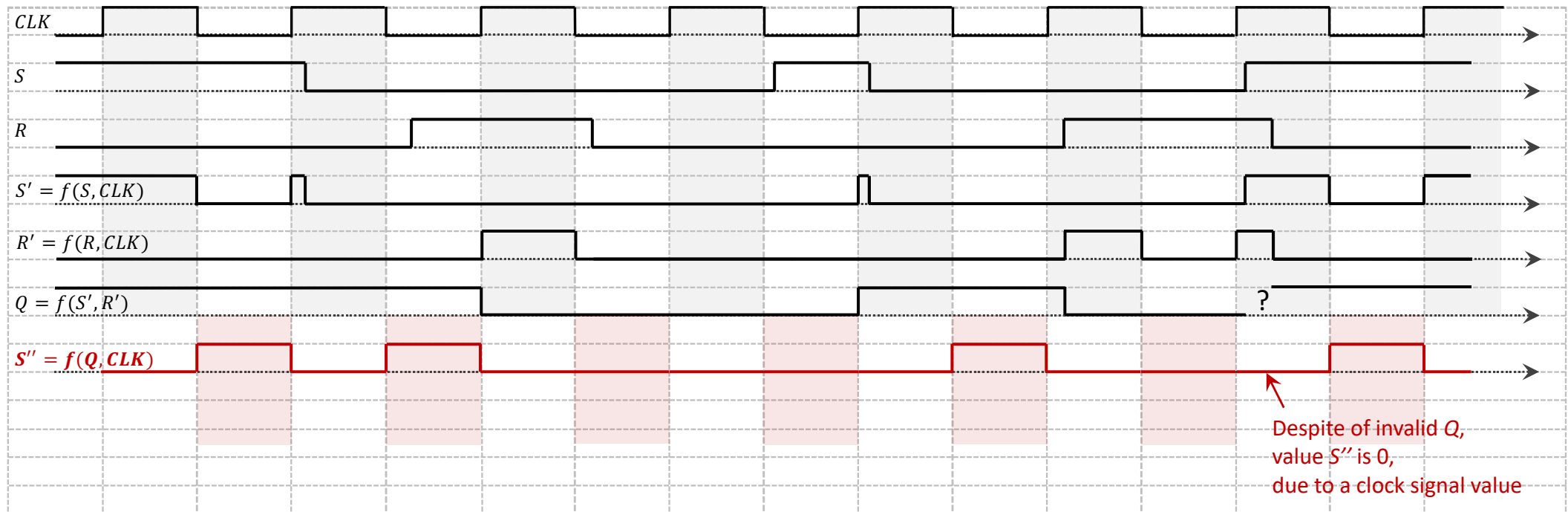
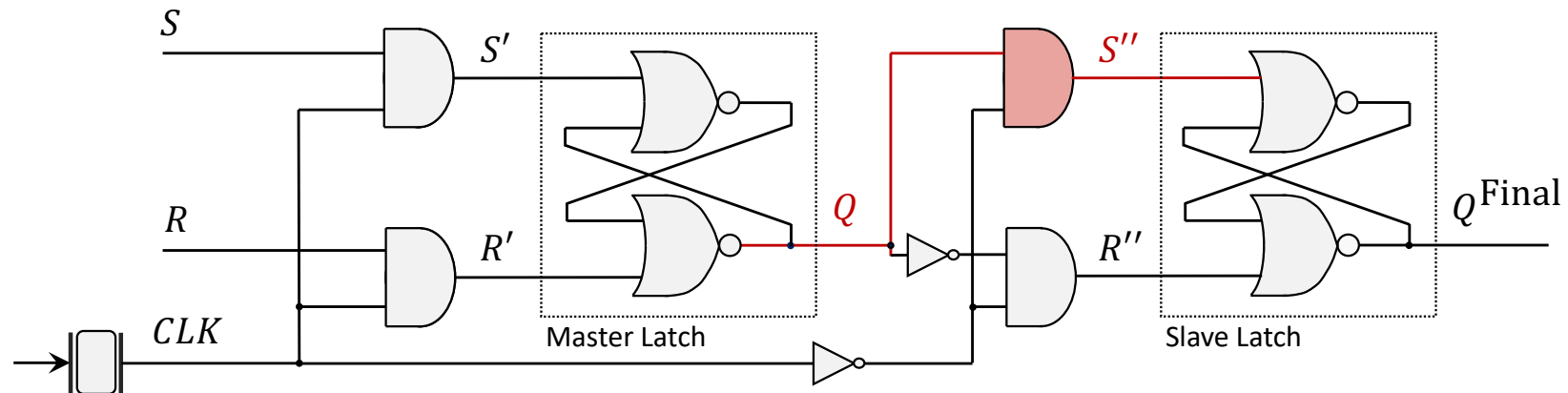
Transformation of an Asynchronous Latch into a Synchronous Flip-Flop




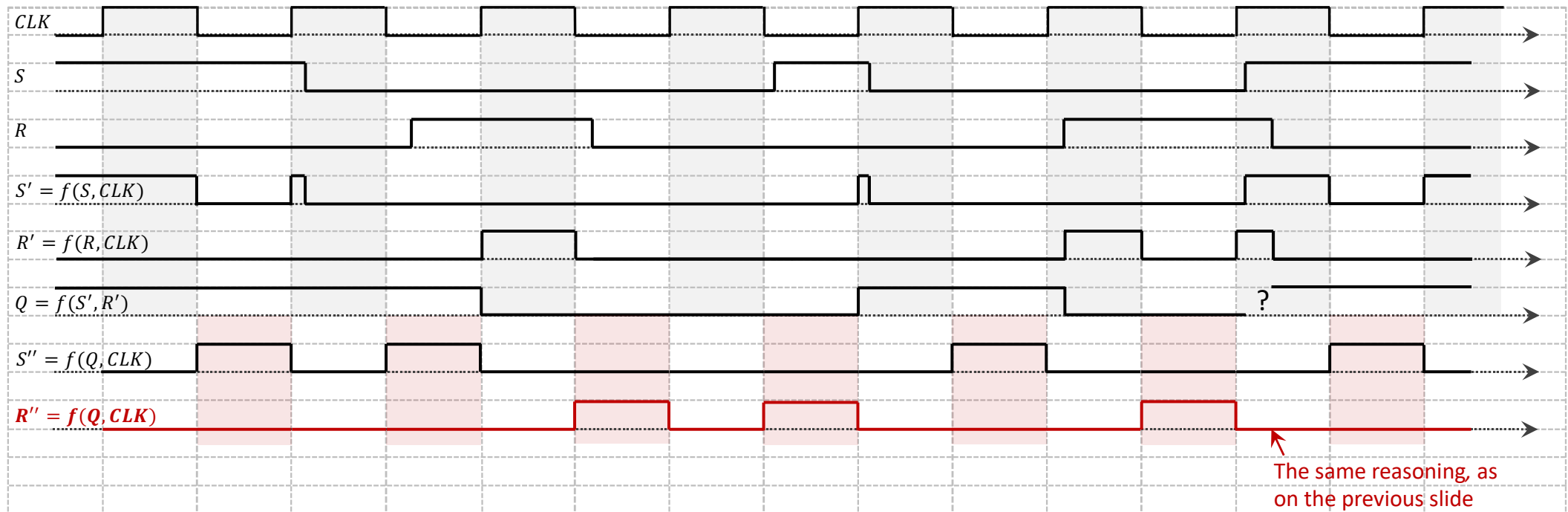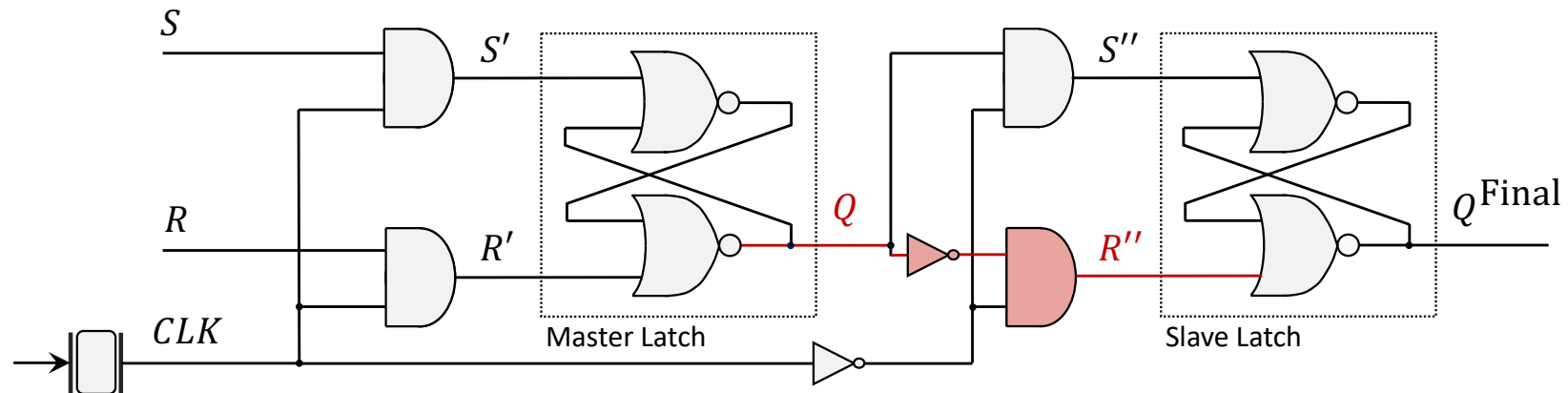Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



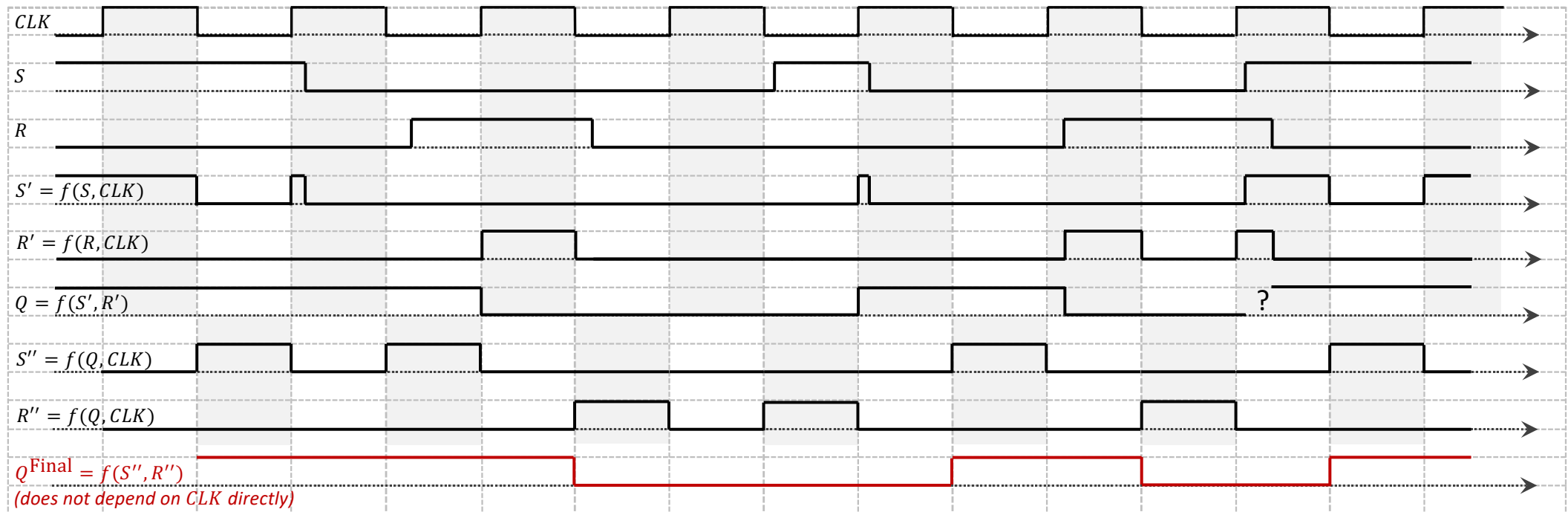 Transformation of an Asynchronous Latch into a Synchronous Flip-Flop



 

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger		
Clock Presence		
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	
Clock Presence		
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence		
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence		Clock governs the entire circuit activity
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)		Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence		Used
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	Higher (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	Higher (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	Simpler , smaller (<i>Note: an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity</i>)	
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	Higher (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	Simpler , smaller (<i>Note: an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity</i>)	More complex , larger
Sample Use Cases		

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	Higher (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	Simpler , smaller (<i>Note: an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity</i>)	More complex , larger
Sample Use Cases		Register files; Most of the circuits containing memory elements

Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	Faster (no clock signal for synchronisation delay is used)	Slower (due to overpessimistic synchronisation delays)
Power Consumption	Lower	Higher (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	Simpler , smaller (<i>Note: an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity</i>)	More complex , larger
Sample Use Cases	Arithmetic-Logic Unit (ALU); Small fast peripheral circuits supporting CPU operation	Register files; Most of the circuits containing memory elements

Digital Circuits Classification

