

Computer Architecture
Computer Engineering Track
Tutorial 13

The Comparison of Memory Types: SRAM and DRAM

Artem Burmyakov, Alexander Tormasov


November 18, 2021



Recap of Hardware Building Blocks


Multiplexor

 Sets a specific output to one of its inputs, based on selector signals




Demultiplexor

 Forwards input signal to one of its multiple outputs, based on the selector signals (other outputs remain "0")




Decoder

 Sets to "1" exactly one output pin, which corresponds to the signals of input pins; All other pins are set to "0"




Encoder

 
The opposite function of a decoder; Only one input pin can be set to "1", while all others – "0"



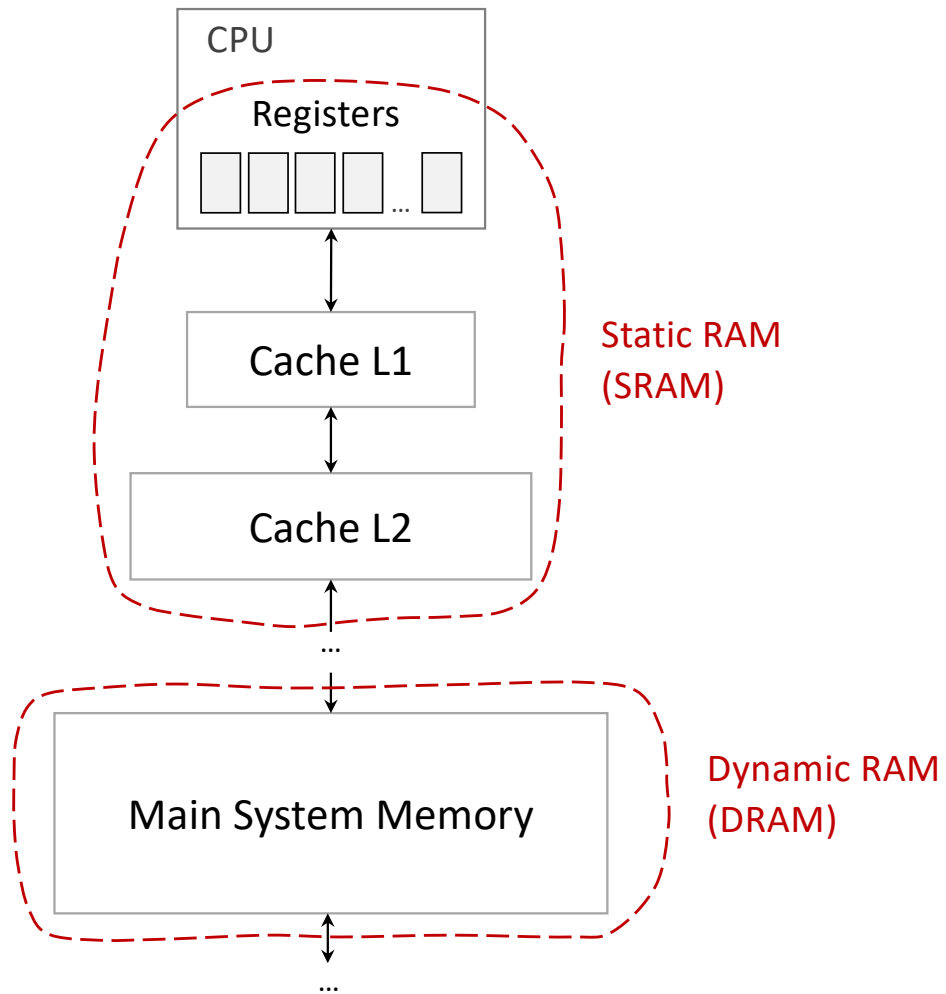Memory Hierarchy – the Fundamental Idea of Computer Architecture




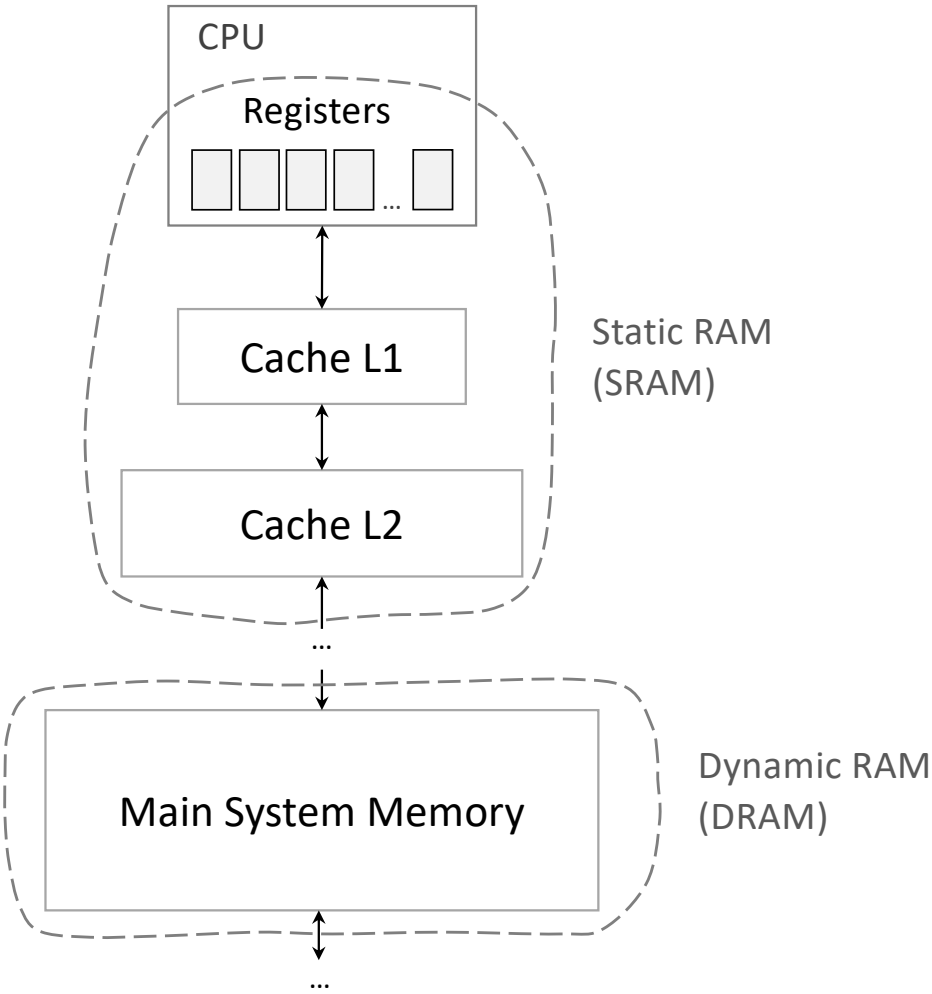The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop (Latch)	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability	More reliable	Less reliable
Volatility	Both are volatile (require electrical power to keep data)	
Memory Cell Access	Each cell is accessed directly, unlike Sequential Access Memory (SAM)	

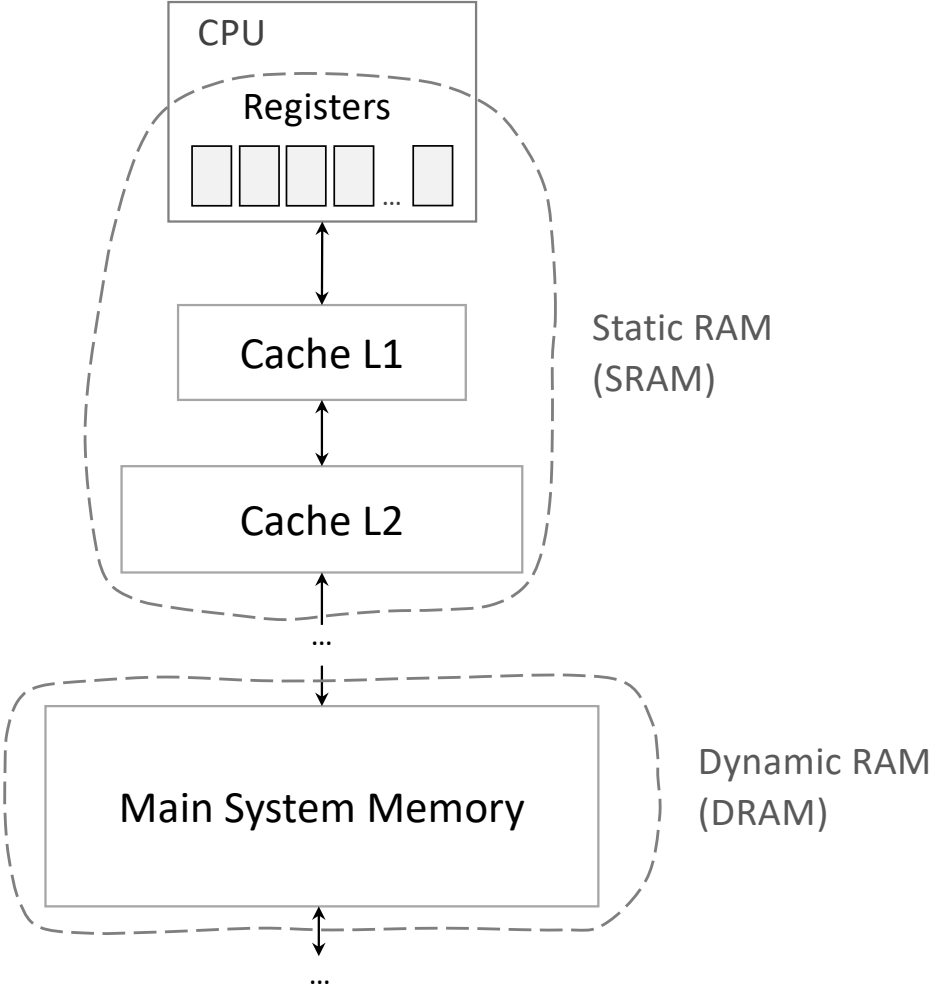The Comparison of DRAM and SRAM Memory Types



Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop (Latch)	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability	More reliable	Less reliable
Volatility	Both are volatile (require electrical power to keep data)	
Memory Cell Access	Each cell is accessed directly, unlike Sequential Access Memory (SAM)	


Transistor Recap

 

Transistor is a fast switch:

If there is voltage at the Base terminal (Base = "1"), then current flows between Emitter and Collector;
Otherwise (Base = "0"), there is no current

Transistor Recap

 


Note: Current direction depends on the transistor type (e.g. NPN or PNP)

Transistor is a fast switch:

If there is voltage at the Base terminal (Base = "1"), then current flows between Emitter and Collector;
Otherwise (Base = "0"), there is no current

Transistor Recap

 

Transistor is a fast switch:


If there is voltage at the Base terminal (Base = "1"), then current flows between Emitter and Collector;
Otherwise (Base = "0"), there is no current

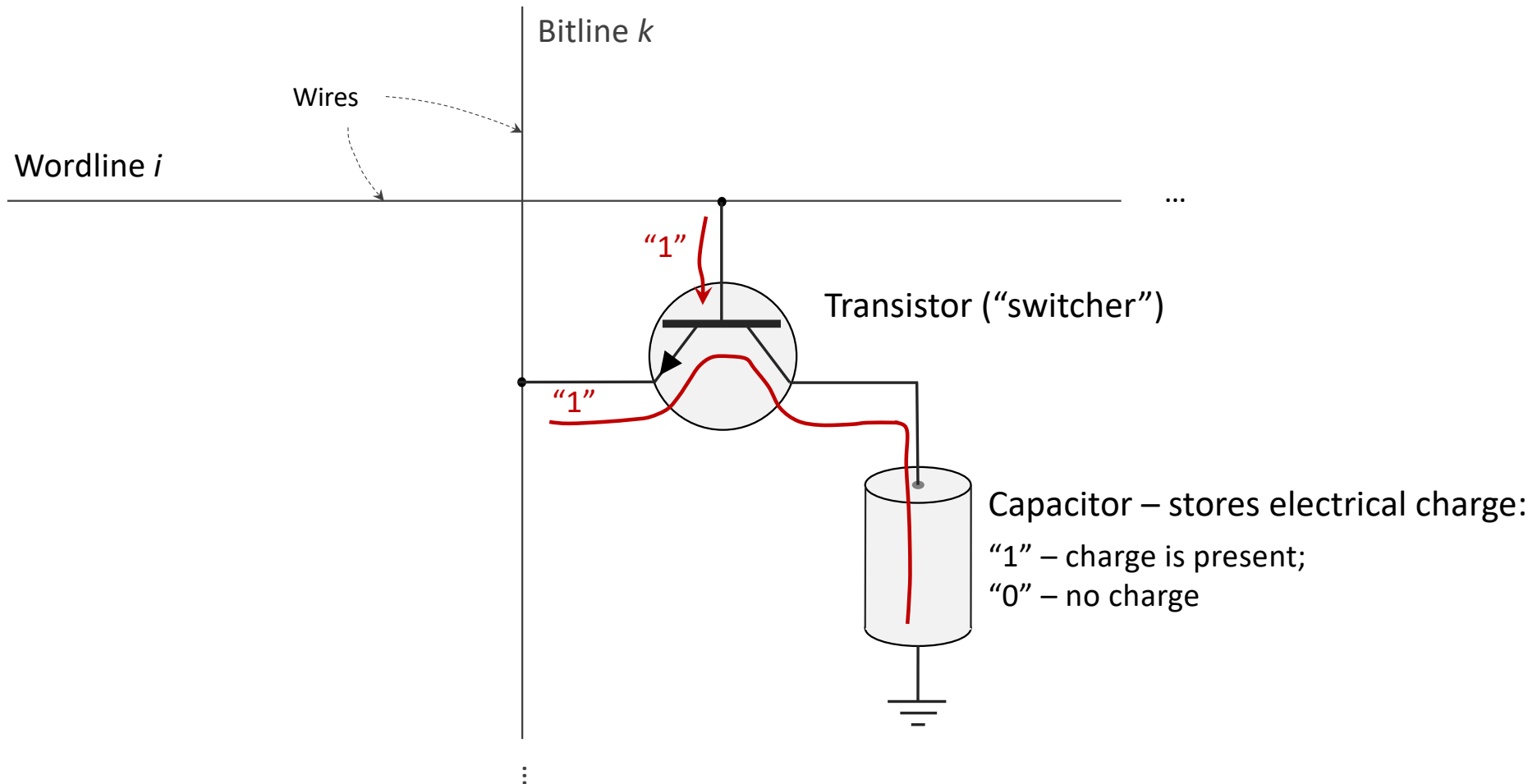Capacitor: a physical device to store electrical charge

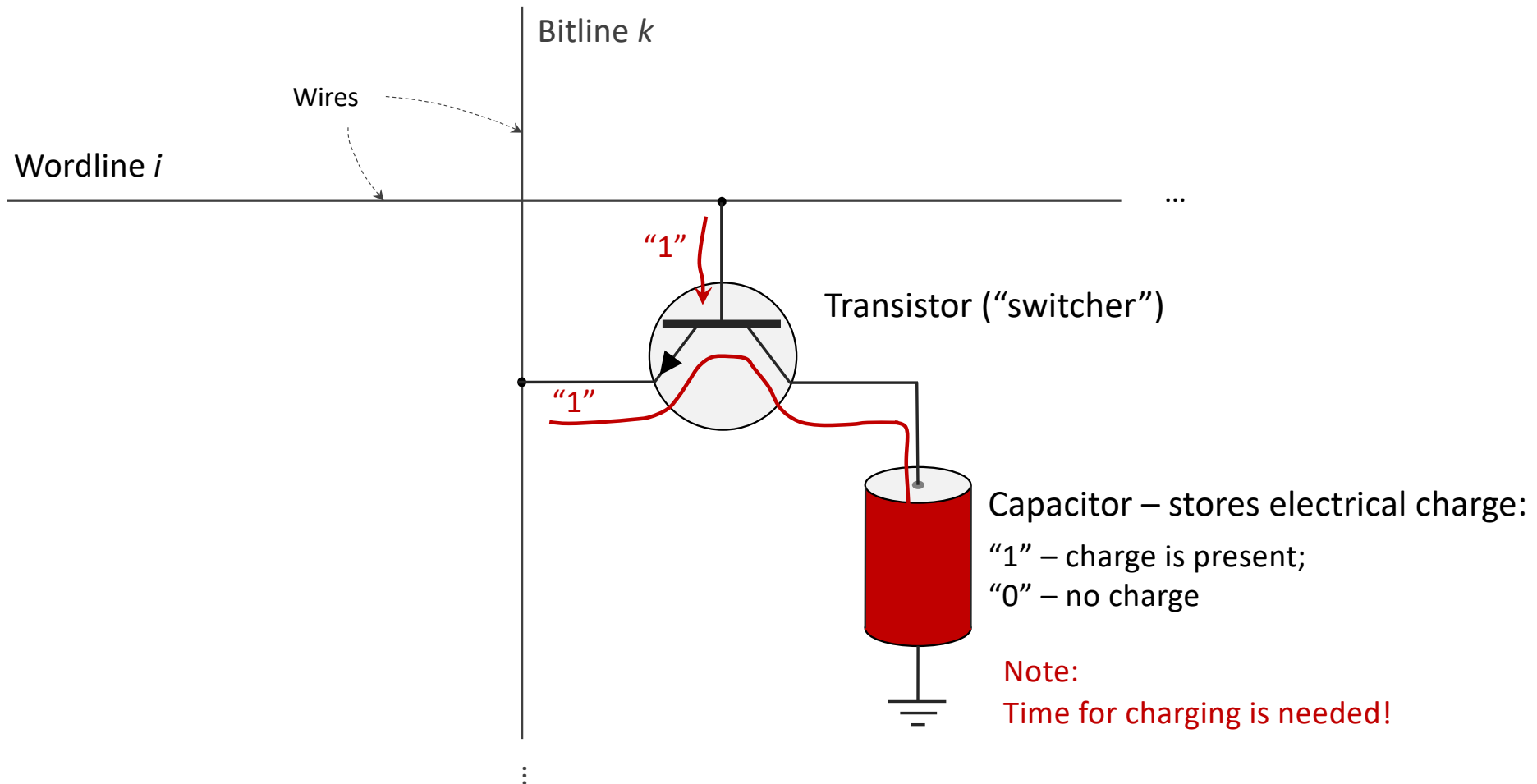


Image is taken from <https://en.wikipedia.org/wiki/Capacitor>


DRAM memory cell




DRAM memory cell



DRAM memory cell

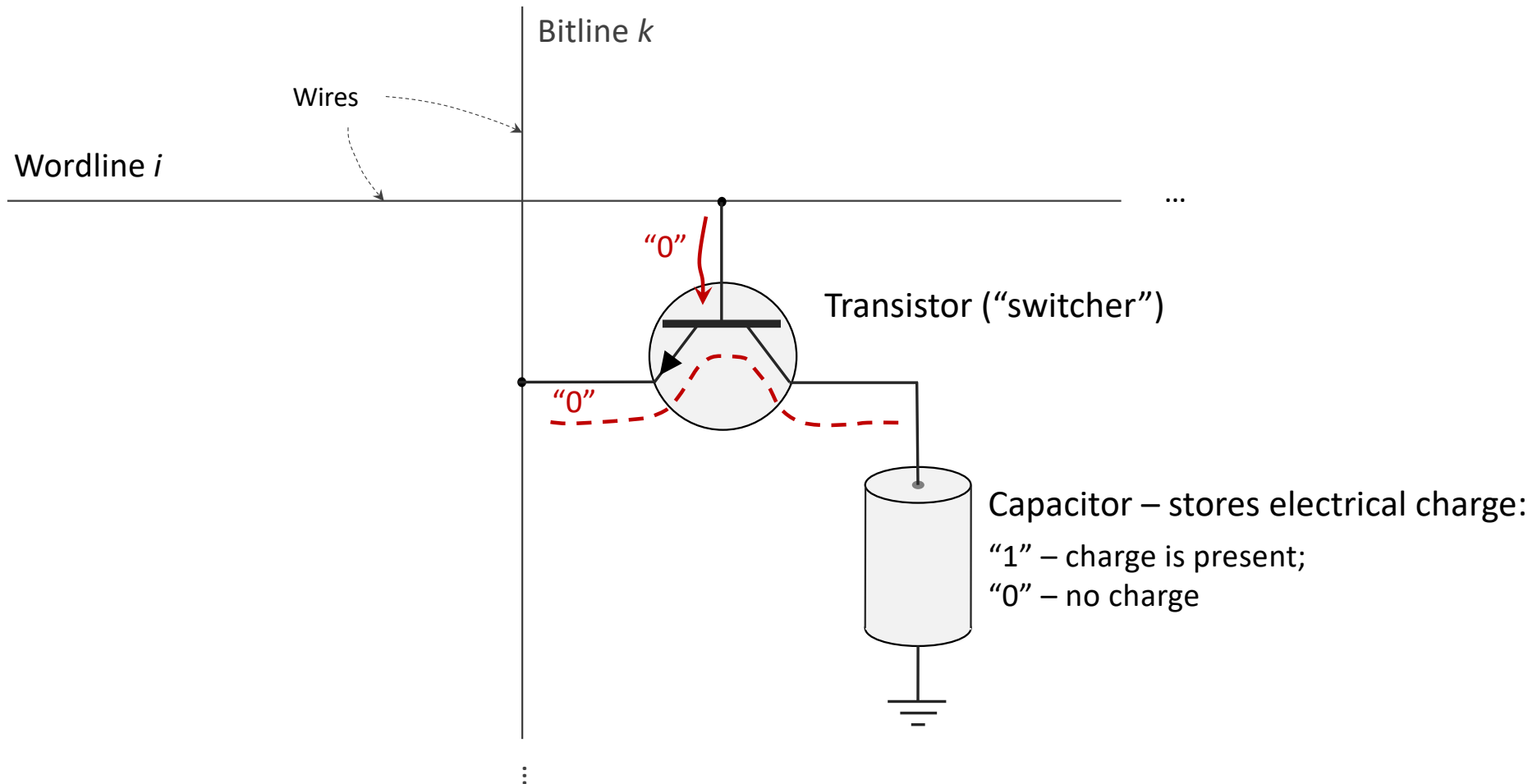

DRAM memory cell

 

DRAM memory cell: capacitor + transistor

DRAM memory cell


Wordline i

activates memory cell
for read/write operations:

Input "1" – line selected for operation,
and thus, transistor is "ON";

Input "0" – line is deactivated

Bitline k

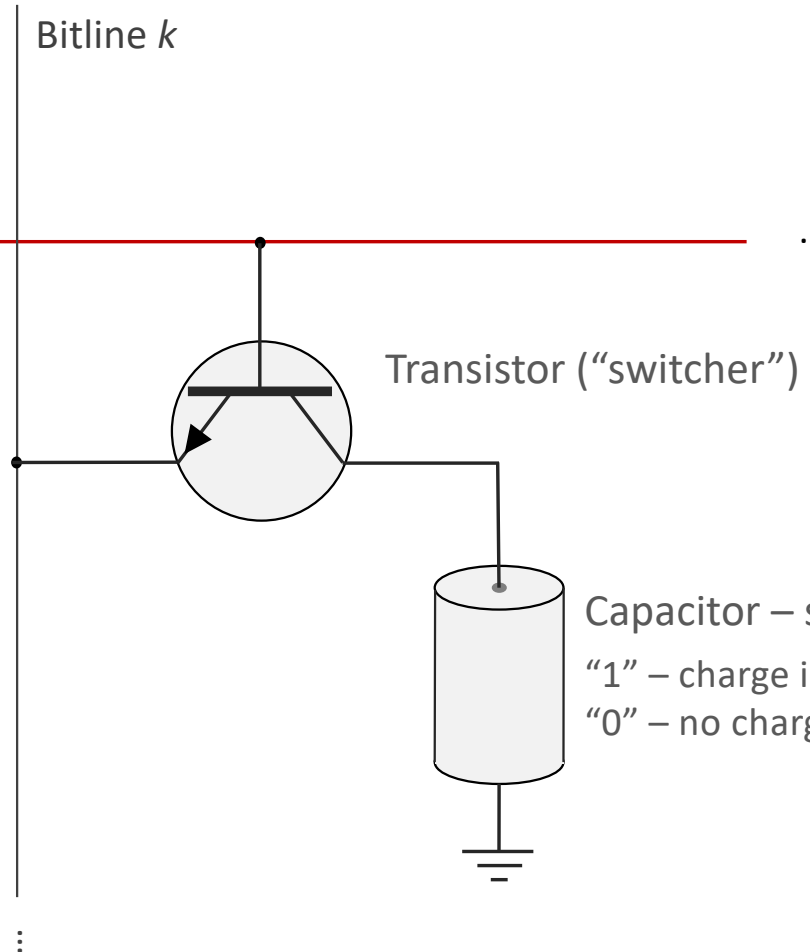


Transistor ("switcher")

Capacitor – stores electrical charge:


"1" – charge is present;

"0" – no charge

DRAM memory cell

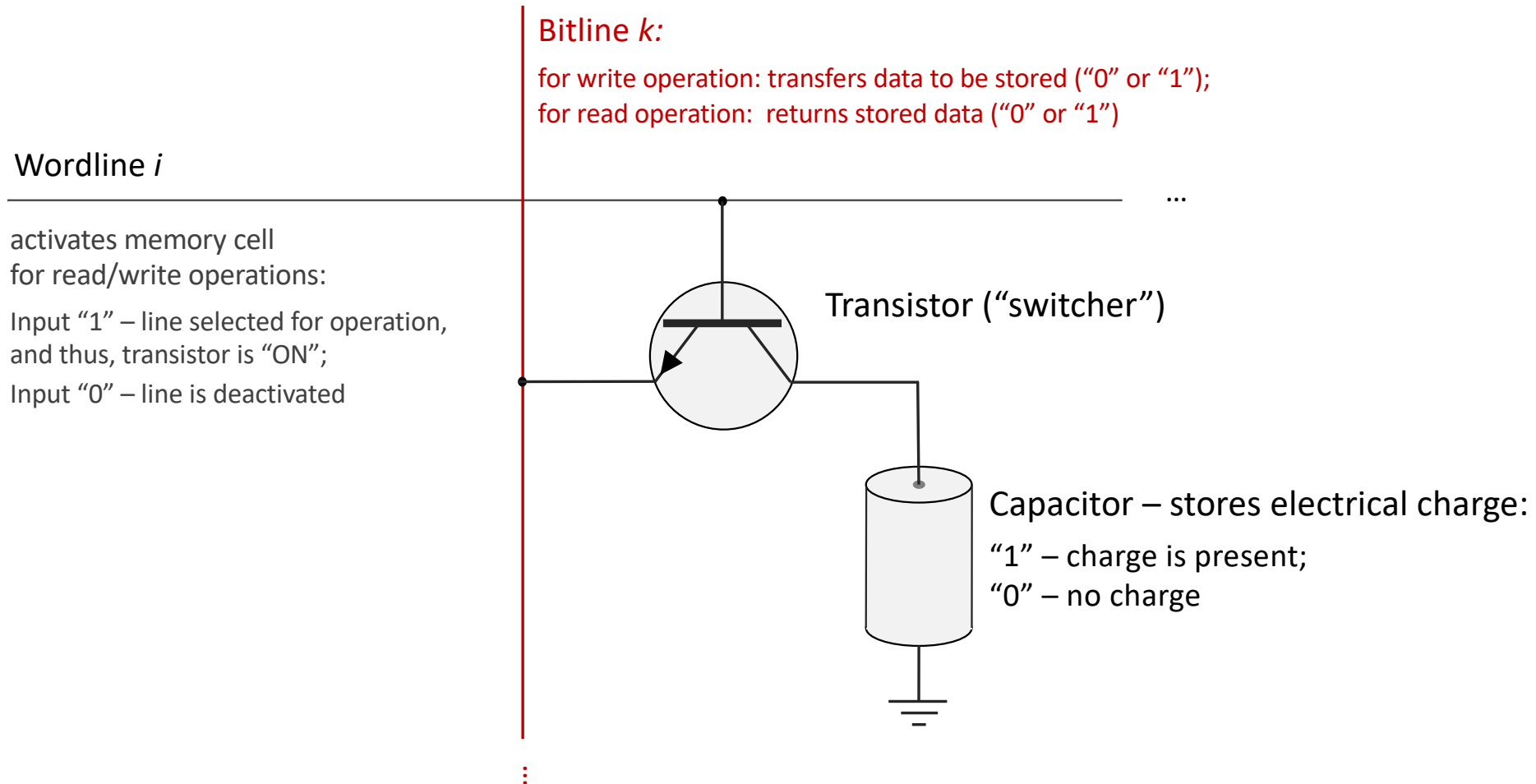

Writing into DRAM memory cell

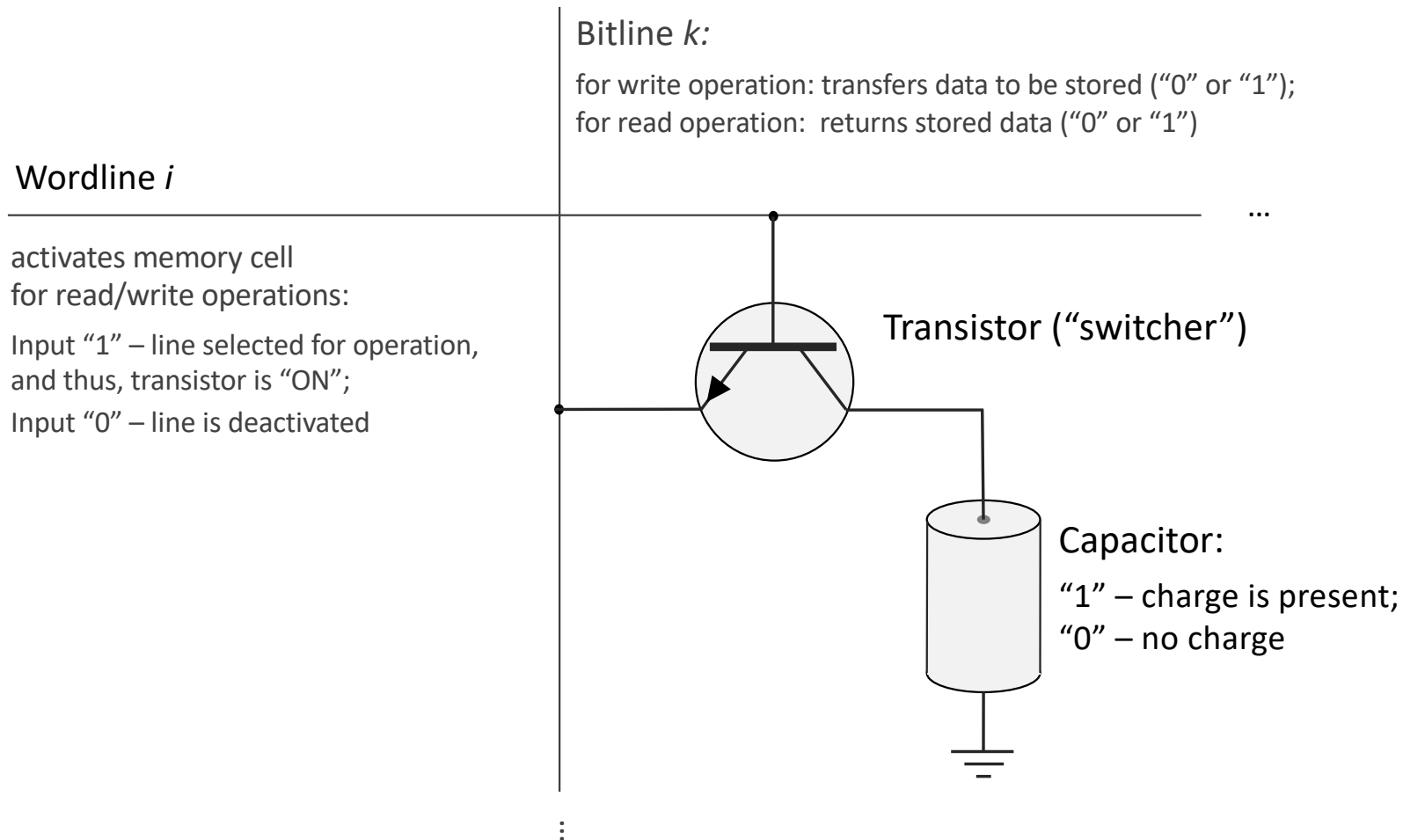

Writing into DRAM memory cell

1) Activation of the wordline,
corresponding to the address of a
memory cell;

Wordline i

activates memory cell
for read/write operations:

Input "1" – line selected for operation,
and thus, transistor is "ON";

Input "0" – line is deactivated

Bitline k :

for write operation: transfers data to be stored ("0" or "1");

for read operation: returns stored data ("0" or "1")

"1"

Transistor ("switcher")

Capacitor:

"1" – charge is present;

"0" – no charge

⋮

Writing into DRAM memory cell

1) Activation of the wordline,
corresponding to the address of a
memory cell;

Wordline i

activates memory cell
for read/write operations:

Input "1" – line selected for operation,
and thus, transistor is "ON";

Input "0" – line is deactivated

2) Transistor is turned on;

Bitline k :

for write operation: transfers data to be stored ("0" or "1");

for read operation: returns stored data ("0" or "1")

"1"


"1"

Transistor ("switcher")

Capacitor:

"1" – charge is present;

"0" – no charge

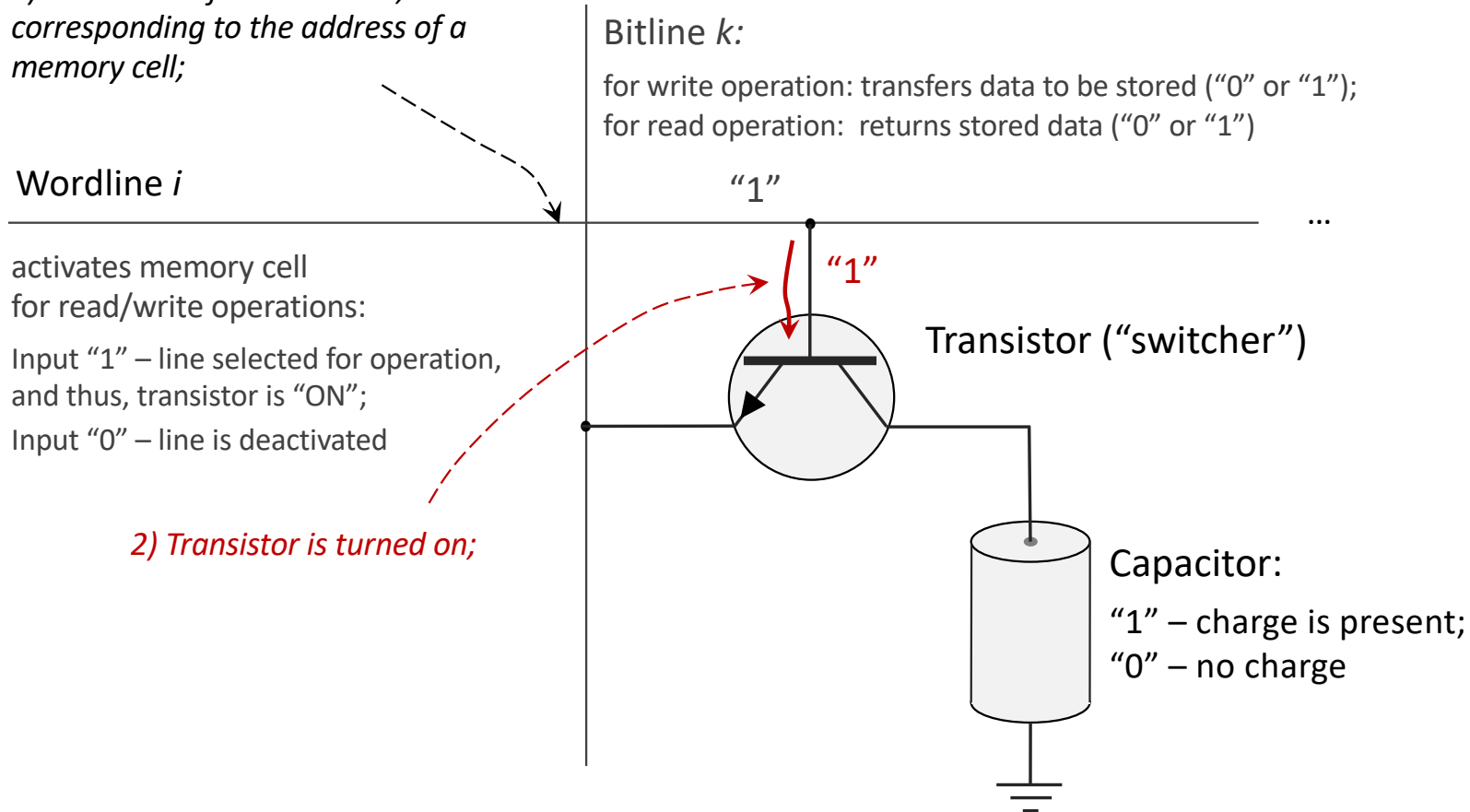

Writing into DRAM memory cell

1) Activation of the wordline, corresponding to the address of a memory cell;

Wordline i

activates memory cell for read/write operations:

Input "1" – line selected for operation, and thus, transistor is "ON";

Input "0" – line is deactivated

2) Transistor is turned on;

Bitline k :

for write operation: transfers data to be stored ("0" or "1");

for read operation: returns stored data ("0" or "1")

"1"

"1"

Transistor ("switcher")

"1"

"1"

Capacitor:

"1" – charge is present;

"0" – no charge

3) Transferring data bit over the bitline, to be stored;

If "1" – capacitor gets charged (however, some time for charging is needed)

Writing into DRAM memory cell

1) Activation of the wordline, corresponding to the address of a memory cell;

Wordline i

activates memory cell for read/write operations:

Input "1" – line selected for operation, and thus, transistor is "ON";

Input "0" – line is deactivated

2) Transistor is turned on;

Bitline k :

for write operation: transfers data to be stored ("0" or "1");

for read operation: returns stored data ("0" or "1")

"1"

"1"

Transistor ("switcher")

"0"

discharging

Capacitor:

"1" – charge is present;

"0" – no charge

"0"

3) Transferring data bit over the bitline, to be stored;

If "1" – capacitor gets charged (however, some time for charging is needed);

Else if "0" – capacitor is discharged

Writing into DRAM memory cell

1) Activation of the wordline, corresponding to the address of a memory cell;

Wordline i

activates memory cell for read/write operations:

Input "1" – line selected for operation, and thus, transistor is "ON";

Input "0" – line is deactivated

2) Transistor is turned on;

Bitline k :

for write operation: transfers data to be stored ("0" or "1");
for read operation: returns stored data ("0" or "1")

"1"

"1"

Transistor ("switcher")

"0"

"0"

Capacitor:

"1" – charge is present;
"0" – no charge

3) Transferring data bit over the bitline, to be stored;

If "1" – capacitor gets charged (however, some time for charging is needed);

Else if "0" – capacitor is discharged

Reading from DRAM memory cell

1) Activation of the wordline,
corresponding to the address of a
memory cell;

Wordline i

activates memory cell
for read/write operations:

Input "1" – line selected for operation,
and thus, transistor is "ON";

Input "0" – line is deactivated

2) Transistor is turned on;

Bitline k :

for write operation: transfers data to be stored ("0" or "1");

for read operation: returns stored data ("0" or "1")

"1"

"1"


Transistor ("switcher")

discharging

Capacitor:

"1" – charge is present;

"0" – no charge

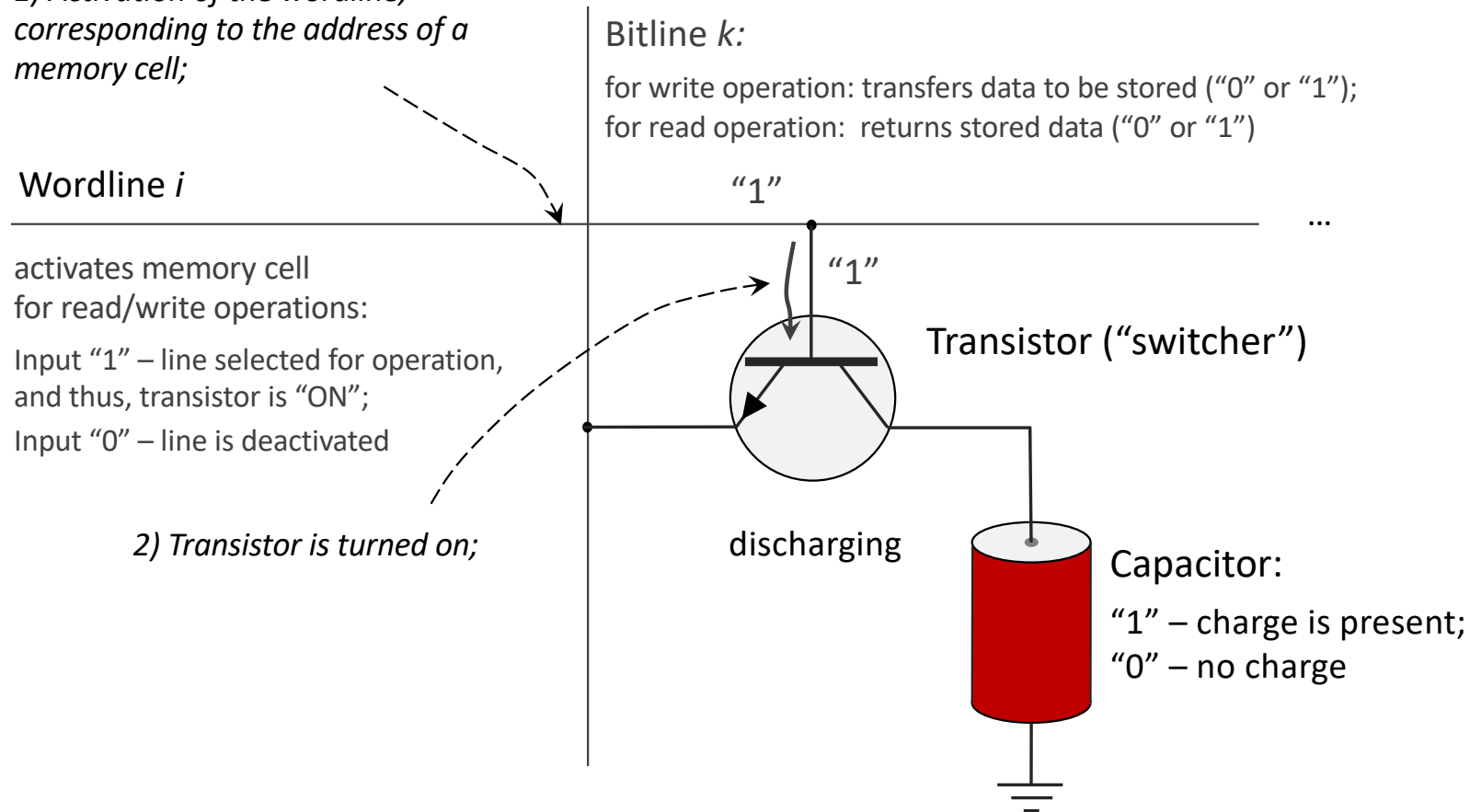

Reading from DRAM memory cell

1) Activation of the wordline, corresponding to the address of a memory cell;

Wordline i

activates memory cell for read/write operations:

Input "1" – line selected for operation, and thus, transistor is "ON";

Input "0" – line is deactivated

2) Transistor is turned on;

Bitline k :

for write operation: transfers data to be stored ("0" or "1");

for read operation: returns stored data ("0" or "1")

"1"

"1"

Transistor ("switcher")

"1"

discharging


Capacitor:

"1" – charge is present;


"0" – no charge

 3) Transferring data bit from capacitor over the bitline


A More Compact Graphical Notation for Electrical Circuits



 A More Compact Graphical Notation for Electrical Circuits




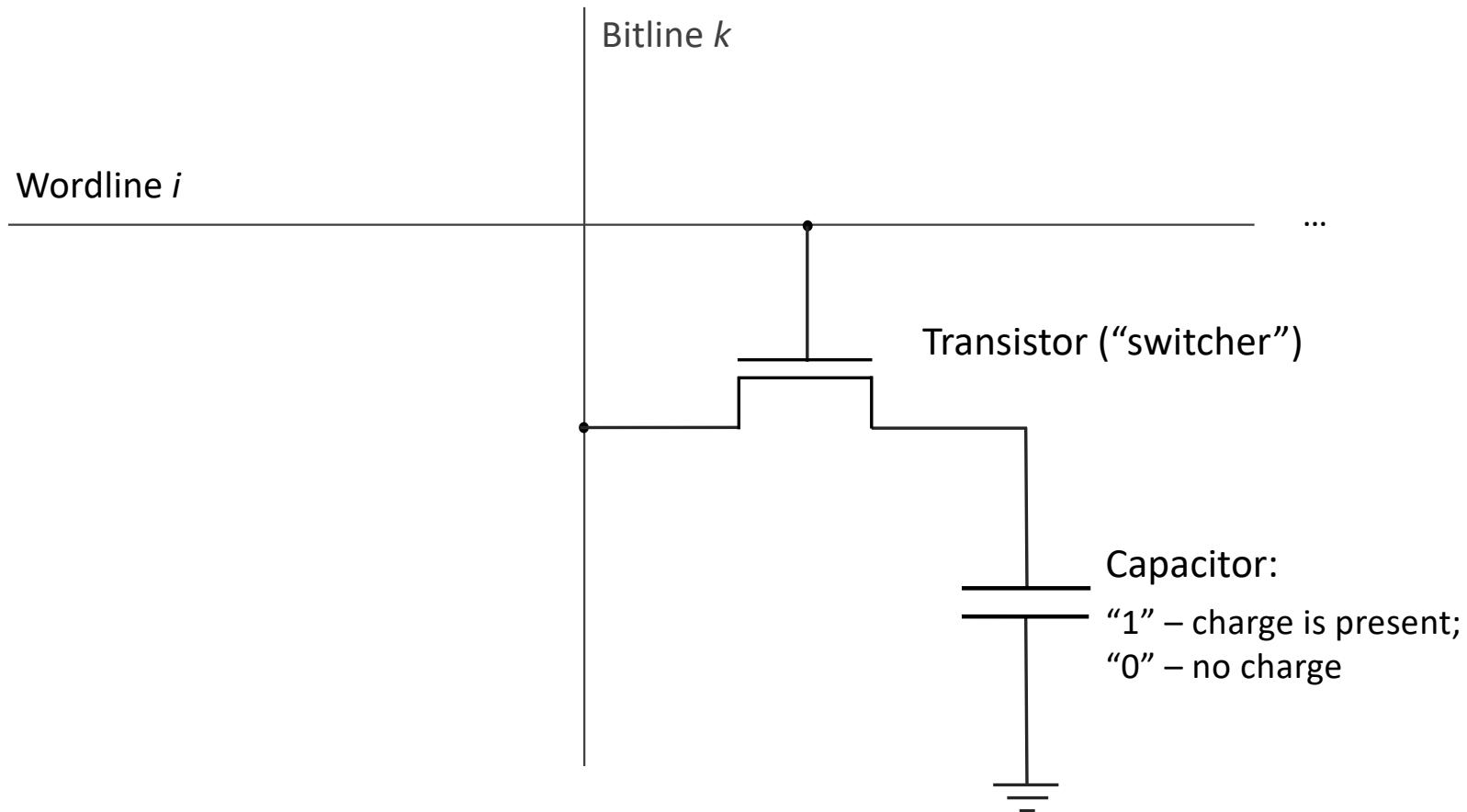A More Compact Graphical Notation for Electrical Circuits



DRAM memory – a set of memory cells
(each cell contains 1 bit of data)


DRAM Memory: the Work Principle

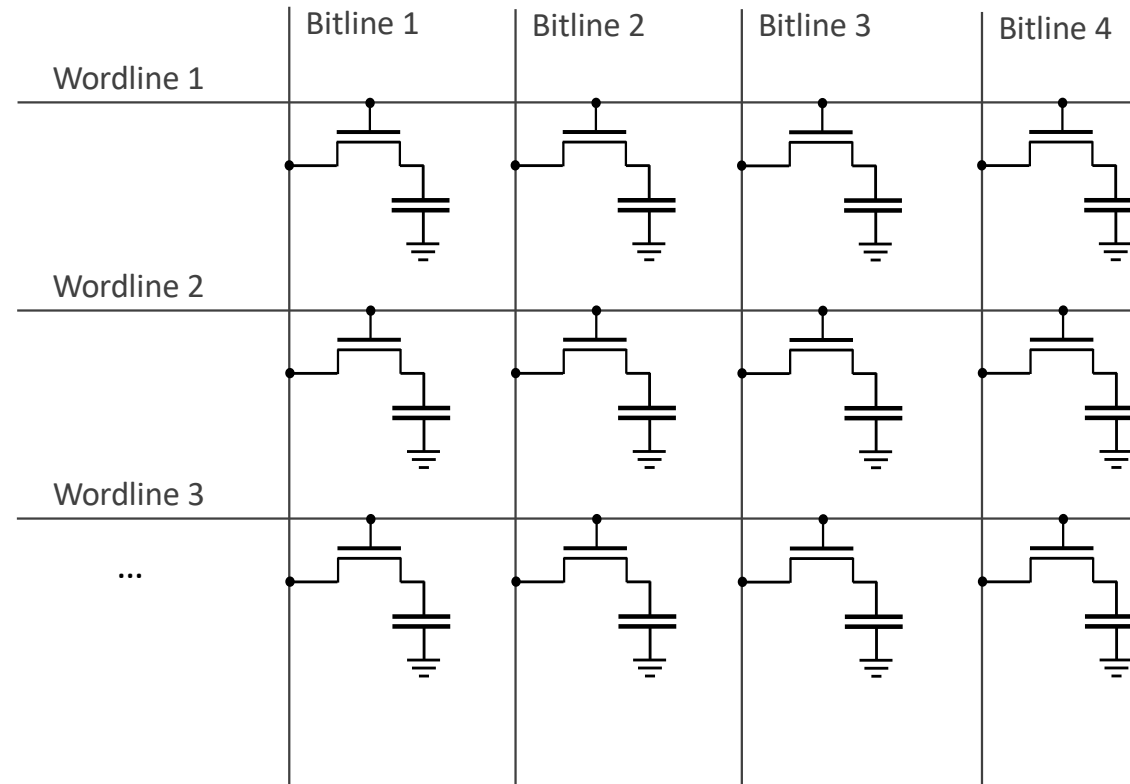

DRAM memory – a set of memory cells
(each cell contains 1 bit of data)


DRAM Memory: the Work Principle

 Several memory cells are
connected to the same wordline




Memory controller operates with memory cells,
by using demultiplexors, encoders, etc.


DRAM Memory: the Work Principle

 

DRAM Memory: the Work Principle

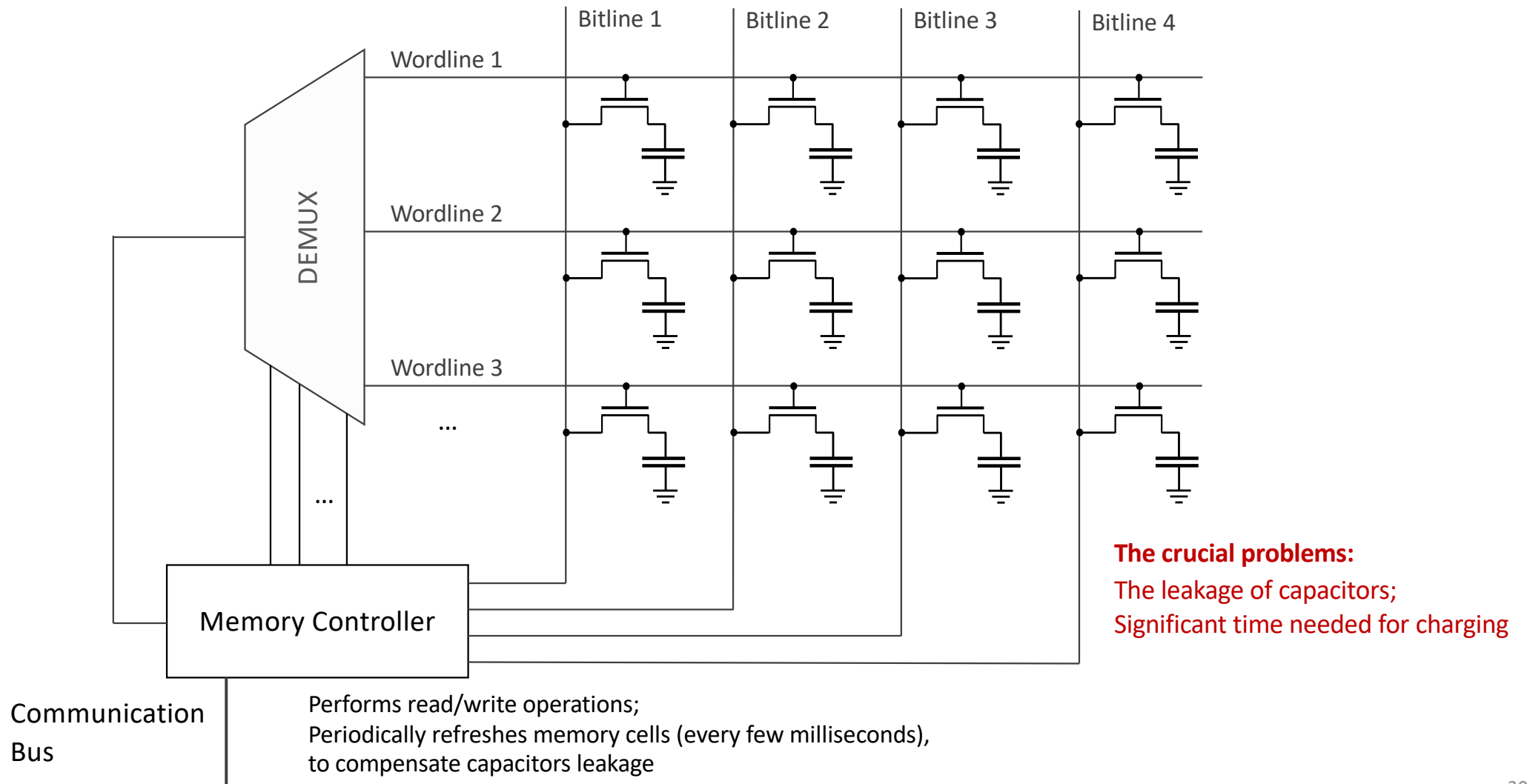

DRAM Memory: the Work Principle

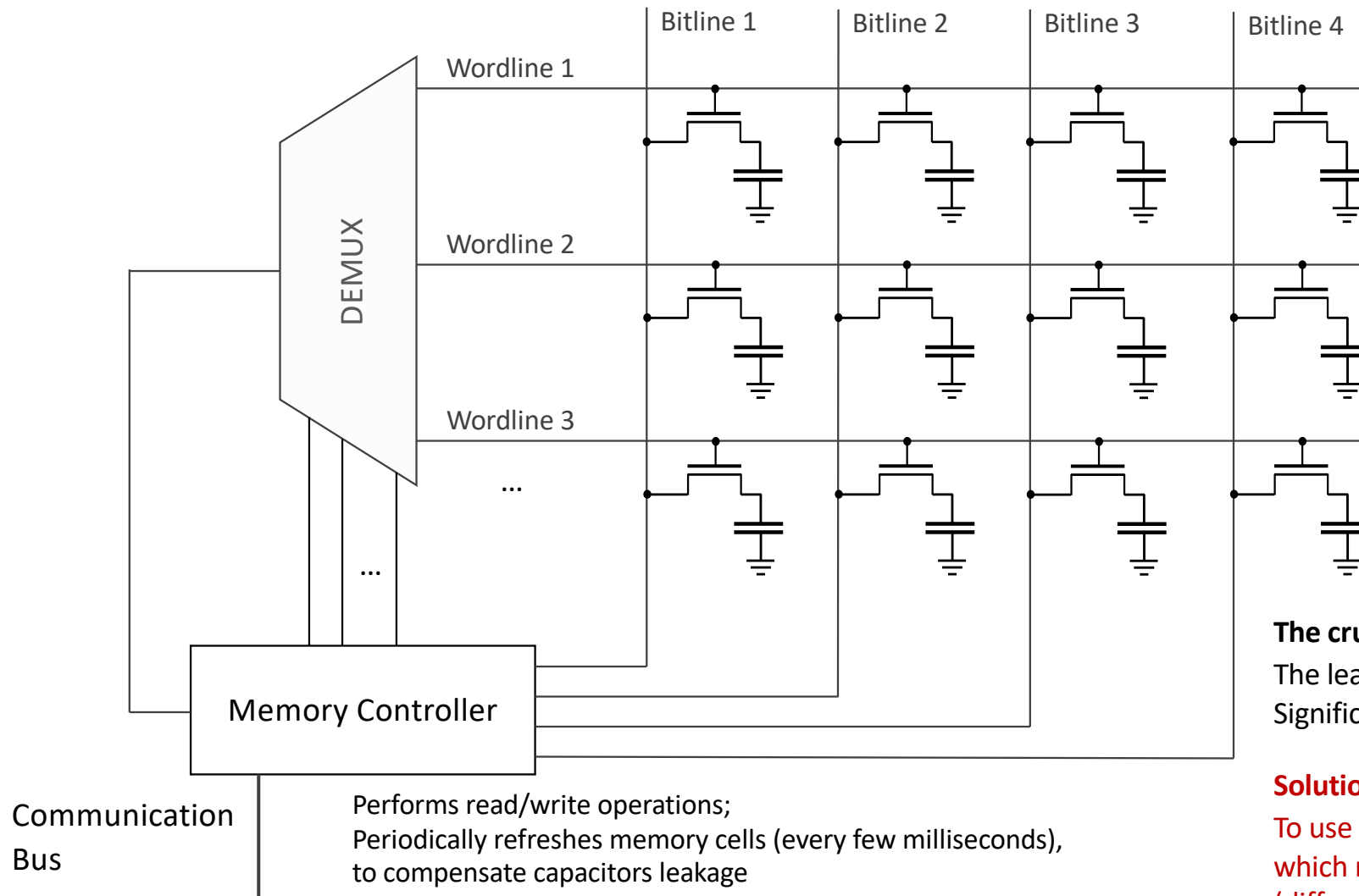


The crucial problems:

The leakage of capacitors;
Significant time needed for charging

Solution:

To use SRAM,
which relies on latches and flip-flops
(different from capacitors)

 
Latch Recap: an electronic circuit to store one bit of information




S	R	Q
1	0	1
0	1	0
0	0	Q^{prev}
1	1	Illegal inputs

Latch Recap: multiple logic implementations are available

 1) Implementation by using NOR logic gates:




2) by using NAND logic gates:

 

These representations are logical oversimplified representations, hiding many implementation details


Latch Logical representation:

 


Before usage, latch is initialized by one of these input combinations:
either $R = 1$ & $S = 0$, or $S = 1$ & $R = 0$;

Latch hardware implementation should be such, that one of these input combinations results into Q and \overline{Q} according to a latch specification

 Electrical circuit implementation (one of many):



Latch Logical representation:

 


Before usage, latch is initialized by one of these input combinations:



either $R = 1$ & $S = 0$, or $S = 1$ & $R = 0$;

Latch hardware implementation should be such, that one of these input combinations results into Q and \bar{Q} according to a latch specification

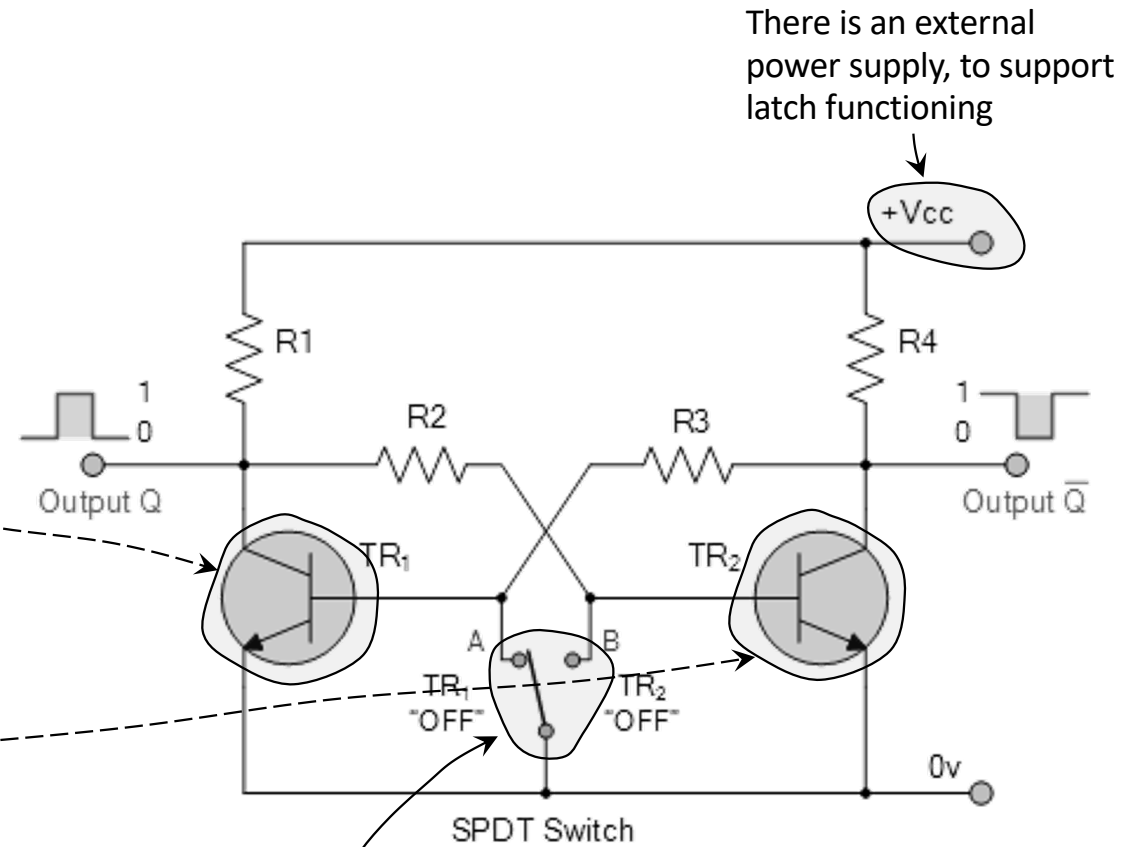
Electrical circuit implementation (one of many):




State Transition Diagram for a Latch

 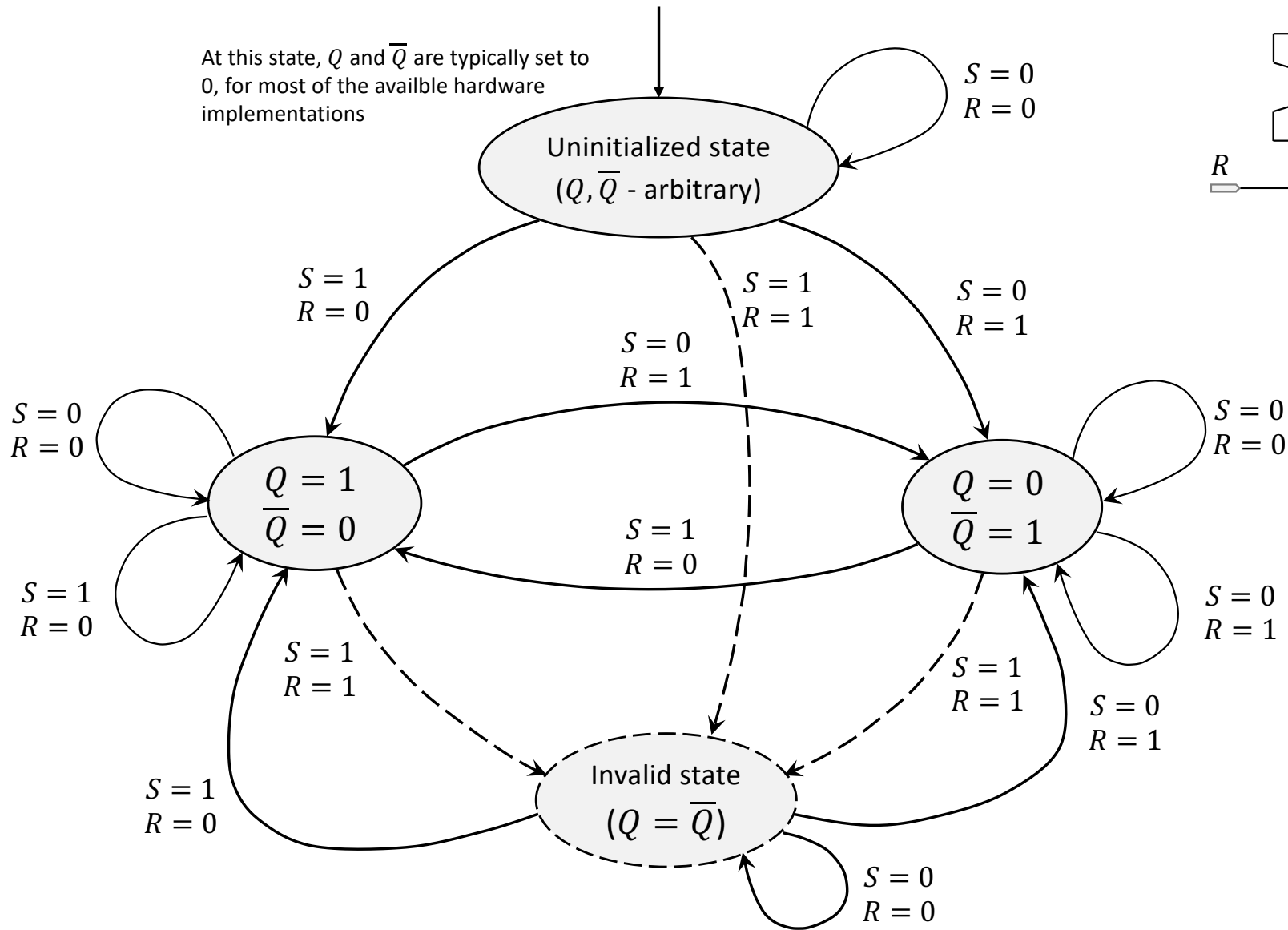

 Recap: A Synchronous Flip-Flop Constructed of S/R Latches




 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed		
Storage Capacity		
Storage Element		
Usage		
Cost		
Power Consumption		
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity		
Storage Element		
Usage		
Cost		
Power Consumption		
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

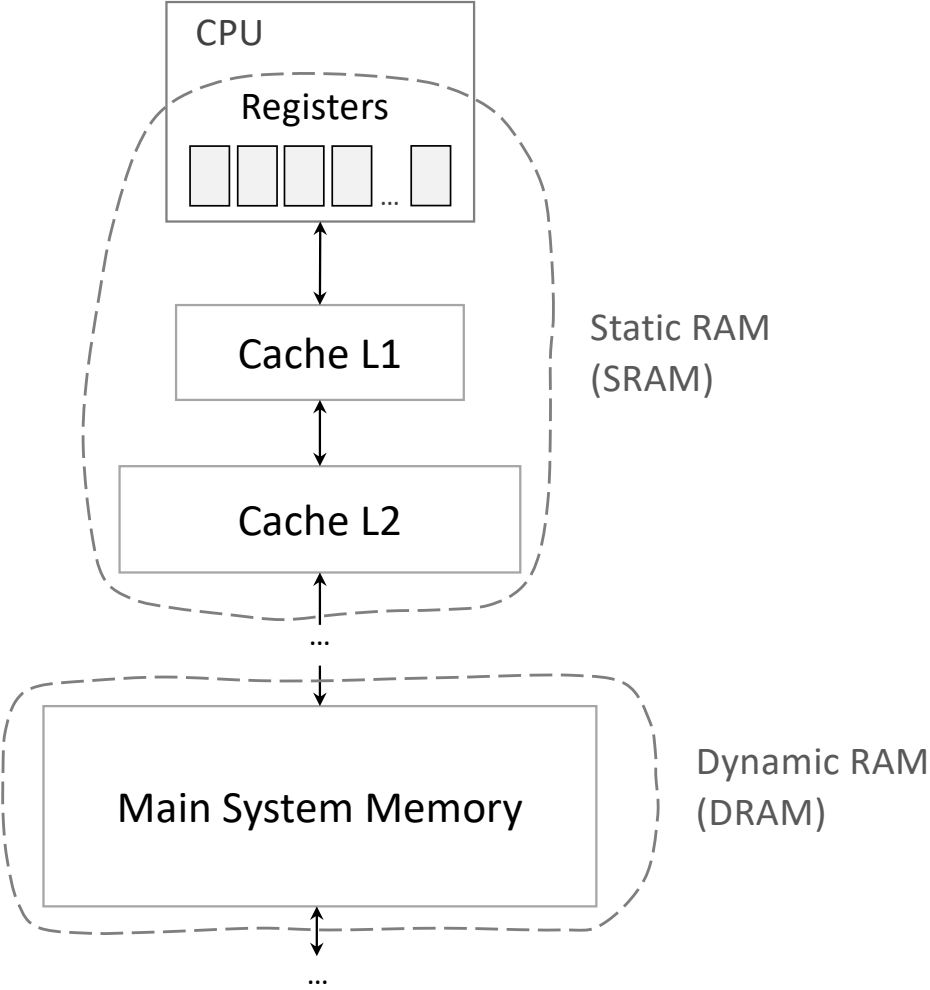The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element		
Usage		
Cost		
Power Consumption		
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage		
Cost		
Power Consumption		
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost		
Power Consumption		
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption		
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation		
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage		
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability		
Volatility		
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability	More reliable	Less reliable
Volatility		
Memory Cell Access		

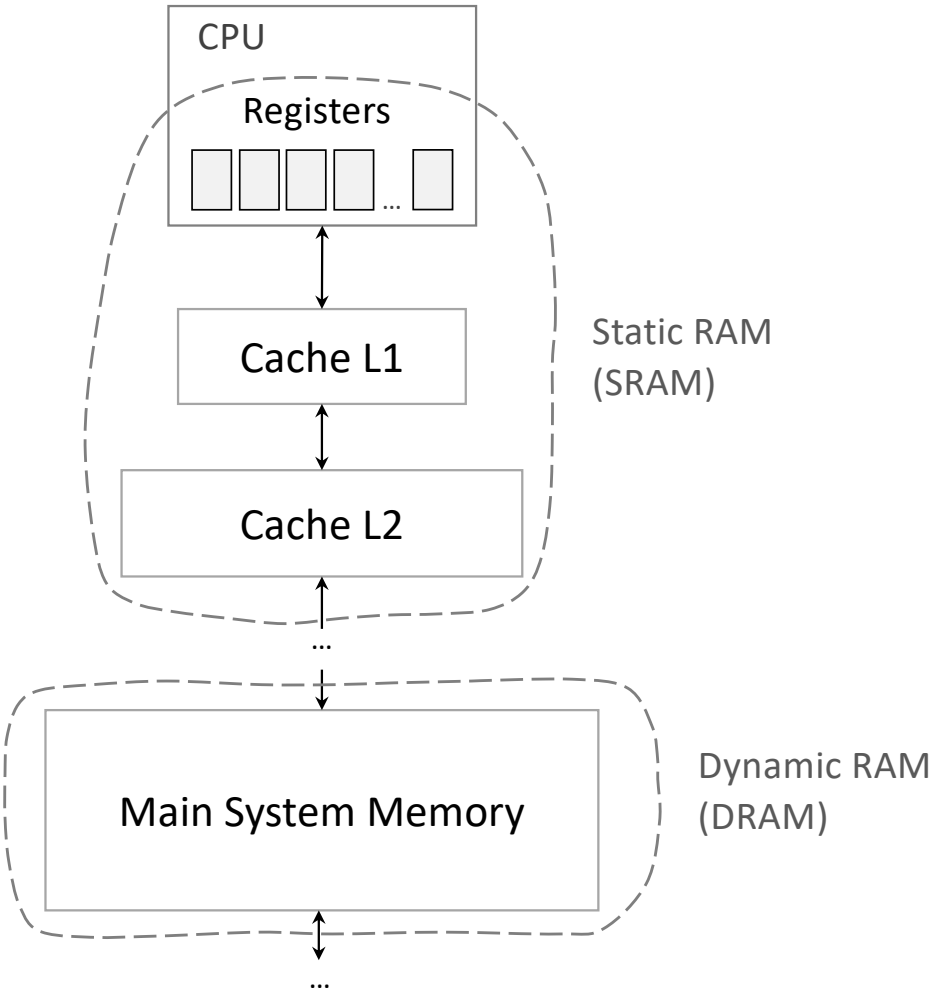The Comparison of DRAM and SRAM Memory Types




Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability	More reliable	Less reliable
Volatility	Both are volatile (lose data if power is off)	
Memory Cell Access		

 The Comparison of DRAM and SRAM Memory Types



Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability	More reliable	Less reliable
Volatility	Both are volatile (require electrical power to keep data)	
Memory Cell Access	Each cell is accessed directly, unlike Sequential Access Memory (SAM)	

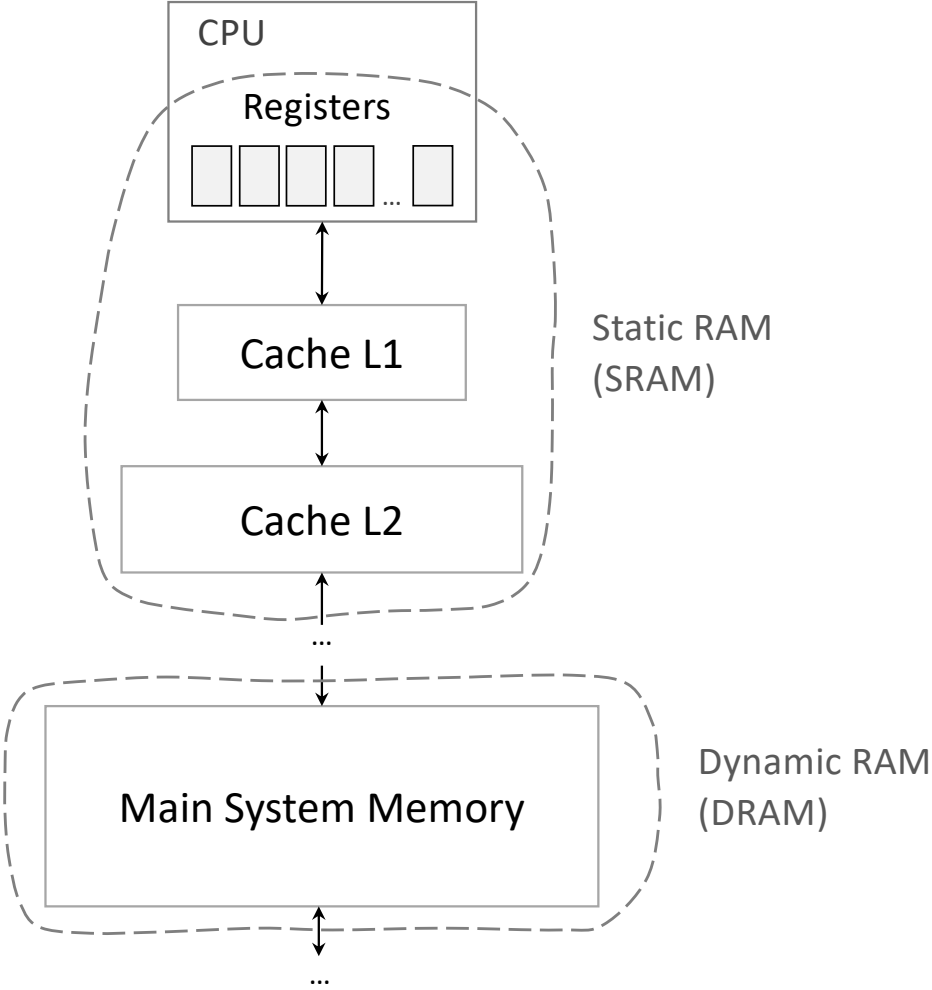The Comparison of DRAM and SRAM Memory Types



Characteristic	SRAM	DRAM
Access Speed	Faster	Slower
Storage Capacity	Smaller	Larger
Storage Element	Flip-flop	Capacitor
Usage	CPU cache, registers	System memory
Cost	Expensive	Cheaper
Power Consumption	Lower	Higher
Organisation	Complex	Simpler
Power Leakage	Not present	Significant
Chip Reliability	More reliable	Less reliable
Volatility	Both are volatile (require electrical power to keep data)	
Memory Cell Access	Each cell is accessed directly, unlike Sequential Access Memory (SAM)	