

Computer Architecture

Lecture 05

## **Finite State Machines**

### **Synchronous and Asynchronous Circuits**


Artem Burmyakov, Alexander Tormasov

September 30, 2021



## Recap: S/R Latch (or Transparent Latch)

A circuit to store 1 bit of information

 


$S$	$R$	$Q$
1	0	1
0	1	0
0	0	$Q^{\text{prev}}$
1	1	Illegal inputs
 
## State Transition Diagram for a Latch



At this state,  $Q$  and  $\bar{Q}$  are typically set to 0, for most of the available hardware implementations

Uninitialized state  
( $Q, \bar{Q}$  - arbitrary)




  
## State Transition Diagram for a Latch



At this state,  $Q$  and  $\bar{Q}$  are typically set to 0, for most of the available hardware implementations





## State Transition Diagram for a Latch

 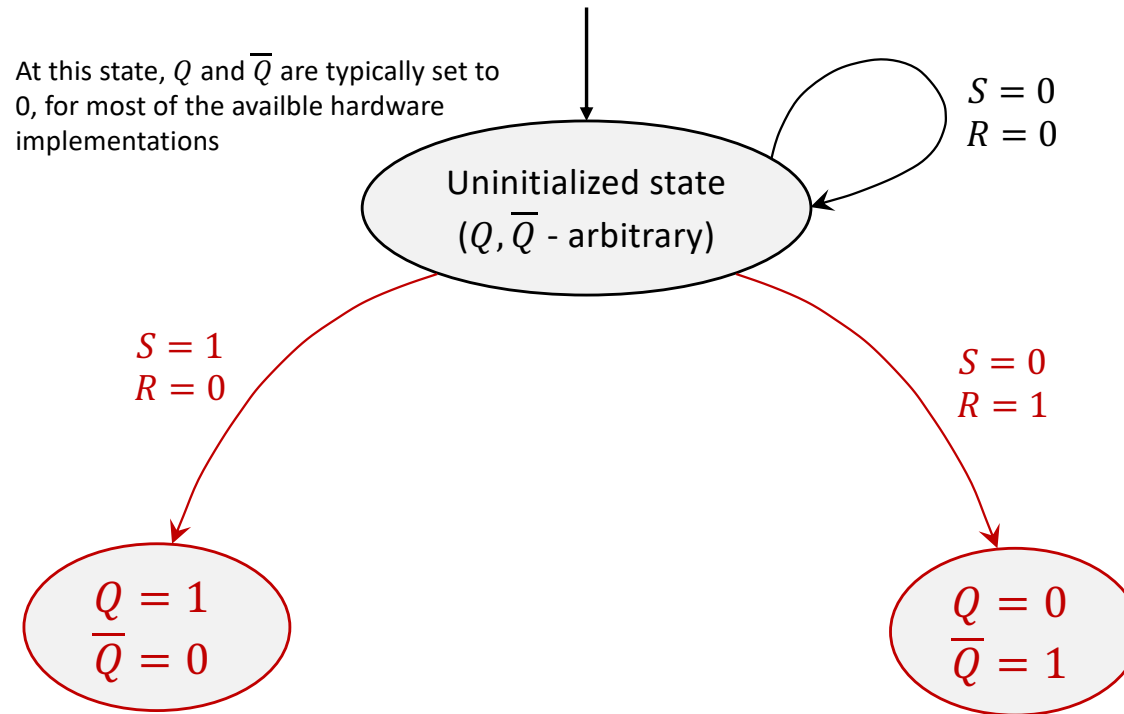



## State Transition Diagram for a Latch

  

## State Transition Diagram for a Latch

 
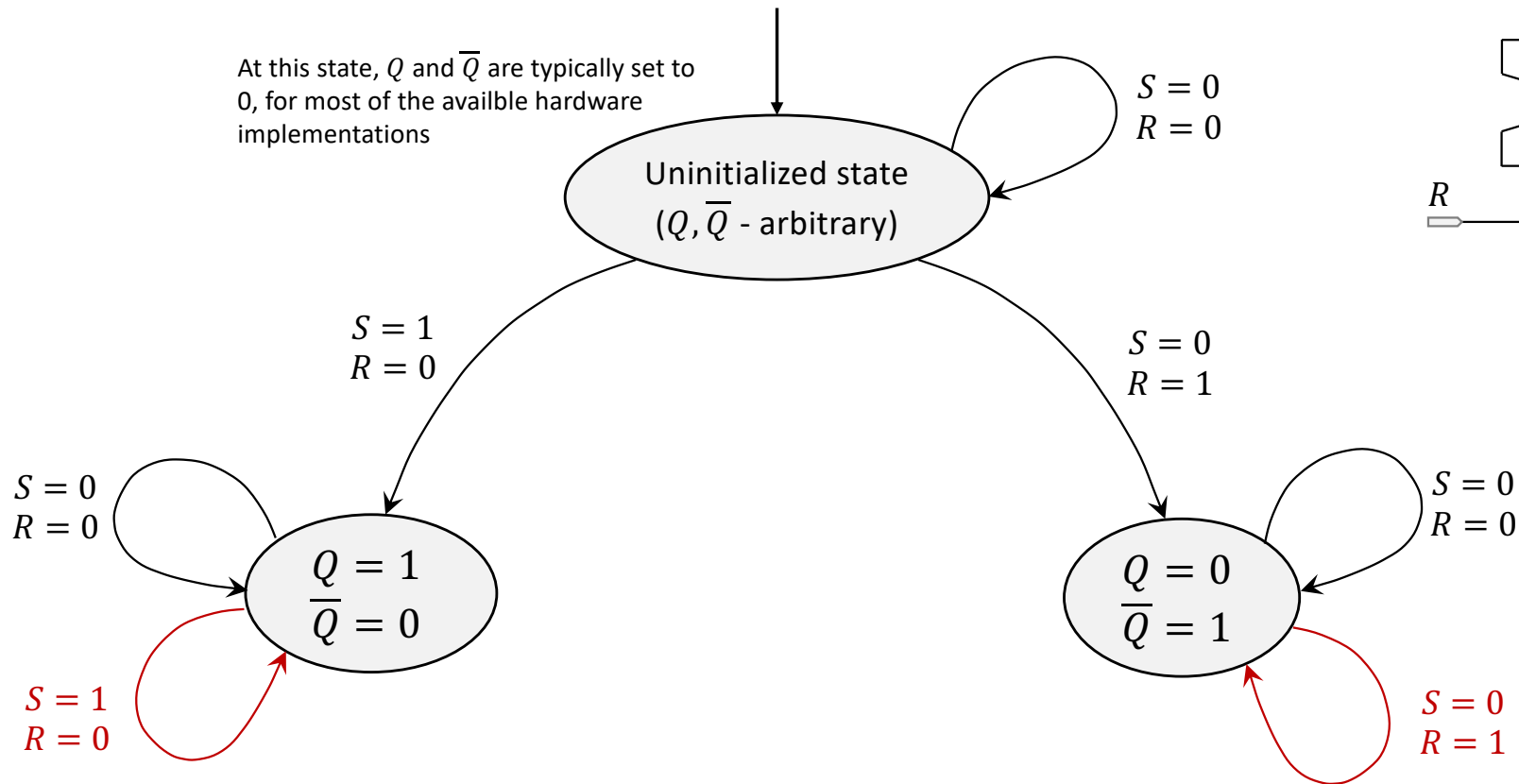


## State Transition Diagram for a Latch

 
 






## State Transition Diagram for a Latch

  



## State Transition Diagram for a Latch

 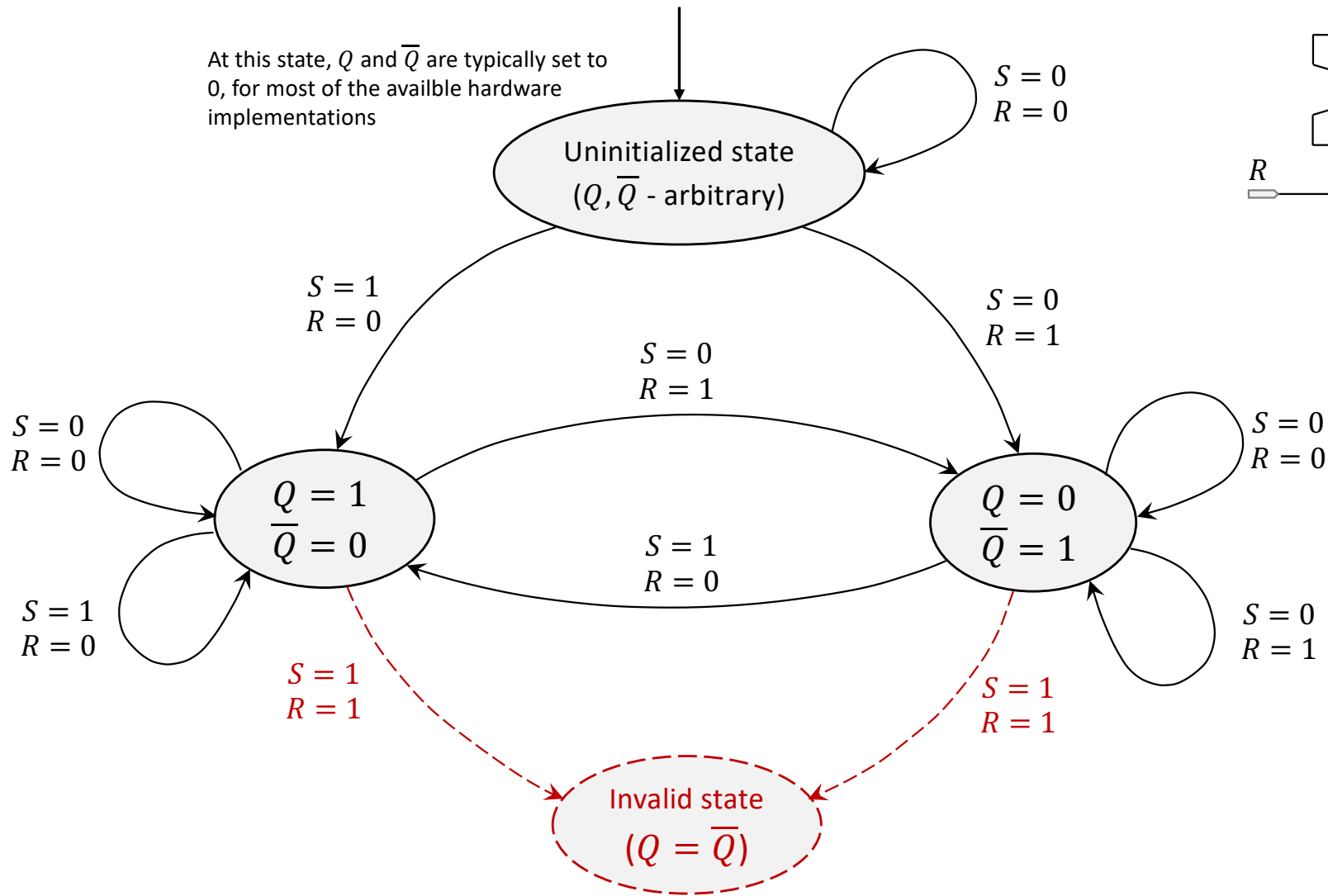

## State Transition Diagram for a Latch

 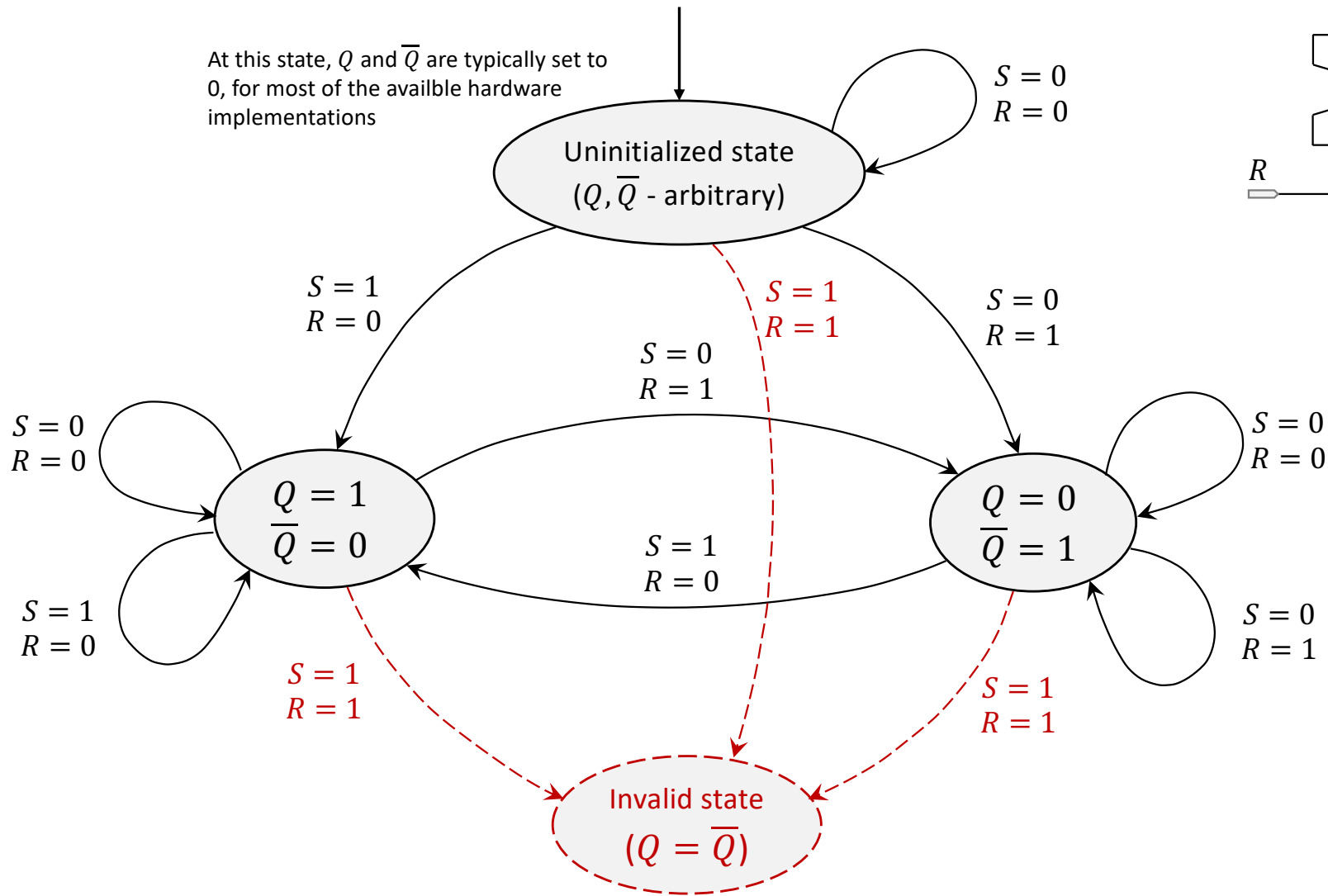


## State Transition Diagram for a Latch

 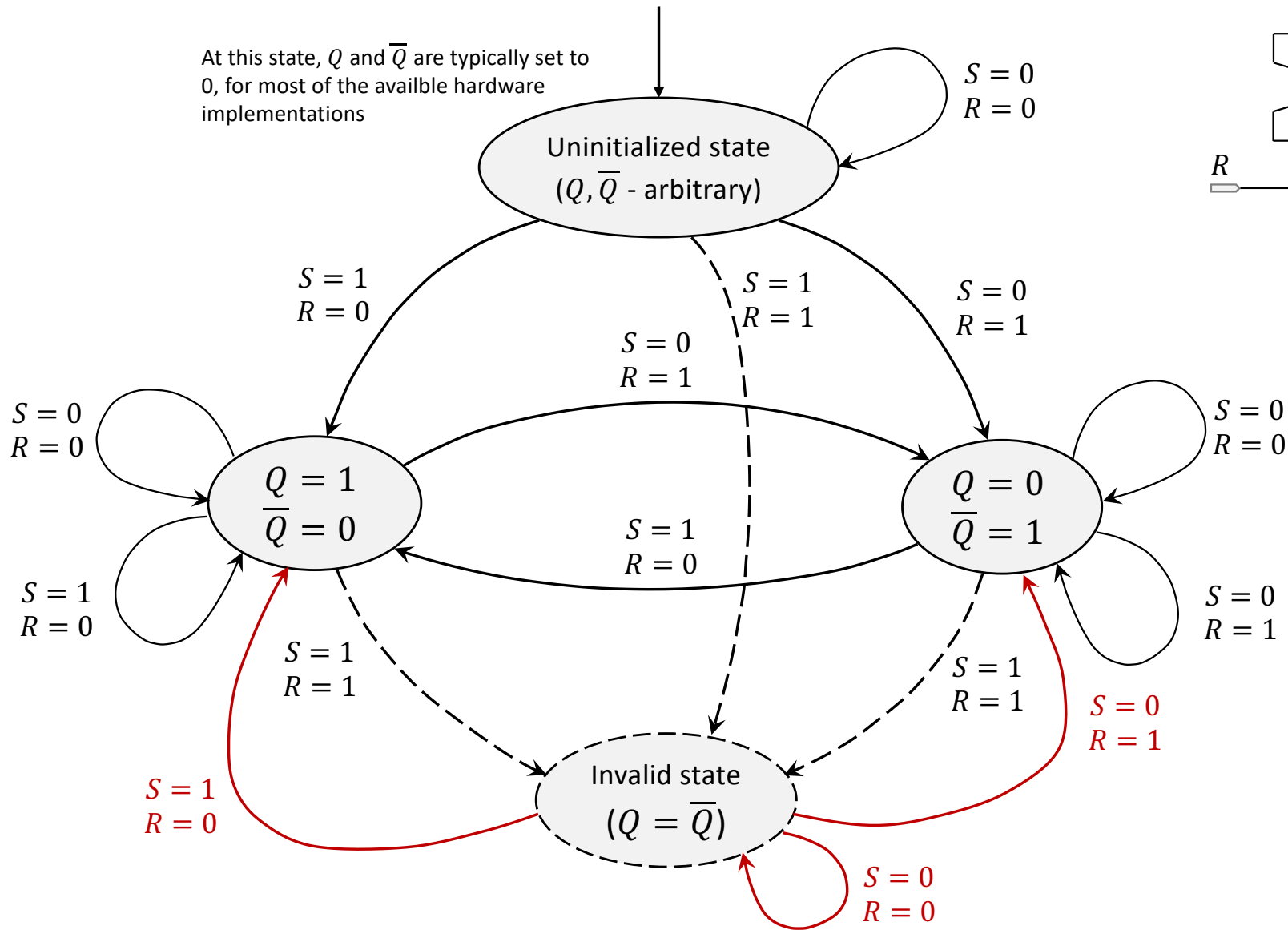

## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

### FSM - an abstract machine

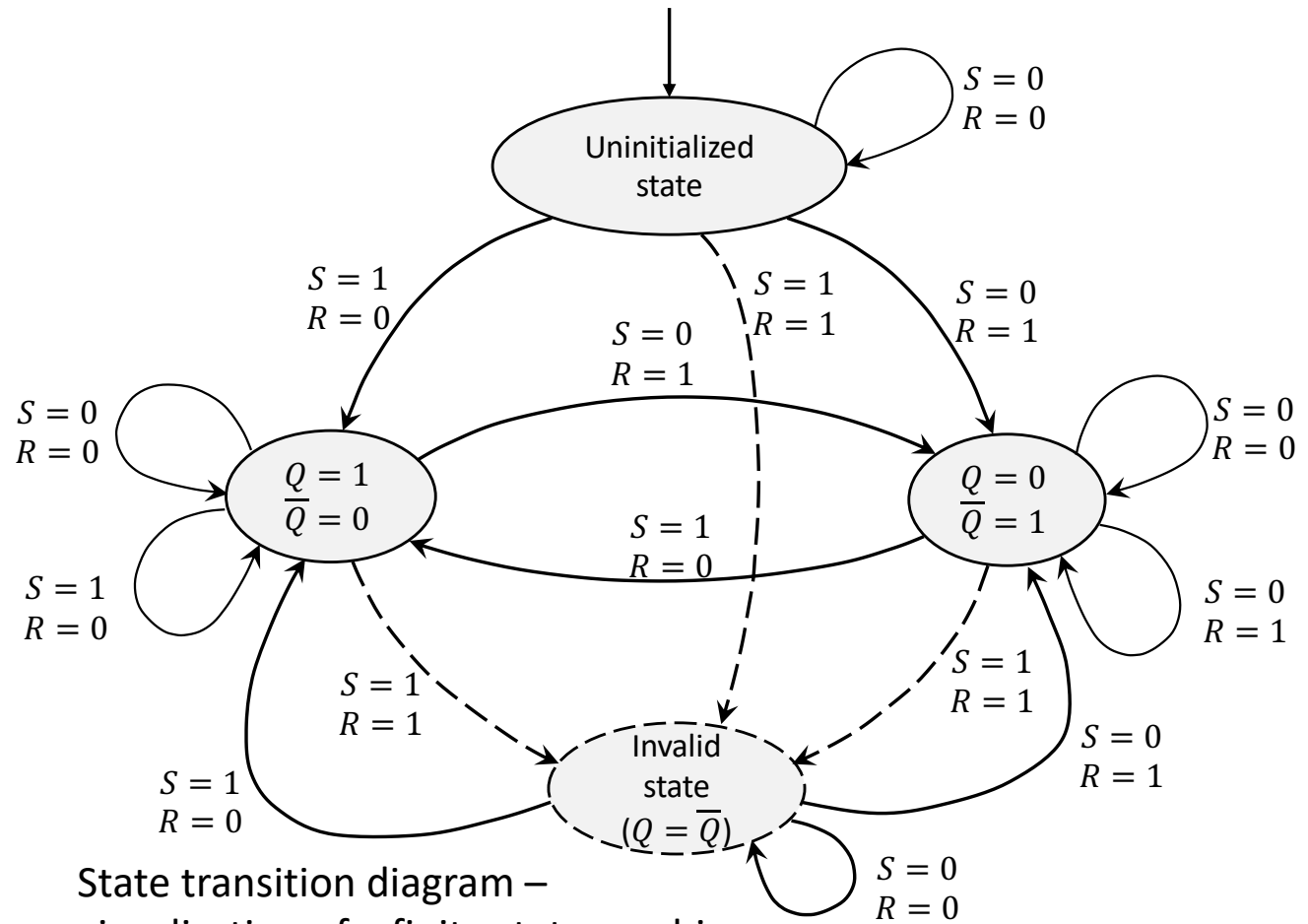


State transition diagram –  
visualization of a finite state machine

## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

FSM - an abstract machine, defined as follows:

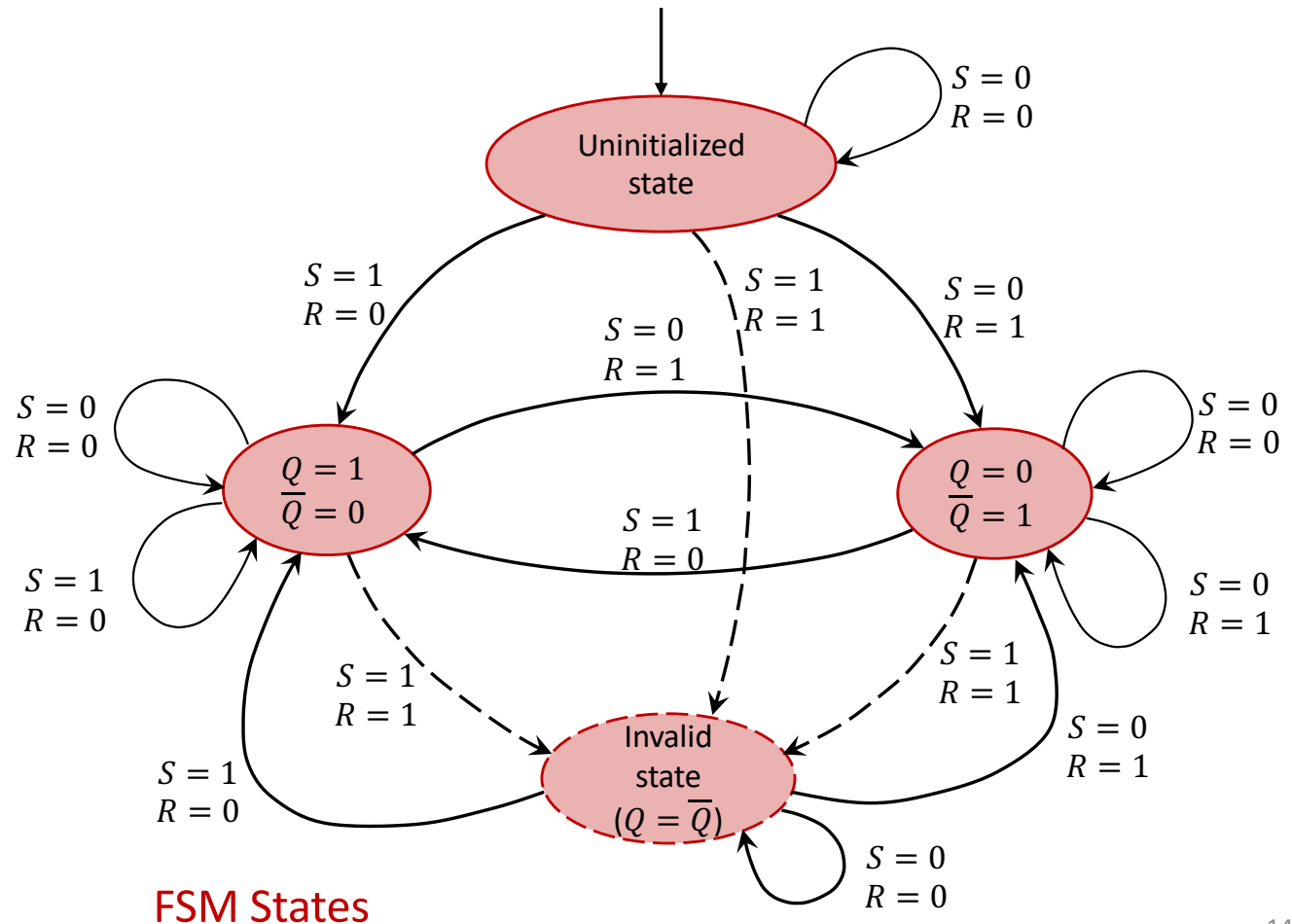
a) It can be in exactly one of a finite number of states at any given time;



## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

FSM - an abstract machine, defined as follows:

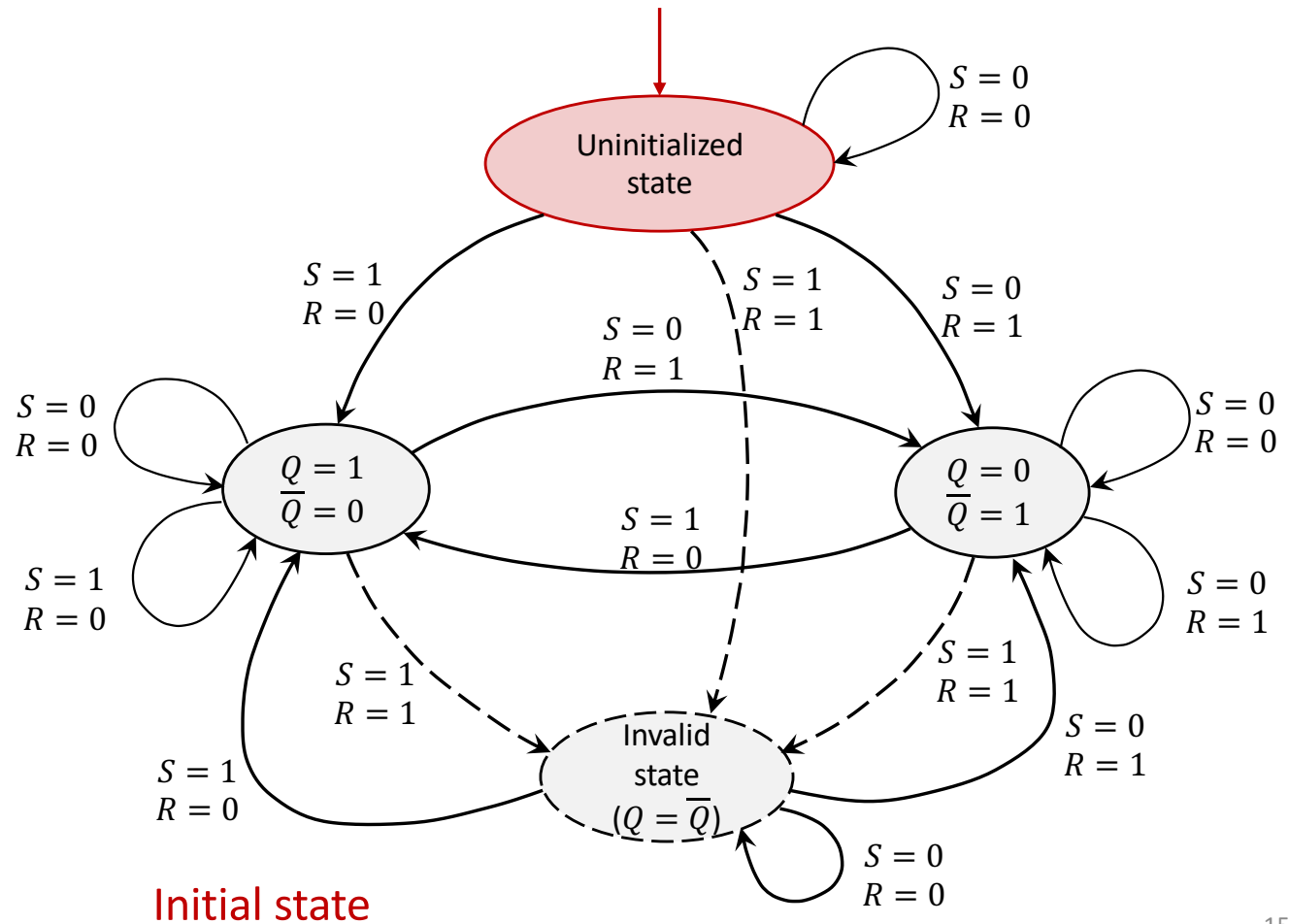
- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;



## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

FSM - an abstract machine, defined as follows:

 - a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside;






## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

FSM - an abstract machine, defined as follows:

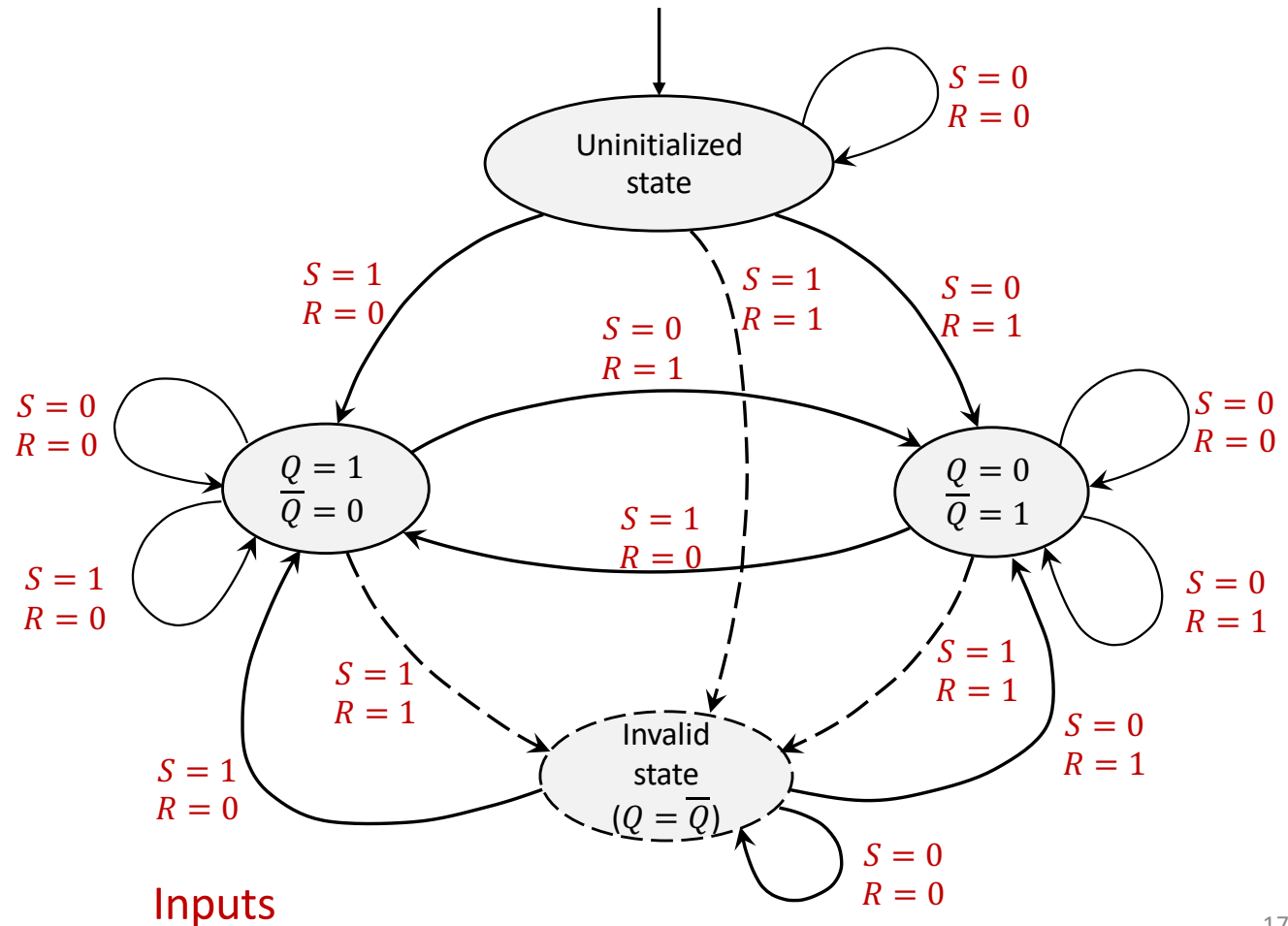
- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside;



## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

FSM - an abstract machine, defined as follows:

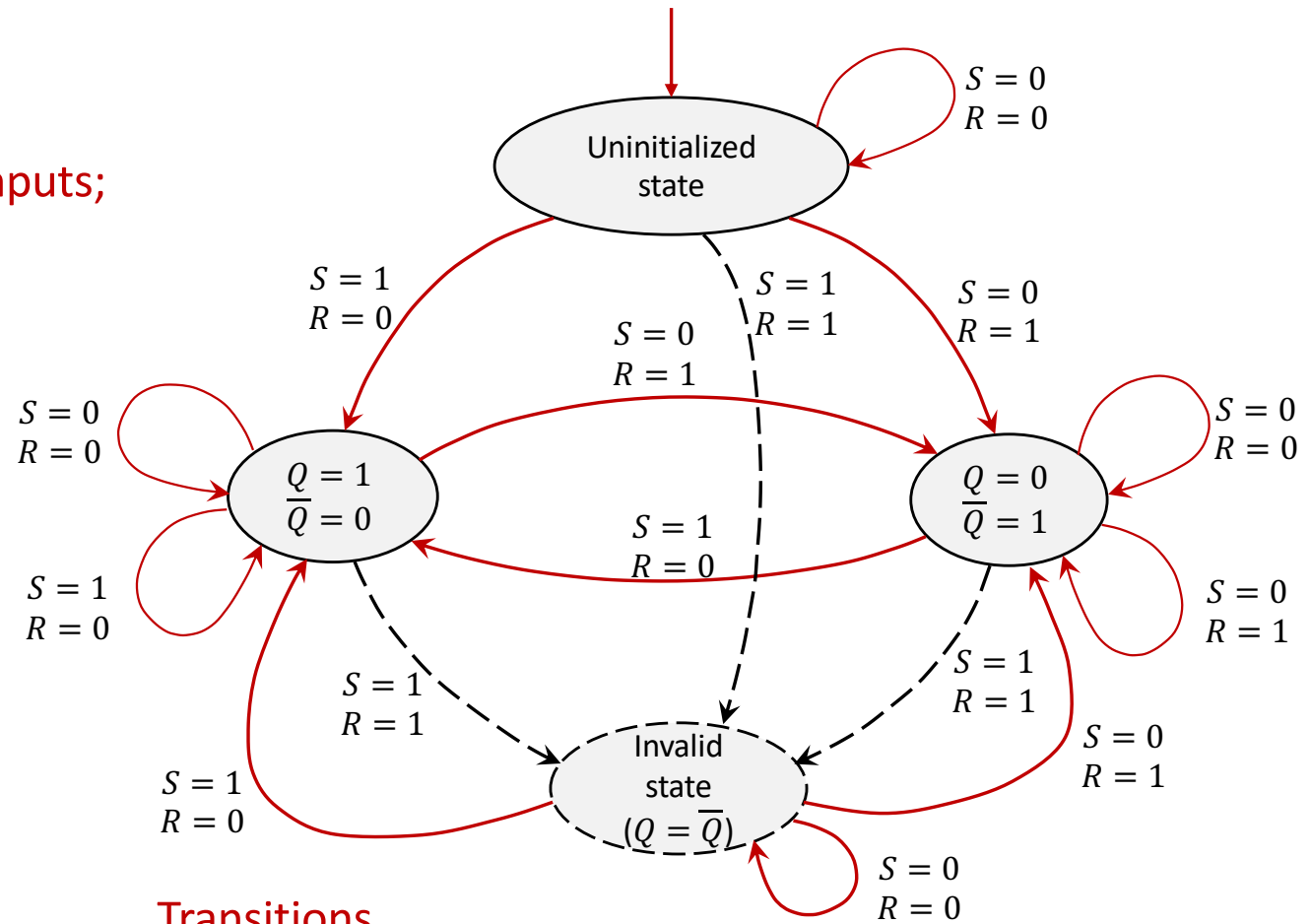
- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside;
- d) It changes its state in response to inputs;



## Finite State Machine (FSM) (or Finite State Automaton, or simply State Machine)

FSM - an abstract machine, defined as follows:

 - a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well




## Finite State Machine (FSM)

FSM - an abstract machine, defined as follows:

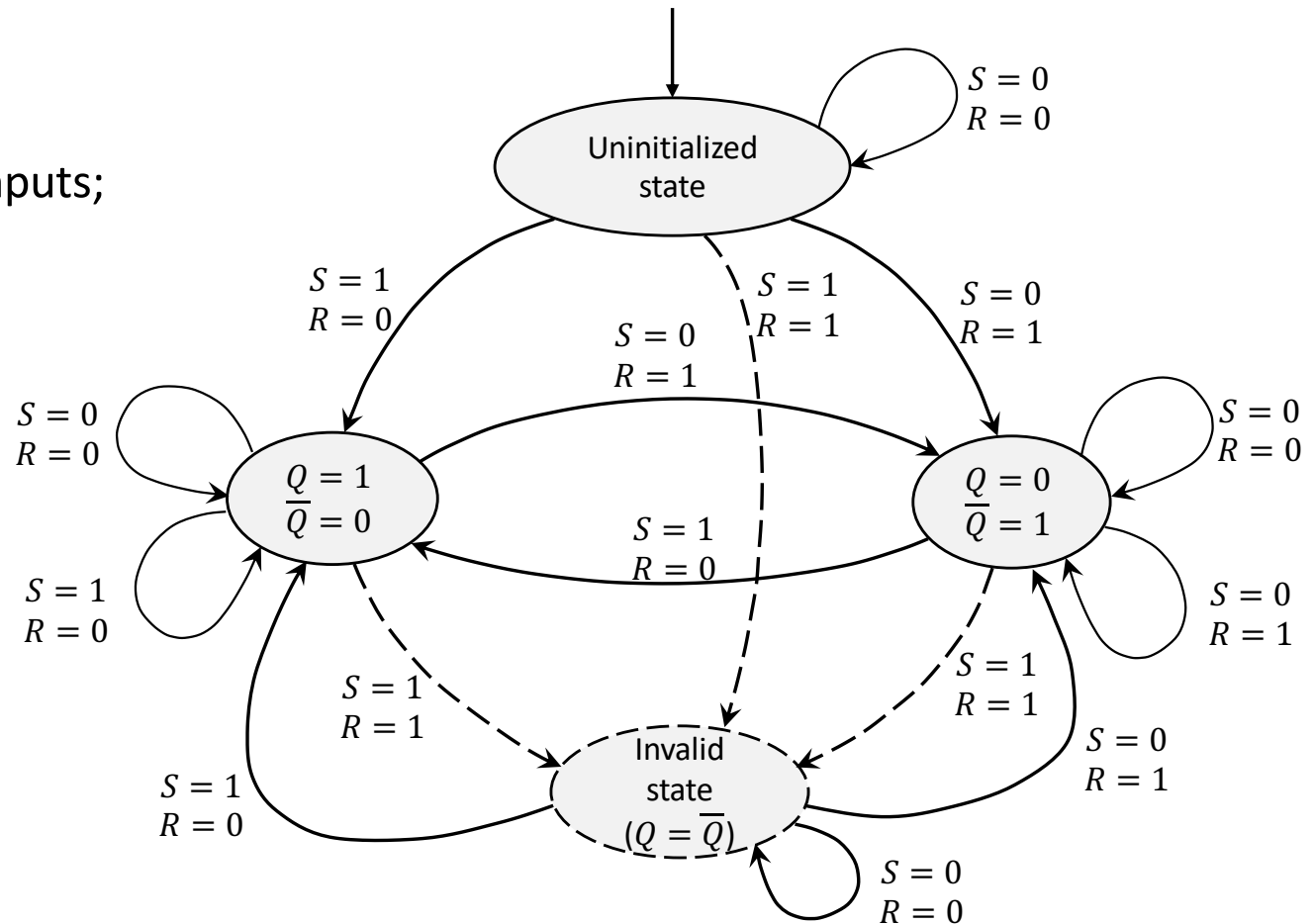- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well

This FSM is deterministic

(There is no state with two outgoing transitions for the same input)



## Finite State Machine (FSM)

FSM - an abstract machine, defined as follows:


- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well

This FSM is deterministic

(There is no state with two outgoing transitions for the same input)

Formalization:

 $S = \{s_0, s_1, \dots, s_n\}$  - set of states



## Finite State Machine (FSM)

FSM - an abstract machine, defined as follows:

- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well


This FSM is deterministic

(There is no state with two outgoing transitions for the same input)

Formalization:

$S = \{s_0, s_1, \dots, s_n\}$  - set of states

$I = \{i_0, i_1, \dots, i_k\}$  - inputs

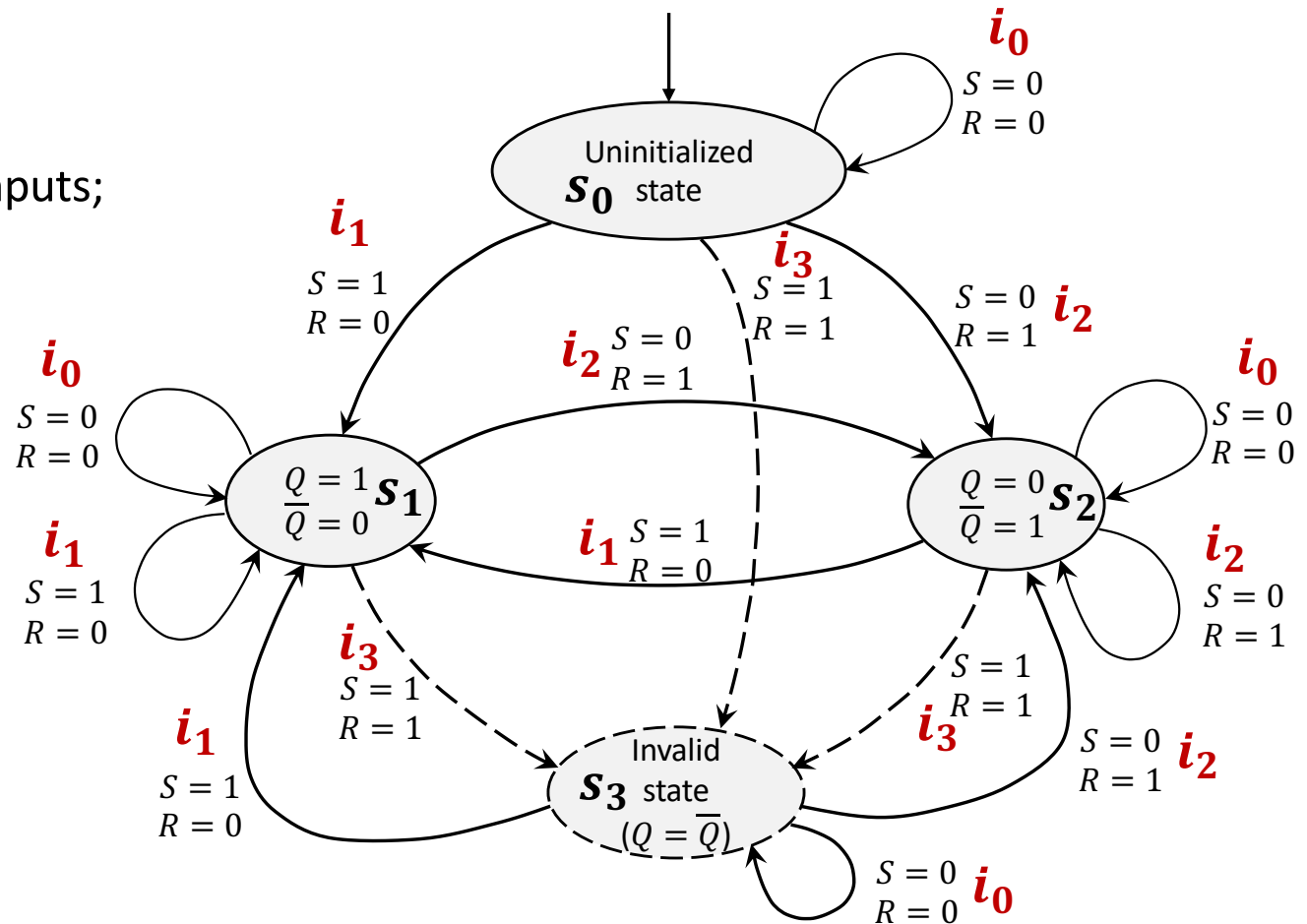

## Finite State Machine (FSM)

FSM - an abstract machine, defined as follows:

- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well

This FSM is deterministic


(There is no state with two outgoing transitions for the same input)

Formalization:

$S = \{s_0, s_1, \dots, s_n\}$  - set of states

$I = \{i_0, i_1, \dots, i_k\}$  - inputs

 $O = \{o_0, o_1, \dots, o_m\}$  - outputs



## Finite State Machine (FSM)

FSM - an abstract machine, defined as follows:

- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well

This FSM is deterministic

(There is no state with two outgoing transitions for the same input)


Formalization:

$S = \{s_0, s_1, \dots, s_n\}$  - set of states

$I = \{i_0, i_1, \dots, i_k\}$  - inputs

$O = \{o_0, o_1, \dots, o_m\}$  - outputs

 $F = (S \times I) \rightarrow (S \times O)$  - transition function





## Finite State Machine (FSM)

FSM - an abstract machine, defined as follows:

- a) It can be in exactly one of a finite number of states at any given time;
- b) Has one initial state;
- c) It gets inputs from outside
- d) It changes its state in response to inputs;
- e) It can produce output as well

This FSM is deterministic

(There is no state with two outgoing transitions for the same input)

Formalization:


$S = \{s_0, s_1, \dots, s_n\}$  - set of states

$I = \{i_0, i_1, \dots, i_k\}$  - inputs

$O = \{o_0, o_1, \dots, o_m\}$  - outputs


$F = (S \times I) \rightarrow (S \times O)$  - transition function

 State transition diagram – visualization of FSM



## Finite State Machine (FSM) Visualization

State transition diagram

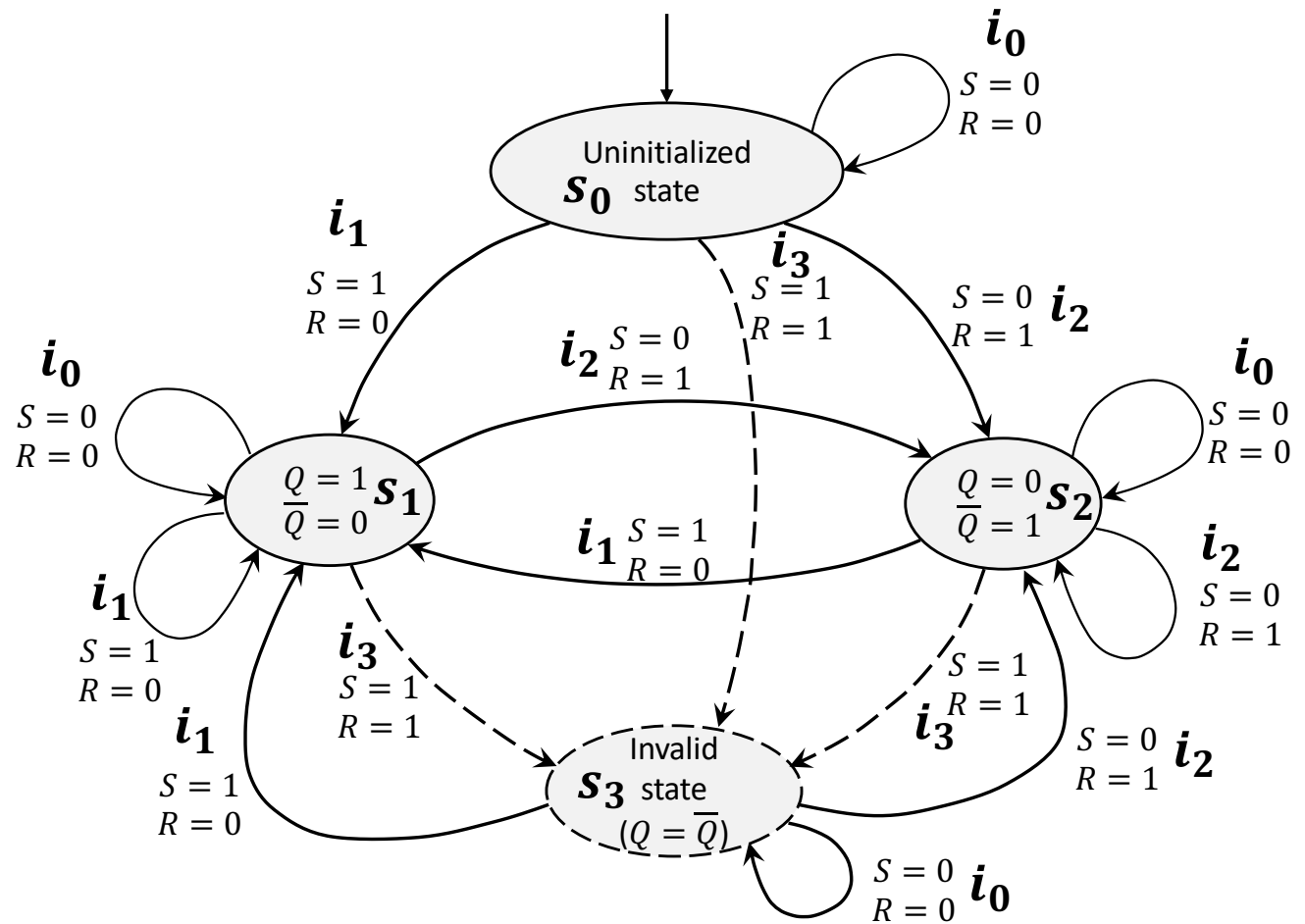


# Finite State Machine (FSM) Visualization


## Transition table – an alternative

Current state	Input	New state	Output
$s_0$	$i_0$	$s_0$	undefined
$s_0$	$i_1$	$s_1$	1
$s_0$	$i_2$	$s_2$	0
...			

## State transition diagram

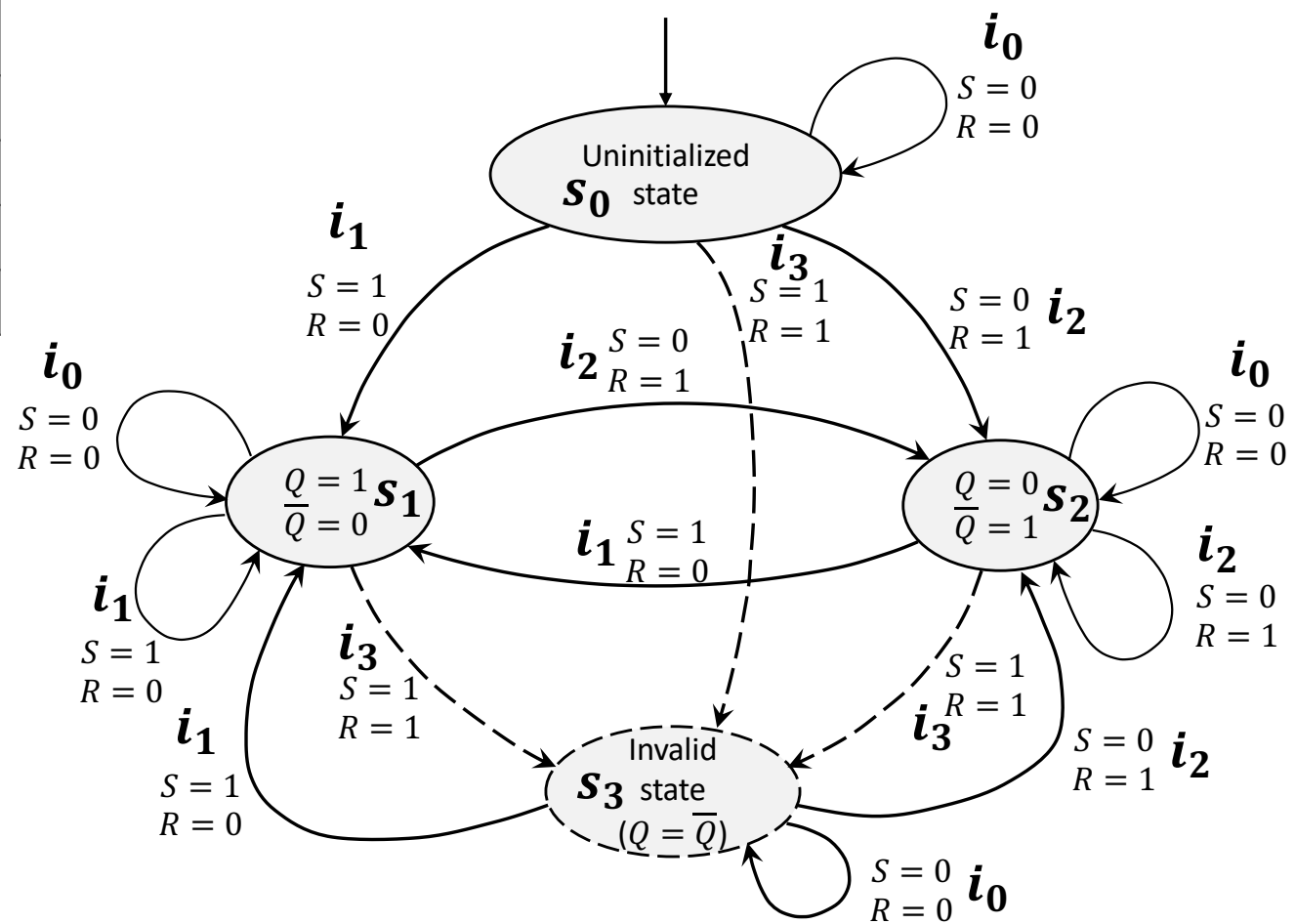


## Recap: Transparent S/R Latch

 

Set/Reset Latch  
(or transparent latch)

$S$	$R$	$Q$
1	0	1
0	1	0
0	0	$Q^{\text{prev}}$
1	1	Illegal inputs

 
## S/R Latch: A Less Detailed Representation




Set/Reset Latch  
(or transparent latch)

$S$	$R$	$Q$
1	0	1
0	1	0
0	0	$Q^{\text{prev}}$
1	1	Illegal inputs
 
## Enable Latch: An Alternative to S/R Latch




Set/Reset Latch  
(or transparent latch)

 


Enable Latch

 
## Enable Latch: An Alternative to S/R Latch




Set/Reset Latch  
(or transparent latch)

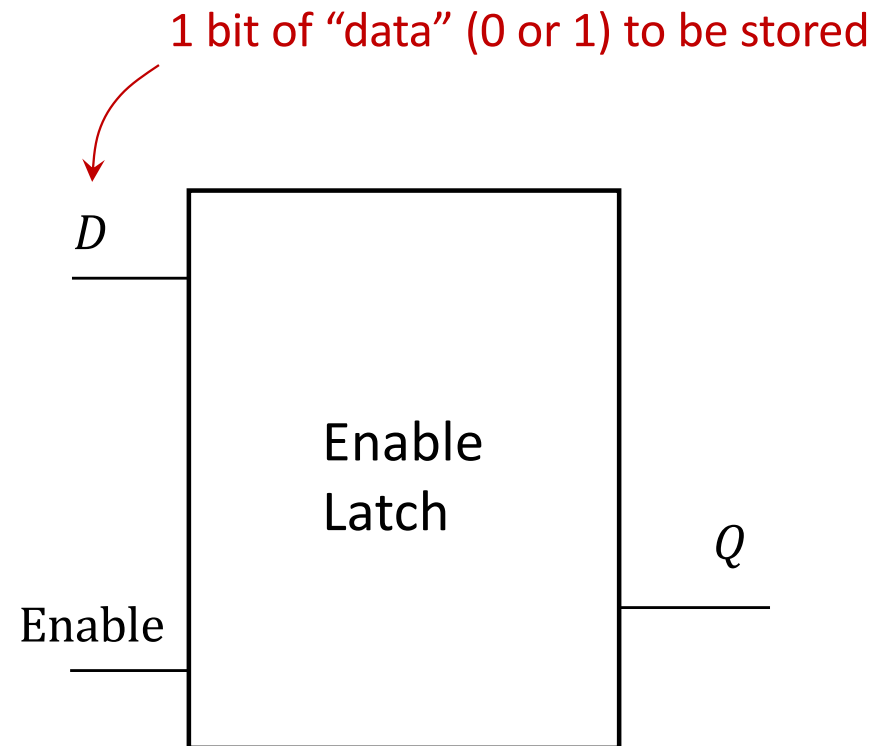
 
## Enable Latch: An Alternative to S/R Latch



Set/Reset Latch  
(or transparent latch)

 


Pin to enable data storage:  
- if set to "1", data is stored;  
- If set to "0", data is ignored



## Enable Latch: An Alternative to S/R Latch
 
### Advantage:

- No need to care about an invalid input combination (like  $S=1, R=1$  is prohibited for S/R latch);
- All input combinations allowed
- Simpler usage




## Enable Latch: An Alternative to S/R Latch

Advantage:

- No need to care about invalid input combination (like  $S=1, R=1$  is prohibited for S/R latch);
- All input combinations allowed
- Simpler usage

 Data is stored by latch, until a different value “D” arrives, at a time when pin “Enable” is activated




## Enable Latch: An Alternative to S/R Latch

Advantage:

- No need to care about invalid input combination (like  $S=1, R=1$  is prohibited for S/R latch);
- All input combinations allowed
- Simpler usage

 Data is stored by latch, until a different value “D” arrives, at a time when pin “Enable” is activated



## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger		
Clock Presence		
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	
Clock Presence		
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence		
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence		Clock governs the entire circuit activity
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)		
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		



## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)		Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	Less reliable (prone to incorrect result, subject to propagation delays)	Reliable (guarantees a correct result, independently of propagation delays)
Memory Element Presence		
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
<b>Memory Element Presence</b>		Used
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
<b>Memory Element Presence</b>	Not used	Used
Operation Speed		
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
<b>Operation Speed</b>	<b>Faster</b> (no clock signal for synchronisation delay is used)	
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
<b>Operation Speed</b>	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
Power Consumption		
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
<b>Power Consumption</b>	<b>Lower</b>	
Logical Complexity, Size (the number of elements)		
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
<b>Power Consumption</b>	<b>Lower</b>	<b>Higher</b> (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)		
Sample Use Cases		



## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
Power Consumption	<b>Lower</b>	<b>Higher</b> (e.g. due to the presence of flip-flops, consuming power for data storage)
<b>Logical Complexity, Size (the number of elements)</b>	<b>Simpler</b> , smaller ( <i>Note: an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity</i> )	
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
Power Consumption	<b>Lower</b>	<b>Higher</b> (e.g. due to the presence of flip-flops, consuming power for data storage)
<b>Logical Complexity, Size (the number of elements)</b>	<b>Simpler</b> , smaller ( <i>Note: an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity</i> )	<b>More complex</b> , larger
Sample Use Cases		

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
Power Consumption	<b>Lower</b>	<b>Higher</b> (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	<b>Simpler</b> , smaller ( <i>Note</i> : an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity)	<b>More complex</b> , larger
<b>Sample Use Cases</b>		Register files; Most of the circuits containing memory elements

## Synchronous vs. Asynchronous Circuits

Characteristic	Asynchronous (like S/R latch)	Synchronous (like Flip-Flop)
Output Update Trigger	Any change of one of the inputs	A clock signal, together with other input signals
Clock Presence	No clock present	Clock governs the entire circuit activity
Reliability (for result correctness)	<b>Less reliable</b> (prone to incorrect result, subject to propagation delays)	<b>Reliable</b> (guarantees a correct result, independently of propagation delays)
Memory Element Presence	Not used	Used
Operation Speed	<b>Faster</b> (no clock signal for synchronisation delay is used)	<b>Slower</b> (due to overpessimistic synchronisation delays)
Power Consumption	<b>Lower</b>	<b>Higher</b> (e.g. due to the presence of flip-flops, consuming power for data storage)
Logical Complexity, Size (the number of elements)	<b>Simpler</b> , smaller ( <i>Note</i> : an asynchronous circuit might behave as a synchronous, but at the price of a higher hardware implementation complexity)	<b>More complex</b> , larger
<b>Sample Use Cases</b>	Arithmetic-Logic Unit (ALU); Small fast peripheral circuits supporting CPU operation	Register files; Most of the circuits containing memory elements

# Digital Circuits Classification

